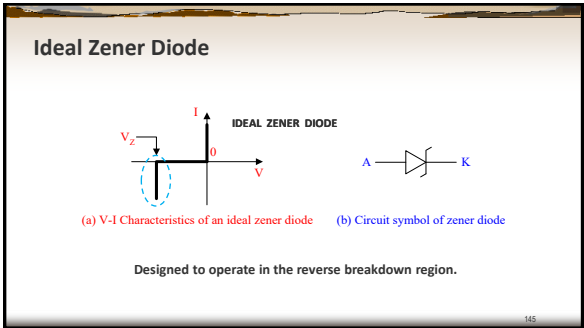



144



145

- ### The Zener Diode
- 1) Some Zener diodes use Zener breakdown ( $< 5V$ )
  - 2) Some Zener diodes use Avalanche breakdown ( $> 5V$ )
  - 3) Neither Zener nor avalanche breakdown are inherently destructive
  - 4) The heat generated by the large current flowing can cause damage in both cases.


146

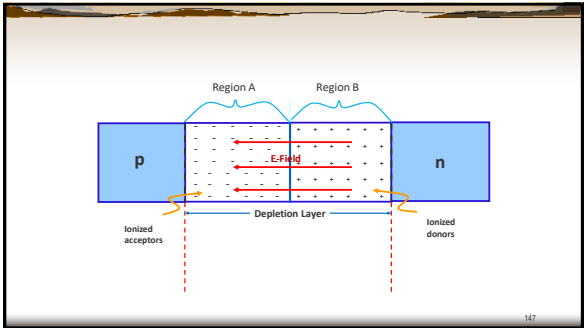

147

- ### Avalanche Breakdown
- ⇒ Doping is small. Depletion region is wide.
  - ⇒ The minority charge carriers get accelerated in this depletion region and gain kinetic energy.
  - ⇒ They knock off, other electrons from the valence
  - ⇒ Avalanche effect caused by Impact Ionization process.
  - ⇒ Occurs at higher reverse bias voltages ( $> 5V$ )
  - ⇒ More heat is generated.

148

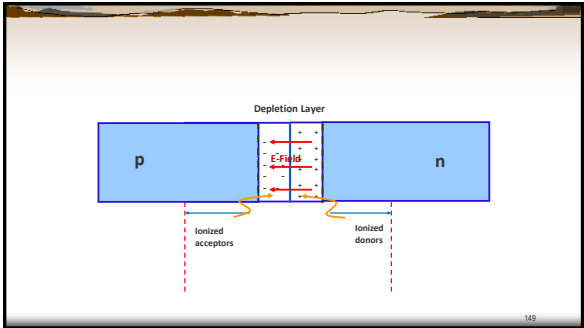

149

### Zener Breakdown

- ⦿ Doping is High. Depletion region is very thin.
- ⦿ Electric field very strong
- ⦿ Narrow depletion region does not allow many charge carriers to get accelerated.
- ⦿ No impact ionization. The Electric force pull off electrons from valance band and make them conduct. The effect is called **quantum tunneling**.
- ⦿ **Occurs at lower reverse bias voltages (<5V)**
- ⦿ **Less heat is generated.**

150

### The Zener Diode

151

### The Zener Diode

152

### Eg. Zener Impedance

153

### Eg.

A 1N4736 zener diode has a  $Z_{ZT}$  of  $3.5\ \Omega$ . The data sheet gives  $V_{ZT} = 6.8\text{ V}$  at  $I_{ZT} = 37\text{ mA}$  and  $I_{ZK} = 1\text{ mA}$ . What is the voltage across the zener terminals when the current is  $50\text{ mA}$ ?

For  $I_Z = 50\text{ mA}$ : The  $50\text{ mA}$  current is a  $13\text{ mA}$  increase above  $I_{ZT} = 37\text{ mA}$ .

$\Delta I_Z = I_Z - I_{ZT} = +13\text{ mA}$

$\Delta V_Z = \Delta I_Z Z_{ZT} = (13\text{ mA})(3.5\ \Omega) = +45.5\text{ mV}$

$V_Z = 6.8\text{ V} + \Delta V_Z = 6.8\text{ V} + 45.5\text{ mV} = \mathbf{6.85\text{ V}}$

154

### FWR with a smoothing circuit and a Zener Regulator

A simple zener voltage regulated dc power supply

155

### Voltage Regulation Using Zener Diode

In order to ensure the voltage regulation

$I_{ZK} < I_Z < I_{ZM}$

To make sure that the Zener diode enters to the reverse breakdown region

To make sure that the Zener diode is not destroyed

156

### Simple Zener Regulator Circuit

$I_T$  here is the DC voltage coming out from the capacitor filter. Its one variable

$I_L$  here is the current drawn by the load. Its another variable.

Irrespective of the variation of  $V_{in}$  and  $I_L$  the output voltage  $V_o$  should be regulated to the Zener voltage  $V_Z$

157

### Case 1 : Variable source with a constant load

$I_T = I_Z + I_L$

$I_Z = \left(\frac{V_{IN} - V_Z}{R}\right) - I_L$

$I_{ZK} < I_Z < I_{ZM}$

$I_{ZK} < \left(\frac{V_{IN} - V_Z}{R}\right) - I_L < I_{ZM}$

$I_{ZK} + I_L < \left(\frac{V_{IN} - V_Z}{R}\right) < I_{ZM} + I_L$

$[(I_{ZK} + I_L)R + V_Z] < V_{IN} < [(I_{ZM} + I_L)R + V_Z]$

158

### E.g. Variable source with a constant load

$I_T = I_Z + I_L$

$I_L = 20 \text{ mA}$

$V_O = V_Z = 12 \text{ V}$

$I_{ZK} = 1 \text{ mA}$   
 $I_{ZM} = 50 \text{ mA}$   
 $V_Z = 12 \text{ V}$   
 $R_Z = 0$

$I_Z = \left(\frac{V_{IN} - V_Z}{R}\right) - I_L$

$I_{ZK} < I_Z < I_{ZM}$

$1 \text{ mA} < \left(\frac{V_{IN} - 12}{0.47}\right) - 20 \text{ mA} < 50 \text{ mA}$

$21 < \left(\frac{V_{IN} - 12}{0.47}\right) < 70$

$21 \times 0.47 + 12 < V_{IN} < 70 \times 0.47 + 12$

$21.9 \text{ V} < V_{IN} < 44.9 \text{ V}$

159

### Ex. Variable source with a constant load

$I_T = I_Z + I_L$

$I_L = 20 \text{ mA}$

$V_O = V_Z = 12 \text{ V}$

$I_{ZK} = 1 \text{ mA}$   
 $I_{ZM} = 50 \text{ mA}$   
 $V_Z = 12 \text{ V}$   
 $R_Z = 0$

Find,

- Minimum and maximum currents in the Zener diode
- Minimum and maximum power dissipated in the Zener diode
- The rated power dissipation that the R should have.

maximum power that R dissipates

160

### Solution : Variable source with a constant load

$I_T = I_Z + I_L$

$I_L = 20 \text{ mA}$

$V_O = V_Z = 12 \text{ V}$

$I_{ZK} = 1 \text{ mA}$   
 $I_{ZM} = 50 \text{ mA}$   
 $V_Z = 12 \text{ V}$   
 $R_Z = 0$

$I_Z = \left(\frac{V_{IN} - V_Z}{R}\right) - I_L$

Solution:

- 20.4 to 33.2 mA
- 245.1 to 398.4 mW
- 1.33W

161

**Case 2 : Constant source with a variable load**

$I_Z = I_T - I_L$

$I_Z = \left( \frac{V_{IN} - V_Z}{R} \right) - I_L$

$I_{ZK} < I_Z < I_{ZM}$

$I_{ZK} < \left( \frac{V_{IN} - V_Z}{R} \right) - I_L < I_{ZM}$

$-I_{ZK} > -\left( \frac{V_{IN} - V_Z}{R} \right) + I_L > -I_{ZM}$

$\left( \frac{V_{IN} - V_Z}{R} \right) - I_{ZK} > I_L > \left( \frac{V_{IN} - V_Z}{R} \right) - I_{ZM}$

162

**Eg : Constant source with a variable load**

$I_T = \left( \frac{34 - 12}{0.47} \right) = 46.8 \text{ mA}$

$I_{ZK} = 1 \text{ mA}$   
 $I_{ZM} = 50 \text{ mA}$   
 $V_Z = 12 \text{ V}$   
 $R_Z = 0$

$I_{ZK} < I_Z < I_{ZM}$

$\left( \frac{V_{IN} - V_Z}{R} \right) - I_{ZK} > I_L > \left( \frac{V_{IN} - V_Z}{R} \right) - I_{ZM}$

$\left( \frac{34 - 12}{0.47} \right) - 1 > I_L > \left( \frac{34 - 12}{0.47} \right) - 50$

$46.8 - 1 > I_L > 46.8 - 50$

$45.8 \text{ mA} > I_L > 0$

$I_{Z, \text{min}} = 1 \text{ mA}$   
 $I_{Z, \text{max}} = 46.8 \text{ mA}$

$R_{L, \text{min}} = \left( \frac{V_Z}{45.8} \right) = 262 \Omega$

163

**Case 3 : Variable source with a variable load**

$I_Z < I_Z < I_{ZM}$

$I_{ZK} < \left( \frac{V_{IN} - V_Z}{R} \right) - I_L < I_{ZM}$

$I_{ZK} < \left( \frac{V_{IN} - V_Z}{R} \right) - I_L$        $\left( \frac{V_{IN} - V_Z}{R} \right) - I_L < I_{ZM}$

$I_{ZK} < \text{Min} \left[ \left( \frac{V_{IN} - V_Z}{R} \right) - I_L \right]$        $\text{Max} \left[ \left( \frac{V_{IN} - V_Z}{R} \right) - I_L \right] < I_{ZM}$

$I_{ZK} < \left( \frac{V_{IN, \text{min}} - V_Z}{R} \right) - I_{L, \text{max}}$        $\left[ \left( \frac{V_{IN, \text{max}} - V_Z}{R} \right) - I_{L, \text{min}} \right] < I_{ZM}$

164

**Case 3 : Variable source with a variable load**

$I_T = I_Z + I_L$

$I_L = 0 \text{ to } 40 \text{ mA}$

$I_{ZK} = 1 \text{ mA}$   
 $I_{ZM} = 50 \text{ mA}$   
 $V_Z = 12 \text{ V}$   
 $R_Z = 0$

$I_{ZK} < \left[ \left( \frac{32 - 12}{0.47} \right) - 40 \right]$        $\left[ \left( \frac{36 - 12}{0.47} \right) - 0 \right] < I_{ZM}$

$I_{ZK} < 2.55 \text{ mA}$        $51.06 < I_{ZM}$

165

**Considering Zener Impedance**

Determine the minimum and the maximum input voltages that can be regulated

$V_Z = 5.1 \text{ V}$  at  $I_{ZT} = 49 \text{ mA}$ ,  $I_{ZK} = 1 \text{ mA}$ , and  $Z_Z = 7 \Omega$  at  $I_{ZT}$ . For simplicity, assume this value of  $Z_Z$  over the range of current values.

166

**When Zener Impedance is to be considered...**

$V_Z = 5.1 \text{ V}$  at  $I_{ZT} = 49 \text{ mA}$ ,  $I_{ZK} = 1 \text{ mA}$ , and  $Z_Z = 7 \Omega$  at  $I_{ZT}$ . For simplicity, assume this value of  $Z_Z$  over the range of current values.

167

### Equivalent cct...

At  $I_{ZK} = 1 \text{ mA}$ , the output voltage is

$$V_{OUT} \approx 5.1 \text{ V} - \Delta V_Z = 5.1 \text{ V} - (I_{ZT} - I_{ZK})Z_Z$$
$$= 5.1 \text{ V} - (48 \text{ mA})(7 \Omega) = 5.1 \text{ V} - 0.336 \text{ V} = 4.76 \text{ V}$$
$$V_{IN(min)} = I_{ZK}R + V_{OUT} = (1 \text{ mA})(100 \Omega) + 4.76 \text{ V} = 4.86 \text{ V}$$

168

### Equivalent cct...

$$I_{ZM} = \frac{P_{D(max)}}{V_Z} = \frac{1 \text{ W}}{5.1 \text{ V}} = 196 \text{ mA}$$

At  $I_{ZM}$  the output voltage is

$$V_{OUT} \approx 5.1 \text{ V} + \Delta V_Z = 5.1 \text{ V} + (I_{ZM} - I_{ZT})Z_Z$$
$$= 5.1 \text{ V} + (147 \text{ mA})(7 \Omega) = 5.1 \text{ V} + 1.03 \text{ V} = 6.13 \text{ V}$$

Therefore,

$$V_{IN(max)} = I_{ZM}R + V_{OUT} = (196 \text{ mA})(100 \Omega) + 6.13 \text{ V} = 25.7 \text{ V}$$

169

### DC Power Supply

170

### Voltage Regulator ICs

IC regulators are available in the market.

**Regulator ICs**

Positive voltage regulator

7805 → 5V regulator  
7809 → 9V regulator  
7812 → 12V regulator

171

### Regulated DC Power Supply with IC regulator

172