

Design Simulation Activity

Name: PEIRIS E.A.S.S

Index No: 230469B

Course: EN1014 Electronic Engineering

(a) Simulated Results: Input V vs Output V

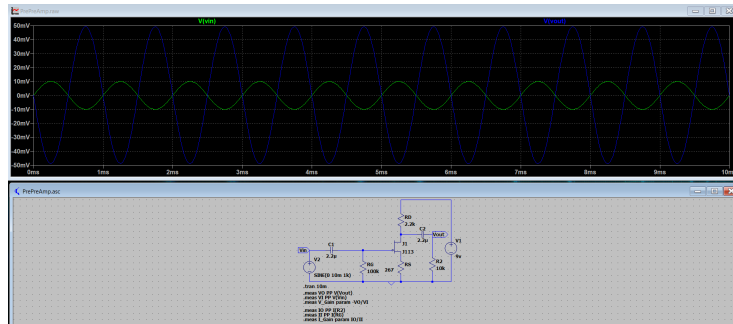


Figure 1: Simulated input and output waveforms with JFET circuit

Drawbacks

- The source resistor R_S introduces **negative feedback** to the input side. This reduces the gate-source voltage V_{GS} , thereby lowering the voltage gain.
- The quiescent point (Q-point) is not positioned at the center of the DC load line. As a result, when the input signal amplitude increases, the output waveform clips on the negative half-cycle.

 


Figure 2: Output waveform showing negative half-cycle clipping

(b) Design Improvements

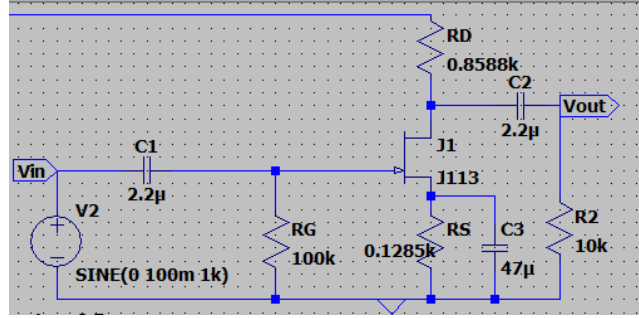


Figure 3: After design improvements

Q point

To center the Q-point on the DC load line, the drain current was chosen as:

$$I_D = \frac{I_{DSS}}{2} = \frac{9.116 \text{ mA}}{2} = 4.558 \text{ mA}$$

The corresponding gate-source voltage was calculated as:

$$V_{GS} = -0.5858 \text{ V}$$

Using Ohm's law, the resistor values were calculated as:

$$R_S = \frac{|V_{GS}|}{I_D} = \frac{0.5858}{4.558} \approx 0.1285 \text{ k}\Omega$$

$$R_D = \frac{V_{DD} - V_{DS(Q)}}{I_D} = \frac{9 - 4.5}{4.558} \approx 0.8588 \text{ k}\Omega$$

These resistor values reposition the Q-point to the center of the DC load line, allowing for maximum undistorted signal swing and improved amplifier performance.

Bypass capacitor

To increase the AC gain of the amplifier, a bypass capacitor was placed in parallel with the source resistor R_S . This capacitor effectively removes the negative feedback for AC signals while preserving the DC biasing condition.

The condition for proper bypassing is:

$$\frac{1}{2\pi fC} \ll R_S$$

Where:

- f is the lowest frequency of interest (guitar low E string: $f = 82.4 \text{ Hz}$),
- C is the capacitance of the bypass capacitor,
- $R_S = 0.1285 \text{ k}\Omega = 128.5 \Omega$.

We choose:

$$C = 47 \mu\text{F}$$

Calculating the capacitive reactance:

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \cdot 82.4 \cdot 47 \times 10^{-6}} \approx 40.9 \Omega$$

Now comparing:

$$X_C = 40.9 \Omega < R_S = 128.5 \Omega$$

This shows that the capacitor's impedance is significantly lower than R_S , satisfying the bypass condition for frequencies above 82.4 Hz.

Conclusion: A $47 \mu\text{F}$ capacitor effectively bypasses R_S for the frequency range of a guitar signal. It reduces AC negative feedback and increases the amplifier's gain while maintaining proper DC biasing.

Input Coupling Capacitor

The input coupling capacitor, together with the gate resistor R_G , forms a high-pass RC filter. This filter blocks DC components from the input signal and allows AC signals (i.e., the guitar signal) to pass.

The cutoff frequency f_c of a high-pass RC filter is given by:

$$f_c = \frac{1}{2\pi R_G C}$$

Where I Choose:

- $R_G = 100 \text{ k}\Omega$
- $C = 2.2 \mu\text{F}$

Substituting the values:

$$f_c = \frac{1}{2\pi \cdot 100 \times 10^3 \cdot 2.2 \times 10^{-6}} \approx 0.724 \text{ Hz}$$

Conclusion: The cutoff frequency is approximately 0.724 Hz, which is well below the lowest frequency produced by a guitar (82.4 Hz). Therefore, the high-pass filter formed by the input capacitor and gate resistor will allow all guitar frequencies to pass through with minimal attenuation.

```

vo: PP(V(Vout))=5.53386668503 FROM 0 TO 0.5
vi: PP(V(Vin))=0.20000000298 FROM 0 TO 0.5
v_gain: -VO/VI=-27.6693330129
io: PP(I(R2))=0.000553386681304 FROM 0 TO 0.5
ii: PP(I(RG))=2.00075209378e-06 FROM 0 TO 0.5
i_gain: IO/II=276.589330095

```

Figure 4: Gain Calculations After Design Improvements

(c) Gain Calculations After Design Improvements

$$\begin{aligned}
V_{\text{out(pp)}} &= 5.5339 \text{ V} \\
V_{\text{in(pp)}} &= 0.2000 \text{ V} \\
I_{\text{out(pp)}} &= 5.5387 \times 10^{-4} \text{ A} \\
I_{\text{in(pp)}} &= 2.0008 \times 10^{-6} \text{ A}
\end{aligned}$$

Voltage Gain

$$A_V = \frac{V_{\text{out(pp)}}}{V_{\text{in(pp)}}} = \frac{-5.5339}{0.2000} = -27.67$$

Current Gain

$$A_I = \frac{I_{\text{out(pp)}}}{I_{\text{in(pp)}}} = \frac{5.5387 \times 10^{-4}}{2.0008 \times 10^{-6}} \approx 276.59$$

Power Gain

$$A_P = A_V \times A_I = 27.67 \times 276.59 \approx 7652.6$$

Conclusion: The amplifier achieves a voltage gain of approximately 27.67, a current gain of 276.59, and a power gain of about 7652.6, indicating strong amplification across all domains.

(e) Need for a Power Amplifier After the Preamplifier

The JFET preamplifier is designed primarily to amplify weak input signals, such as those from a musical instrument, to a usable voltage level. However, it does not provide sufficient current or power to drive low-impedance loads such as speakers or headphones.

A **power amplifier** is therefore connected in cascade after the preamplifier for the following reasons:

- **Current and Power Drive:** The preamplifier has high voltage gain but limited current driving capability. Power amplifiers are designed to deliver large amounts of current and power to drive low-impedance loads (e.g., 8Ω speakers).
- **Impedance Matching:** Power amplifiers have low output impedance, allowing efficient power transfer to the load, whereas preamplifiers typically have high output impedance.
- **Load Isolation:** A power amplifier isolates the preamplifier from the effects of varying load conditions, ensuring stable operation and signal integrity.
- **Final Signal Boost:** The power amplifier provides the final amplification stage required to bring the signal up to a level suitable for audible output through a speaker system.

Conclusion: While the preamplifier conditions and amplifies the input signal voltage, the power amplifier ensures that the signal has sufficient power to effectively drive the intended output load.

Final Design with AC to DC Power supply

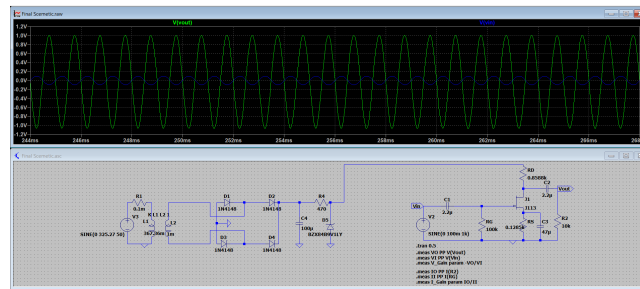


Figure 5: Final Design with AC to DC Power supply