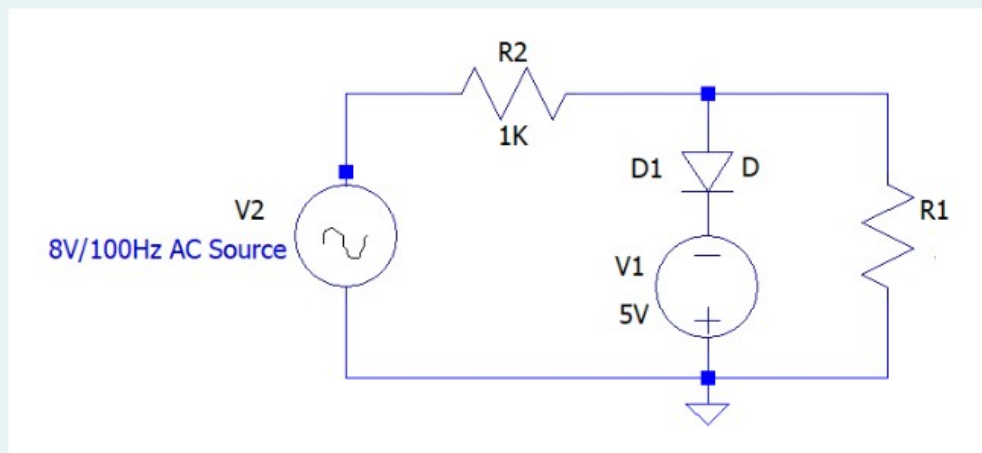


1.



The peak clipper circuit given above has a Load resistor R1 is $91\text{ k}\Omega$.

What is the magnitude of peak-to-peak load current variation ?

Use Si diode near-ideal diode model for your calculations.

Give your answer accurate to **two decimal places** in **Microamperes(μA)**

Answer:


2.

An input of $5\text{V}/50\text{Hz}$ is applied to a half wave rectifier operating with a load of $403\ \Omega$. The Silicon rectifier diode has a forward resistance of $10\ \Omega$. Find the peak current through the load in **mA**. Enter your answer to **two decimal places** of accuracy.

Answer:

15.43 mA

3.

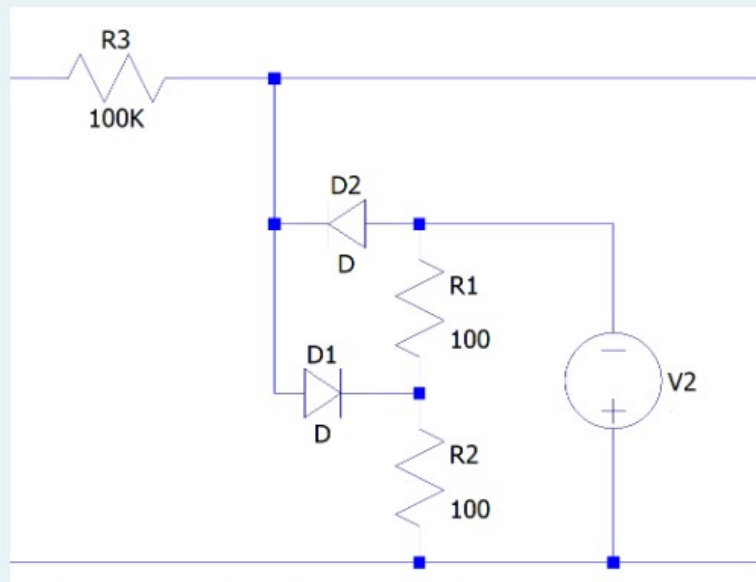

AC $230\text{V}/50\text{Hz}$ is applied to the input of the above circuit.

If V2 is 190 V DC Source, What is the magnitude of peak-to-peak output voltage variation in the dual peak clipping circuit given above?


Use Si diode near-ideal model to represent each diode,

Give your answer in **Volts**, correct to **two decimal places** of accuracy.

Answer:

96.4v

4.

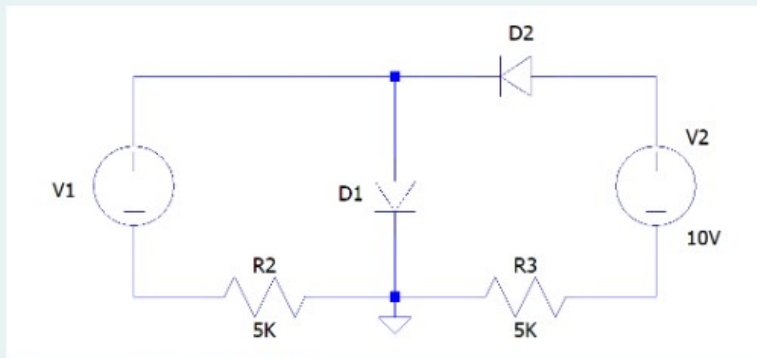

Voltage source V1 is set to 7 Volts.


What is the current through diode D1?

Use near-ideal diode model for your calculations.

Give your answer accurate to **two decimal places** in **Milliamperes**.

Answer:

5.

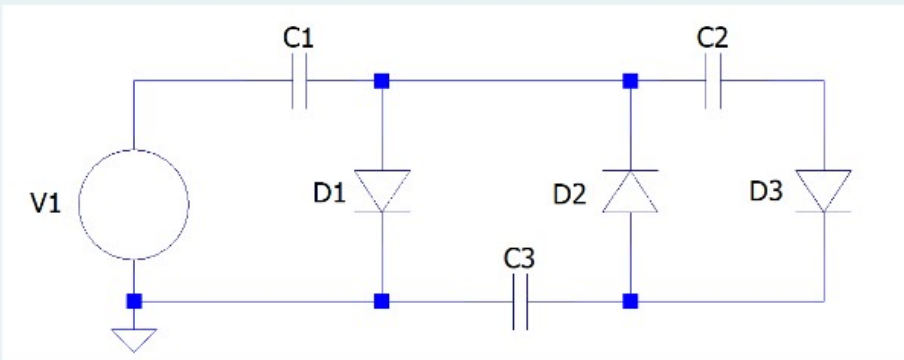

V1 is a 159V/50Hz AC source.

What is the magnitude of the DC voltage that appears across the C3 capacitor in **Volts**?

Use Si diode near-ideal diode model to represent each diode.

Give your answer correct to **two decimal places**.

Answer: