

Mathematical Solution by Iterative Method

$V_D = 26 \ln \left[\frac{(6000 - V_D)}{1000 \times 10.8 \times 10^{-12}} + 1 \right] \text{ mV}$

$V_D = 26 \ln \left[\frac{(6000 - 600)}{1000 \times 10.8 \times 10^{-12}} + 1 \right] = 700.3847$

$V_D = 26 \ln \left[\frac{(6000 - 700.3847)}{1000 \times 10.8 \times 10^{-12}} + 1 \right] = 699.8968$

$V_D = 26 \ln \left[\frac{(6000 - 699.8968)}{1000 \times 10.8 \times 10^{-12}} + 1 \right] = 699.8992$

$V_D = 699.8992 \text{ mV} \approx 0.7 \text{ V}$

$V_D = \eta V_T \ln \left[\frac{(E - V_D)}{R \cdot I_S} + 1 \right]$

$I = \frac{E - V_D}{R} = \frac{6 - 0.7}{1} = 5.3 \text{ mA}$

82

Superimposing an AC drive signal :

Superimpose an AC signal of $1.\sin(\omega t)\text{V}$ on the DC 6V

$[6 + 1.\sin(\omega t)] \text{ V}$ v_m $R = 1000 \Omega$ I_D

83

DC Analysis

$Q = [V_{D,Q}, I_{D,Q}] = [0.7\text{V}, 5.3\text{mA}]$

Q Point: The intersection of the load line and the transconductance curve.

$I_{D,Q} = 5.3$

$V_{D,Q} = 0.7$

$V_D = 1.4$

84

AC Analysis

$[6 + 1.\sin(\omega t)] \text{ V}$ v_m $R = 1000 \Omega$ $I_D = 5.3 \text{ mA}$

$r_d = \frac{\eta V_T}{I_D} = \frac{1 \times 26 \text{ mV}}{5.3 \text{ mA}} = 4.9 \Omega$

$v_{ac} = \frac{r_d}{r_d + R} \sin(\omega t)$

$v_{ac} = \frac{4.9}{4.9 + 1000} \sin(\omega t)$

$v_{ac} = 4.88 \sin(\omega t) \text{ mV}$

$V_D = [700 + 4.9 \sin(\omega t)] \text{ mV}$

85

Visualizing graphically

v_m $R = 1000 \Omega$ I_D

$r_d = \frac{\eta V_T}{I_D} = \frac{1.26 \text{ mV}}{5.3 \text{ mA}} = 4.9 \Omega$

Q Point

$V_D = 1.4$

86

Mathematical Solution (dc+ac)

Let the source voltage is $v_m = 6 + \sin(\omega t)$ Volts.

$v_m = 6 + \sin(\omega t) \text{ V}$ $R = 1000 \Omega$ $I = I_D$

$I = I_S \left[e^{\frac{V_D}{\eta V_T}} - 1 \right]$

$\frac{I}{I_S} = e^{\frac{V_D}{\eta V_T}} - 1$

$\frac{I}{I_S} + 1 = e^{\frac{V_D}{\eta V_T}}$

$\frac{V_D}{\eta V_T} = \ln \left[\frac{I}{I_S} + 1 \right]$

$I = I_S \left[e^{\frac{V_D}{\eta V_T}} - 1 \right]$

$V_D = \eta V_T \ln \left[\frac{I}{I_S} + 1 \right]$

$V_D + IR = V_{in}$

$I = \frac{V_{in} - V_D}{R}$

$V_D = \eta V_T \ln \left[\frac{(V_{in} - V_D)}{I_S R} + 1 \right]$

$V_D = \eta V_T \ln \left[\frac{(6 + \sin \omega t - V_D)}{I_S R} + 1 \right] \parallel$


87

Mathematical Solutions with Different Diode Abstraction Models

- Different abstractions can be used when analyzing diode circuits.
- Choice depends on the desired accuracy of your circuit calculations.
- These are also called Piecewise linear models

88


Model 1 : Ideal Diode Model

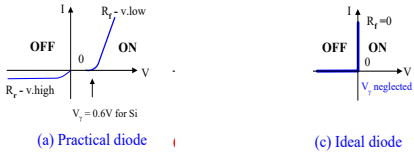

89


Model 1 : Ideal Diode Model

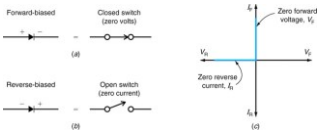This abstraction treats a forward-biased diode like a switch with a voltage drop of zero volts.



90


Model 1 : Ideal Diode Model

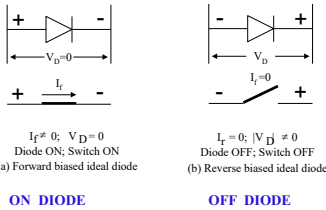

91

Model 1 : Ideal Diode Model

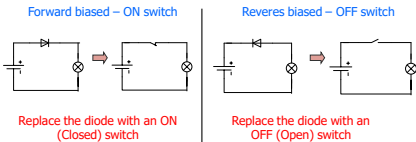
- Ideal diode model.
Ideal diode (which is hypothetical but makes the analysis simpler) is like an ON-OFF switch.



92

Model 2 : Near(Nearly) Ideal Diode Model

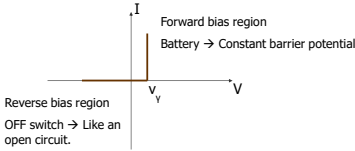
- The earlier model (approximation) didn't consider the barrier potential which is peculiar to diodes. This model takes that also in to account, hence it is more realistic.



95


Model 2 : Near(Nearly) Ideal Diode Model

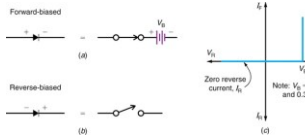This approximation treats a forward-biased diode like an ideal diode in series with a battery.



96


Nearly Ideal Diode Graphical Abstraction

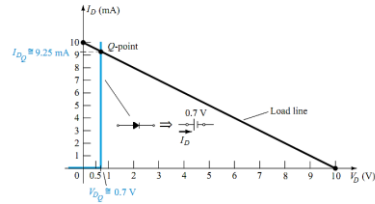

98


Model 3 : Three-piece Diode Model

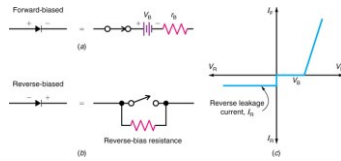- The third approximation of a diode includes the **bulk resistance**, r_B .
- The bulk resistance, r_B is the resistance of the p and n materials.




99

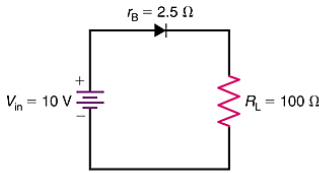Tutorial Question:
Find the Load voltage using each model...




100

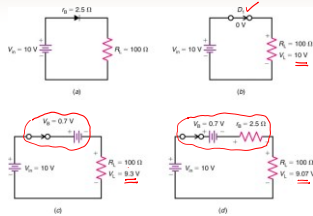

101

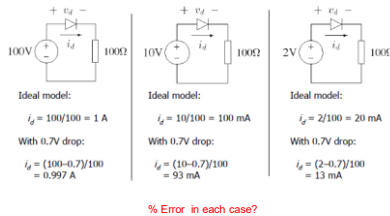Tutorial Question : Circuit current? Which model to use?



102

Which model to use?

The choice depends on the external voltage magnitudes.

103

Tutorial Question
Find the potential across the diode in each circuit.
Use Near Ideal Model.

(a) -3 V (b) 0.7 V (c) 0.7 V (d) 0.7 V

104

Troubleshooting...
Find the problem in each circuit

(a) (b) (c) (d)

105

DC Power Supply
Block schematic diagram

AC input V_{ac} → Rectifier → Filter → Regulator → Load

106

Diode as a Rectifier

(a) Half-wave rectifier

107

Half wave Rectifier (HWR)

(b) Positive half-cycle
(c) Negative half cycle

108

Half wave Rectifier

ac input

(a) Half-wave rectifier

dc output

109

Average Voltage (DC Level)

$V_{AVG} = \frac{V_p}{\pi} = \frac{50\text{ V}}{\pi} = 15.9\text{ V}$

110

Average Voltage (DC Level)

$v = V_p \sin \theta$

$$V_{AVG} = \frac{\text{area}}{2\pi} = \frac{1}{2\pi} \int_0^\pi V_p \sin \theta \, d\theta = \frac{V_p}{2\pi} (-\cos \theta) \Big|_0^\pi$$
$$= \frac{V_p}{2\pi} [-\cos \pi - (-\cos 0)] = \frac{V_p}{2\pi} [-(-1) - (-1)] = \frac{V_p}{2\pi} (2)$$
$$V_{AVG} = \frac{V_p}{\pi}$$

111

RMS value

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) \, dt}$$
$$= \sqrt{\frac{1}{2\pi} \int_0^\pi V_p^2 \sin^2 \theta \, d\theta + \int_\pi^{2\pi} 0 \, d\theta}}$$
$$= \sqrt{\frac{V_p^2}{2\pi} \int_0^\pi \sin^2 \theta \, d\theta}}$$
$$\sin^2 \theta = \frac{1}{2} (1 - \cos 2\theta), \quad \theta = 0 \text{ to } \pi$$
$$V_{rms} = \sqrt{\frac{V_p^2}{4\pi} \int_0^\pi (1 - \cos 2\theta) \, d\theta}}$$
$$= \sqrt{\frac{V_p^2}{4\pi} \left[\theta - \frac{1}{2} \sin 2\theta \right]_0^\pi}}$$
$$= \sqrt{\frac{V_p^2}{4\pi} \left(\pi - \frac{1}{2} \sin(2\pi) - 0 + \frac{1}{2} \sin(0) \right)}}$$
$$= \sqrt{\frac{V_p^2}{4\pi} (\pi - 0 - 0 + 0)}}$$
$$= \frac{V_p}{2}$$

112

Form Factor

Form Factor(F) = $\frac{\text{rms value}}{\text{average value}}$

$$F = \frac{\frac{V_m}{2}}{\frac{V_m}{\pi}}$$
$$F = \frac{\pi}{2}$$
$$F = 1.57$$

113

Efficiency at DC Load

$\eta = (\text{dc output power} / \text{total input power to load}) \times 100\%$

$$\eta = \frac{V_{dc}^2 / R_L}{V_{rms}^2 / R_L} = \frac{(V_m / \pi)^2}{(V_m / 2)^2} = \frac{4}{\pi^2} = 0.406$$

or

$$\eta = 40.6\%$$

114

Ex: Find Average Voltage (DC Level)

$V_{p(sec)} = V_{p(sec)} - 0.7\text{ V} = 5\text{ V} - 0.7\text{ V} = 4.30\text{ V}$

$V_{p(sec)} = V_{p(sec)} - 0.7\text{ V} = 100\text{ V} - 0.7\text{ V} = 99.3\text{ V}$

115

With Transformer Coupling

116

With Transformer Coupling

$V_{p(sec)} = V_{p(sec)} - 0.7\text{ V} = 78\text{ V} - 0.7\text{ V} = 77.3\text{ V}$

117

Full Wave Rectifier

$V_{dc} = 2(V_{max})/\pi$

AC input and DC output voltage waveforms

118

Example...

$V_{AVG} = \frac{2V_p}{\pi} = \frac{2(15\text{ V})}{\pi} = 9.55\text{ V}$

119

Diode in a Full Wave Rectifier

Center tapped transformer type

120

Diode in a Full Wave Rectifier

Centre-tapped transformer type full-wave rectifier giving a dc output across a load resistor R_L

121

(a) During positive half-cycles, D_1 is forward-biased and D_2 is reverse-biased.

(b) During negative half-cycles, D_2 is forward-biased and D_1 is reverse-biased.

122

Peak Inverse Voltage of Each Diode

$V_{P(out)} = \frac{1}{2} V_{P(sec)} - 0.7$

$PIV = V_{P(sec)} - 0.7 = 2V_{P(out)} + 0.7$

123

Tutorial Question: Find PIV of the diodes

Find PIV of the diodes

124

Solution

$PIV = 2V_{P(out)} + 0.7 = 2(24.3 \text{ V}) + 0.7 \text{ V} = 49.3 \text{ V}$


125

Bridge Type Full Wave Rectifier


(a) Bridge circuit diagram

(b) Output voltage waveform


126

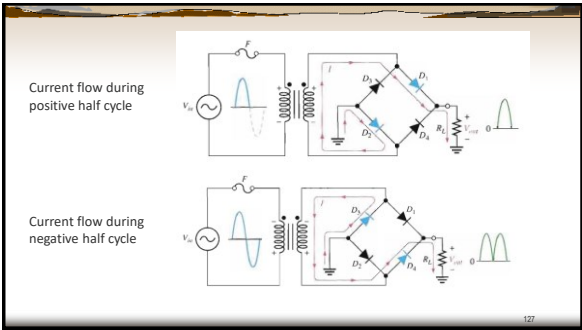


127

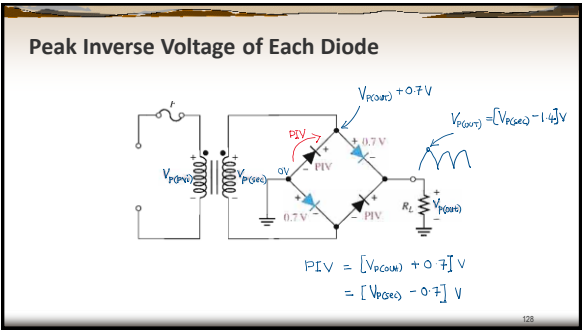


128

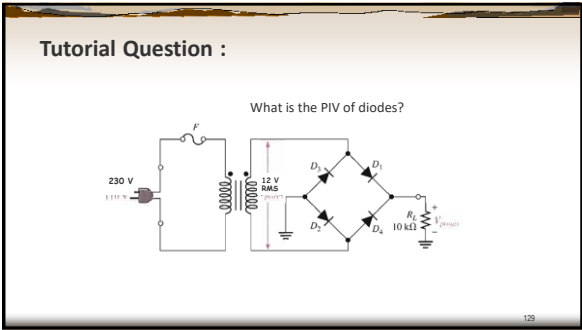


129

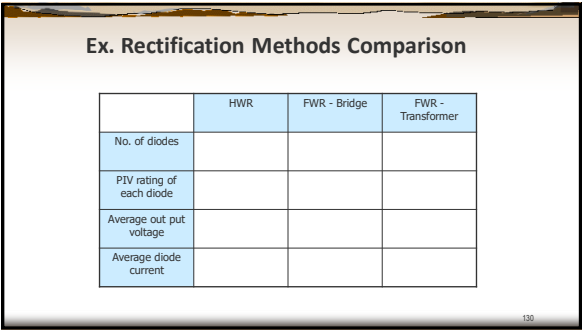

130

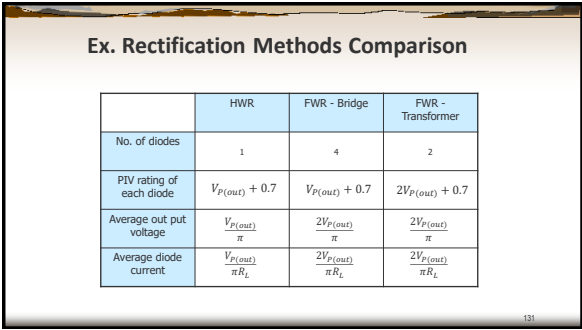


131

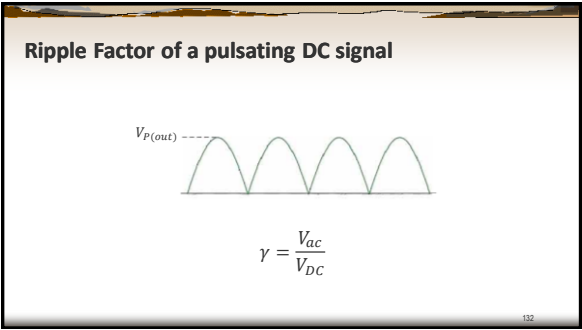

132

Ripple Factor at the Rectifier Output

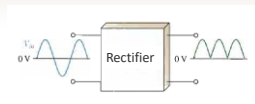

$$HWR\ RF = \sqrt{\left[\frac{V_{P(out)}}{2}\right]^2 - 1} = 1.21$$


$$FWR\ RF = \sqrt{\left[\frac{V_{P(out)}}{2\sqrt{2}}\right]^2 - 1} = 0.48$$

$$V_{rms} = \sqrt{(V_{DC})^2 + (V_{ac})^2}$$

$$\frac{V_{ac}}{V_{DC}} = \sqrt{\left[\frac{V_{rms}}{V_{DC}}\right]^2 - 1}$$


133

Connecting a Smoothing Circuit

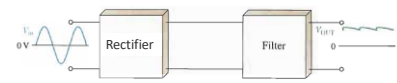

134

Smoothing by a capacitor filter

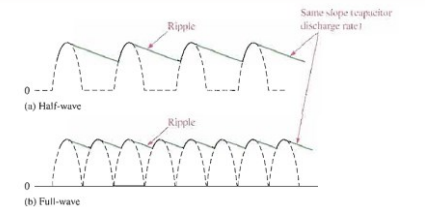


(a) Half-wave

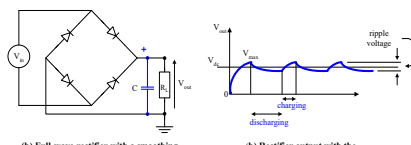(b) Full-wave

135

E.g. Consider a FWR with a capacitor smoothing circuit




(b) Full-wave rectifier with a smoothing capacitor

(b) Rectifier output with the capacitor

136

Ripple Voltage

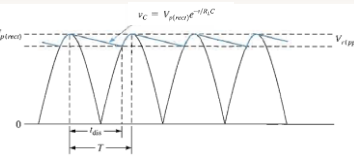

$$V_C = V_{P(rec)} e^{-t/R_L C}$$

$$V_{C(min)} = V_{P(rec)} e^{-T/R_L C}$$

$$V_{C(max)} = V_{P(rec)}$$


$$V_{C(PP)} = V_{C(max)} - V_{C(min)}$$

$$V_{C(PP)} = V_{P(rec)} \left(1 - e^{-T/R_L C}\right)$$

$$V_{C(PP)} \approx \left(\frac{1}{f R_L C}\right) V_{P(rec)}$$

137

Ripple Voltage

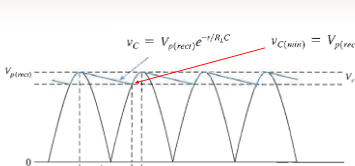

$$V_C = V_{P(rec)} e^{-t/R_L C}$$

$$V_{C(min)} = V_{P(rec)} e^{-T/R_L C}$$


$$V_{C(max)} = V_{P(rec)}$$

$$V_{C(PP)} = V_{C(max)} - V_{C(min)}$$


$$V_{C(PP)} = V_{P(rec)} \left(1 - e^{-T/R_L C}\right)$$

$$V_{C(PP)} \approx \left(\frac{1}{f R_L C}\right) V_{P(rec)}$$


138

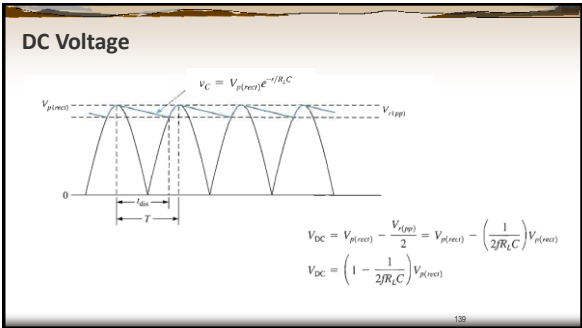


139

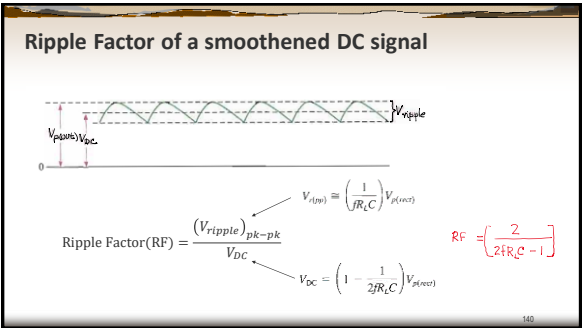


140

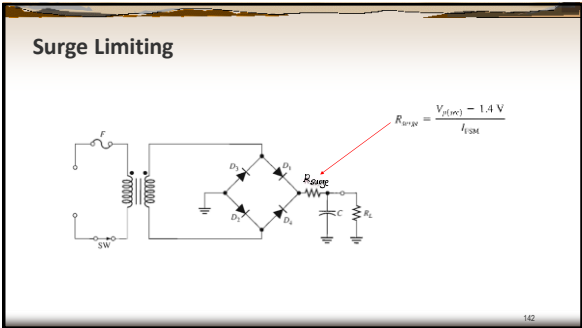


142

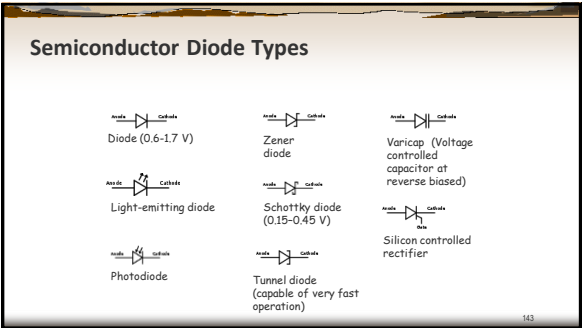

143

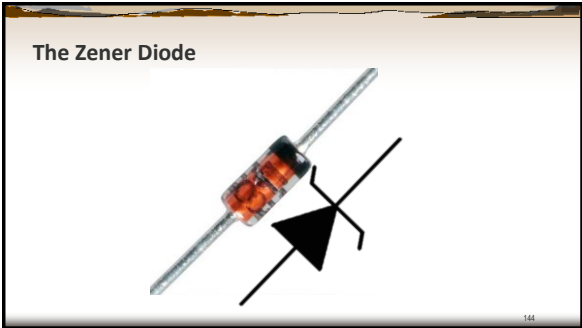

144

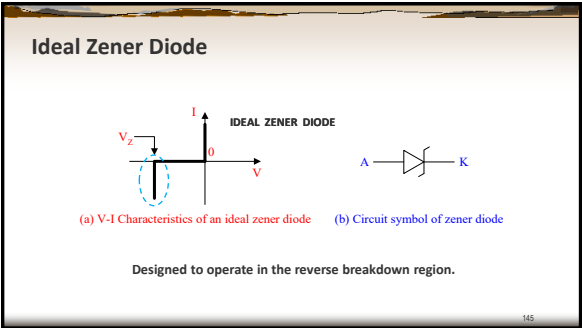

145

The Zener Diode

- 1) Some Zener diodes use Zener breakdown ($< 5V$)
- 2) Some Zener diodes use Avalanche breakdown ($> 5V$)
- 3) Neither Zener nor avalanche breakdown are inherently destructive
- 4) The heat generated by the large current flowing can cause damage in both cases.

146

146