

OPERATIONAL AMPIIFIER

OPAMPs & Applications


1

Kithsiri Samarasinghe
Senior Lecturer, Dept. of ENTC, UoM

1

An OPAMP is...


- An Integrated Circuit (IC) Voltage amplifier with two differential inputs and a single output
- A very popular Building block in designing Electronic Circuits.




2

2

An OPAMP IC

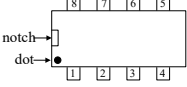

(a) top view

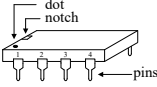


(b) side view

8-pin chip

3

3

The 741 OPAMP

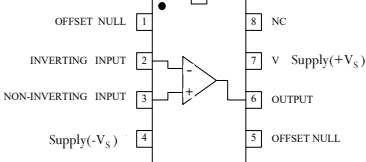


Pin configuration of op-amp IC 741

4

4

Terminals in a OPAMP

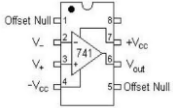
- Inputs
 - Non-inverting input (V^+ or V_1)
 - Inverting input (V^- or V_2)
- Outputs
 - Output (V_{out})
- Power Supply
 - Positive power supply ($+V_S$ or $+V_{CC}$)
 - Negative power supply ($-V_S$ or $-V_{CC}$)



5

5

Differential Input and Differential Gain

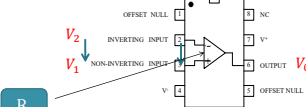


Pin configuration of op-amp IC 741

$$V_{id} = V_1 - V_2$$
$$V_0 = A_{vd} \cdot (V_{id})$$
$$V_0 = A_{vd} \cdot (V_1 - V_2)$$

6

6

OPAMP Circuit Symbol

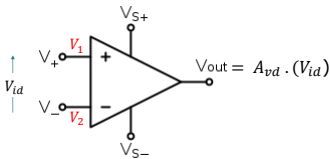


Ideal Op-Amp Characteristics

- Infinite open-loop gain
- Infinite input impedance
- Zero output impedance
- Infinite bandwidth

The Virtual Short Circuit

$V_{id} = V_1 - V_2$
 $V_o = A_{vd} \cdot (V_{id})$
 $V_o = A_{vd} \cdot (V_1 - V_2)$
 $\frac{V_o}{A_{vd}} = (V_1 - V_2)$
 $(V_1 - V_2) = 0$
 $V_1 = V_2$

Ideal OPAMP : I/O Characteristics

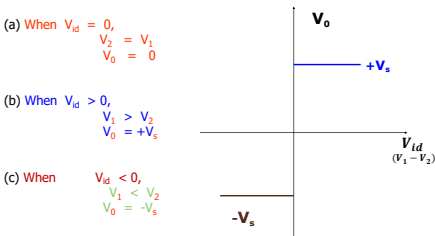

OPAMP Applications

Application Circuits

- 1) Voltage Comparator
- 2) Unity Gain Amplifier/Voltage Follower/Buffer Circuit
- 3) Non-Inverting Amplifier
- 4) Inverting Amplifier
- 5) Scaling Adder
- 6) Scaling Subtractor
- 7) Instrumentation Amplifier
- 8) Integrator
- 9) Differentiator
- 10) Constant Current Source
- 11) Current to Voltage Converter
- 12) Voltage to Current Converter/Transconductance Amplifier
- 13) Output Bounding Circuit
- 14) Schmidt Trigger

1) Voltage Comparator

If $(V) = 0$
It is called a Zero Comparator

If $(V) = V_{TH}$
It is called a Threshold Detector or a Level Detector

13

Example

IF $R1 = R2 = 10K$
What is V_o ?

$V_o = 0$

14

Example (Cont.)

15

2) Unity Gain Amplifier

$V_o = A_{vd} \cdot (V_{id})$
 $V_o = A_{vd} \cdot (V_1 - V_2)$
 $V_o = A_{vd} \cdot (V_i - V_o)$
 $\frac{V_o}{A_{vd}} = (V_i - V_o)$
 $(V_i - V_o) = 0$
 $V_i = V_o$

- 100% negative feedback.
- So gain is unity
- Pass both dc and ac
- Takes no current from input
- High current drives available to the load

16

3) Inverting Amplifier

$V_1 = V_2 = 0$
 $V_p = 0$

17

Inverting Amplifier

$A_v = -\left(\frac{R_f}{R}\right)$

$I_i + I_f = 0$
 $\left(\frac{V_i - V_p}{R}\right) + \left(\frac{V_o - V_p}{R_f}\right) = 0$
 $\left(\frac{V_i - 0}{R}\right) + \left(\frac{V_o - 0}{R_f}\right) = 0$

$\left(\frac{V_i}{R}\right) + \left(\frac{V_o}{R_f}\right) = 0$
 $\left(\frac{V_i}{R}\right) = -\left(\frac{V_o}{R_f}\right)$
 $A_v = \frac{V_o}{V_i} = -\left(\frac{R_f}{R}\right)$

18

Inverting Amplifier

$$A_v = -\left(\frac{R_f}{R}\right)$$

- Vol. gain totally depend on the two resistors.
- Opamp provides the virtual short circuit and current drive
- Amplify **ac and dc components of input signal by same gain.**
- If $R_f < R$, the circuit can act as an inverting attenuator

19

Tutorial 1, Question 4.

$$A_v = -\left(\frac{R_f}{R}\right)$$
$$A_v = -\left(\frac{100}{5}\right)$$
$$A_v = -20$$
$$V_o = A_v V_i$$
$$V_o = -20(20 + 5 \sin \omega t)$$
$$V_o = -(400 + 100 \sin \omega t) \text{ mV}$$

$I_i = (4 + \sin \omega t) \mu A$
 $I_f = -(4 + \sin \omega t) \mu A$

23