

A Design Example

- Requirement: To build a JFET preamplifier for a musical instrument.
- Given : Drain Resistance = $2.2\text{ k}\Omega$
- The parameters you need to design are:
 - DC Bias (V_{cc})
 - Quiescent channel current
 - Quiescent Gate voltage
 - Cut off frequency of the preamplifier
 - Coupling capacitors

74

Design Choices

- 1) JFET selection : Use J113 general purpose FET
 - V_{DS} (maximum) = 35V
 - $V_{GS, (off)} = -2\text{ V}$
 - $I_{DSS} = 8.34\text{ mA}$
 - Max Power Dissipation = 625 mW
 - Drain to Source Resistance = $100\text{ }\Omega$
- 2) Supply Voltage Selection :
 - Choose 9v as V_{cc}
 - Most musical instrument circuits run on 9V
- 3) Gate-Source Voltage : Let us choose $V_{GS,Q} = 0.8\text{ V}$

75

J113 JFET

Electrical Characteristics

Values are at T_A = 25°C unless otherwise noted.


Symbol	Parameter	Conditions	Min.	Max.	Unit
Off Characteristics					
V _{(BR)GSS}	Gate-Source Breakdown Voltage	I _G = -1.0 μA, V _{DS} = 0	-35		V
I _{GSS}	Gate Reverse Current	V _{GS} = -15 V, V _{DS} = 0		-1.0	nA
V _{GS(off)}	Gate-Source Cut-Off Voltage	V _{DS} = 15 V, I _D = 1.0 μA	111	-3.0	V
			112	-1.0	
			113	-0.5	
I _{D(off)}	Drain Cutoff Leakage Current	V _{DS} = 5.0 V, V _{GS} = -10 V		1.0	nA
On Characteristics					
I _{DSS}	Zero-Gate Voltage Drain Current ⁽⁵⁾	V _{DS} = 15 V, V _{GS} = 0	111	20	mA
			112	5.0	
			113	2.0	
r _{DS(on)}	Drain-Source On Resistance	V _{DS} ≤ 0.1 V, V _{GS} = 0	111	30	Ω
			112	50	
			113	100	
Small Signal Characteristics					
C _{dg(on)} C _{sg(on)}	Drain-Gate &Source-Gate On Capacitance	V _{DS} = 0, V _{GS} = 0, f = 1.0 MHz		28	pF
C _{dg(off)}	Drain-Gate Off Capacitance	V _{DS} = 0, V _{GS} = -10 V, f = 1.0 MHz		5.0	pF
C _{sg(off)}	Source-Gate Off Capacitance	V _{DS} = 0, V _{GS} = -10 V, f = 1.0 MHz		5.0	pF

Note:

5. Pulse test: pulse width ≤ 300 μs, duty cycle ≤ 2%.

76

J113 JFET

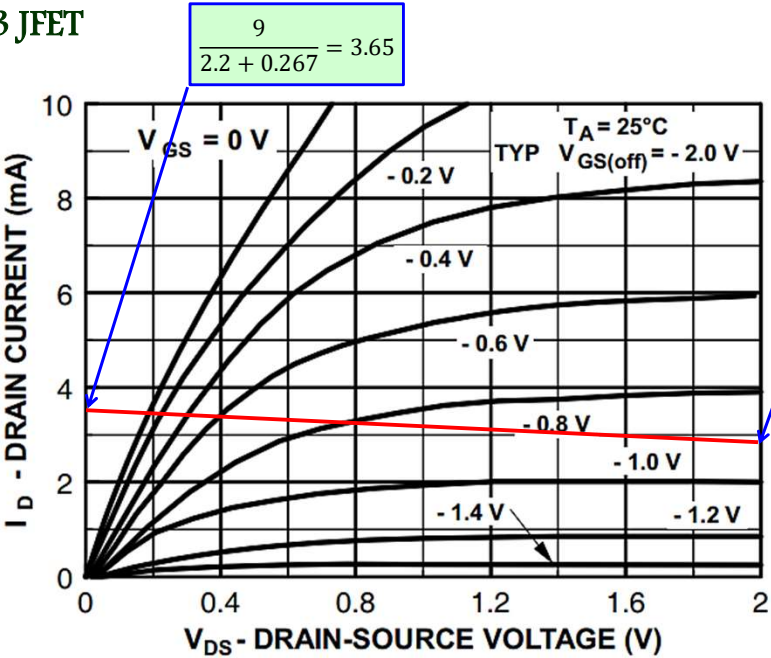

77

Design (cont.) : Operating Point

Chosen $V_{GS} = -0.8\text{ V}$

$$R_S = \left| \frac{0.8\text{ V}}{3\text{ mA}} \right| = 267\text{ k}\Omega$$


$$I_D = 8.34 \left(1 - \frac{0.8}{2} \right)^2 = 3\text{ mA}$$

$$V_S = I_D R_S = 3 \times 267 = 0.8\text{ V}$$

$$V_L = I_D R_D = 3 \times 2200 = 6.6\text{ V}$$


$$V_D = 9 - 6.6 = 2.4\text{ V}$$

$$V_{DS} = 2.4 - 0.8 = 1.6\text{ V}$$

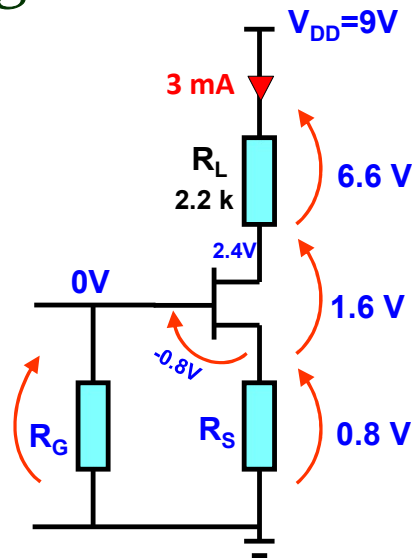

78

Design (cont.) : Operating Point

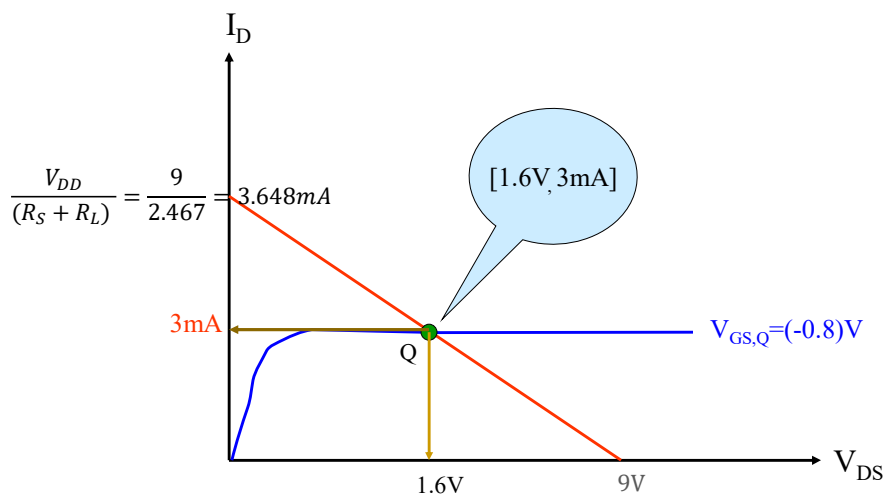


Design (Cont.) : Input Interface with Source

- Input Impedance
 - Too low : Loading on the source i.e Guitar pickup.
 - Too high : Circuit will be noisier due to the thermal noise of the resistor
 - 100 k Ω to 1 M Ω is OK.
 - Let us use a value of 100 k Ω for R_G

$$\tau = R_G \cdot C_C$$

$$f_c = \frac{1}{2 \cdot \pi \cdot \tau}$$
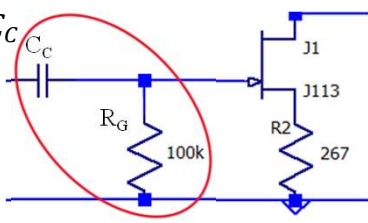
$$f_c = \frac{1}{2 \cdot \pi \cdot R_G \cdot C_C}$$


80

Design (Cont.) : Input Interface with Source

Assuming standard guitar;

We can choose the lower cutoff frequency as 82.4Hz

$$f_c = \frac{1}{2 \cdot \pi \cdot R_G \cdot C_C} = 82.4\text{Hz (assuming standard guitar)}$$

$$C_C = \frac{1}{2 \cdot \pi \cdot R_G \cdot f_c} = \frac{1}{2 \cdot \pi \cdot (100,000) \cdot (82.4)} = 19.1 \text{ nF}$$

$$C_C > 19.1 \text{ nF}$$


Any higher value is OK. Therefore, we can choose a typical μF value.

81

Design (Cont.) : Input Interface with Source

When $C_C = 19.1 \text{ nF}$; $f_c = \frac{1}{2 \cdot \pi \cdot R_G \cdot C_C} = 82.4 \text{ Hz}$

Use the command; `.ac dec 10 0.1 2000`

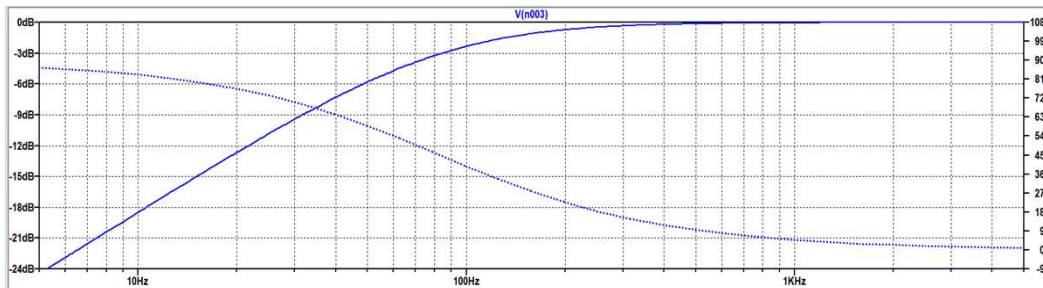


However, $X_c = \frac{1}{2 \cdot \pi \cdot f \cdot C_C} = \frac{1}{2 \cdot \pi \cdot (82.4) \cdot (19.1)} \approx 100 \text{ k}\Omega$! (*too much*)

For C_C any higher value is OK. Therefore, we can choose a typical μF value.

82

Design (Cont.) : Input Interface with Source

Let us use $C_C = 2.2 \mu\text{F}$

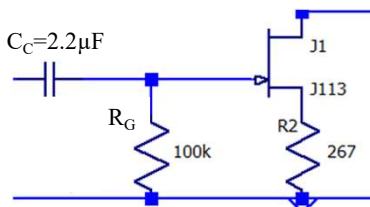


$$X_c = \frac{1}{2 \cdot \pi \cdot f \cdot C_C}$$

$$X_c = \frac{1}{2 \cdot \pi \cdot (82.4) \cdot (2.2)} \text{ M}\Omega$$

$$X_c = 878 \Omega$$

$$f_c = \frac{1}{2 \cdot \pi \cdot R_G \cdot C_C}$$
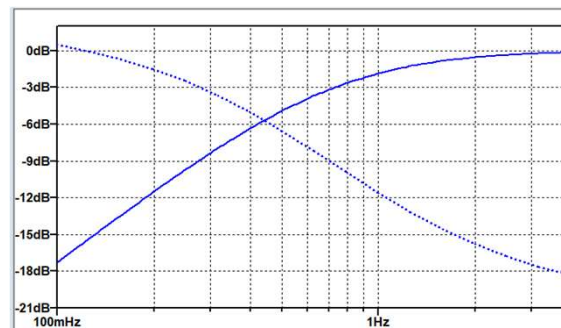
$$f_c = \frac{1}{2 \cdot \pi \cdot (100) \cdot (2.2)} \text{ kHz} = 0.7 \text{ Hz}$$



82

Design (Cont.) : Output Interface with Load


- Input impedance of the next stage?
 - Let us assume a standard and quite low value, such as 10kΩ.
 - Always make sure this is larger than R_D .

$$C_c = \frac{1}{2 \cdot \pi \cdot R_L \cdot f_c} = \frac{1}{2 \cdot \pi \cdot (10,000) \cdot (82.4)} = 194 \text{ nF}$$

$$C > 194 \text{ nF}$$

- Any higher value is OK. Therefore, we can choose a typical μF value.
- E.g. 1 μF coupling capacitor can give us a lower cut off frequency of 7 Hz.


84

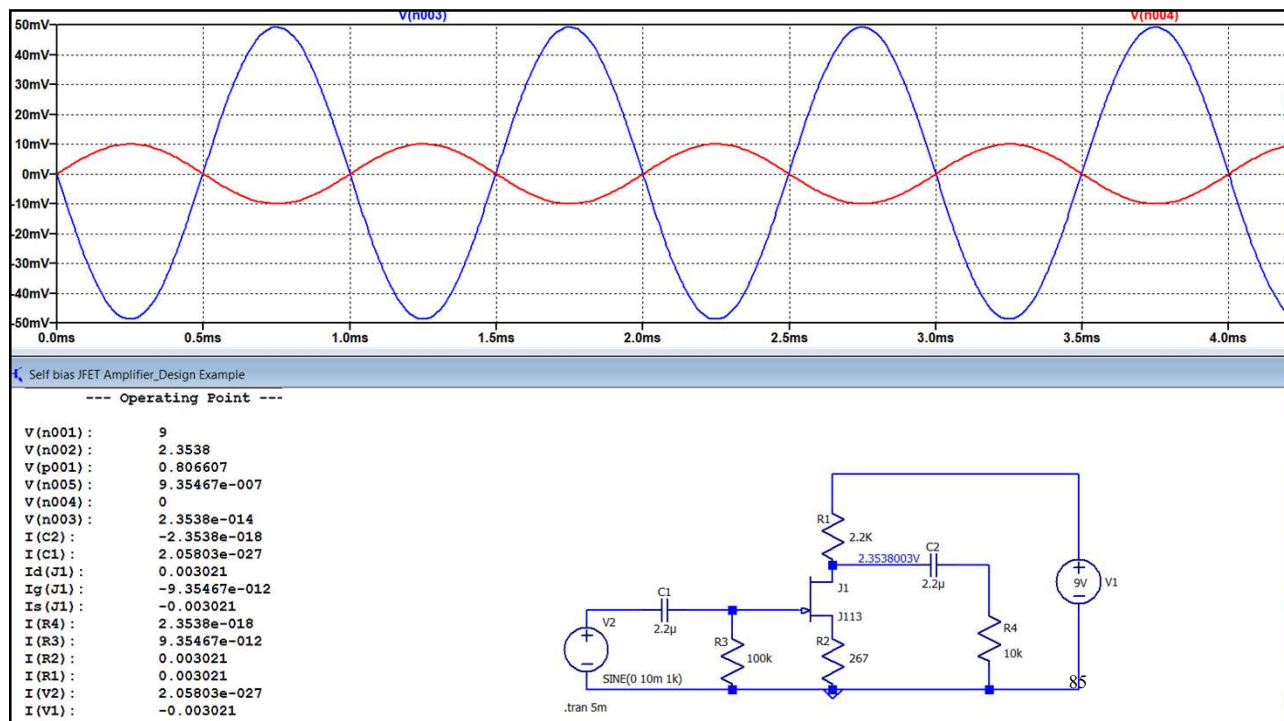


$$A_v = -\frac{V_{o,(pk-pk)}}{V_{i,(pk-pk)}} = -\frac{100mV}{20mV} = -5$$

$$A_i = \frac{I_{o,(pk-pk)}}{I_{i,(pk-pk)}} = -\frac{10\mu A}{200nA} = 50$$

$$G = \frac{P_o}{P_i} = |A_v| \cdot |A_i| = 5 \times 50 = 250$$

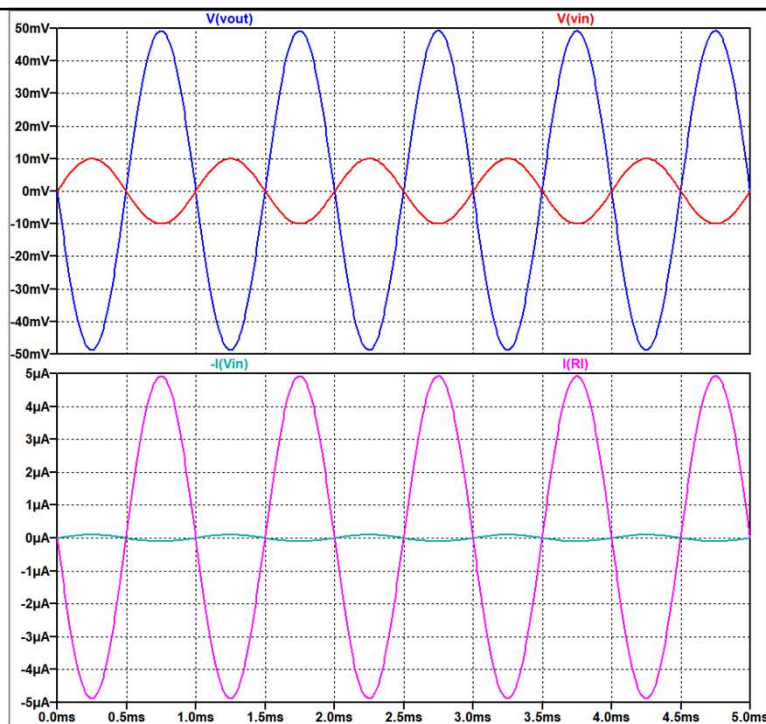


With a bypass capacitor...

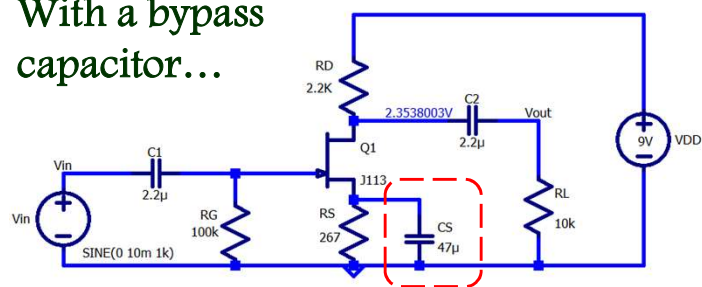


$$A_v = -\frac{V_{o,(pk-pk)}}{V_{i,(pk-pk)}} = -\frac{364mV}{20mV} = -18.2$$

$$A_i = \frac{I_{o,(pk-pk)}}{I_{i,(pk-pk)}} = -\frac{36.4\mu A}{199.7nA} = 182.2$$

$$G = \frac{P_o}{P_i} = |A_v| \cdot |A_i| = 18.2 \times 182.2 = 3316 = 35.2dB$$

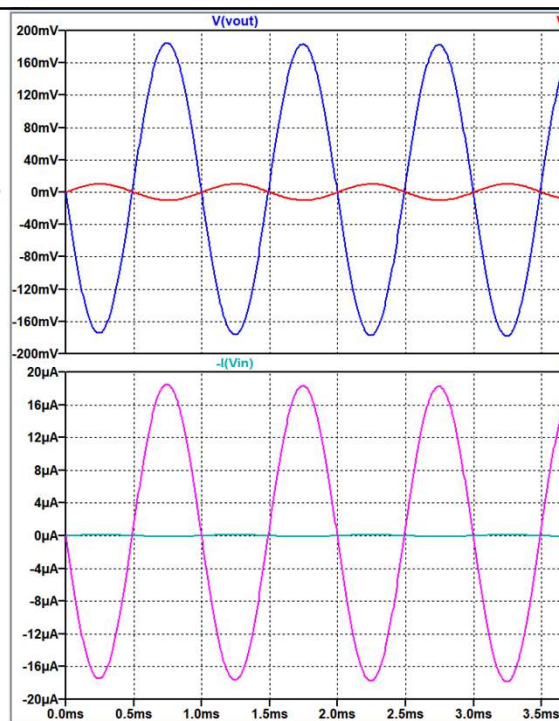


Graphical Illustration

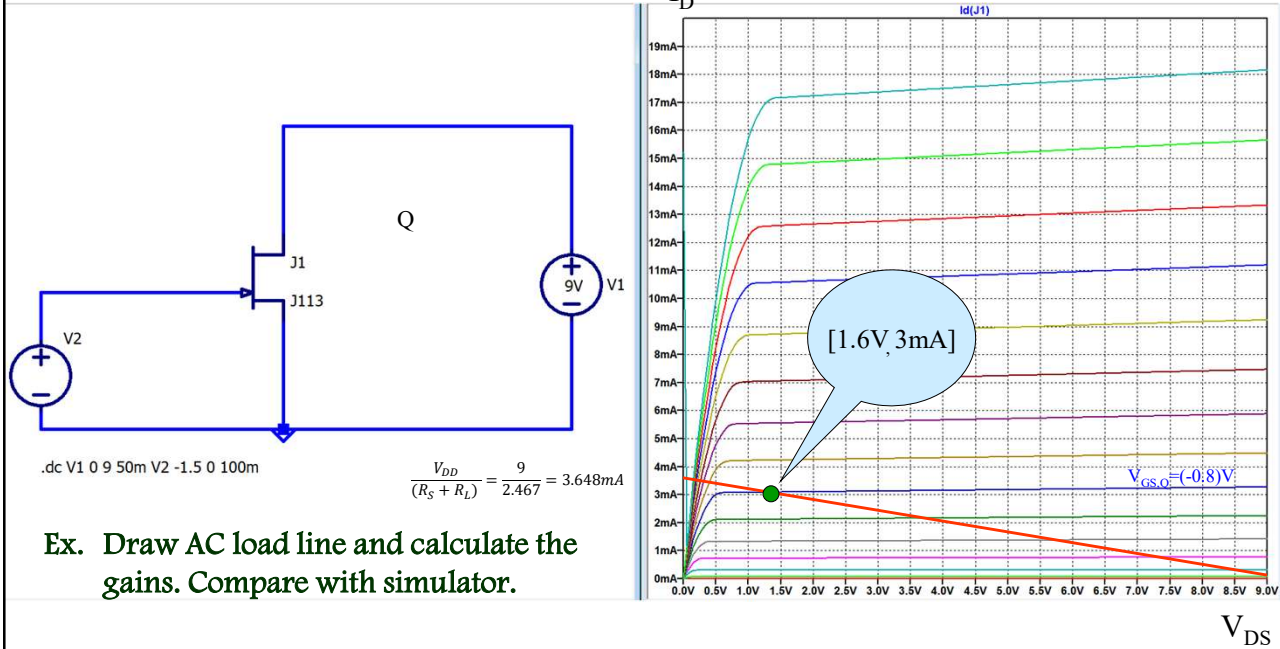


Ex. Draw AC load line and calculate the gains. Compare with simulator.

Potential Divider Biasing Method

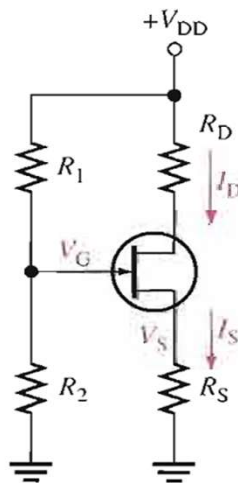


Potential Divider Bias

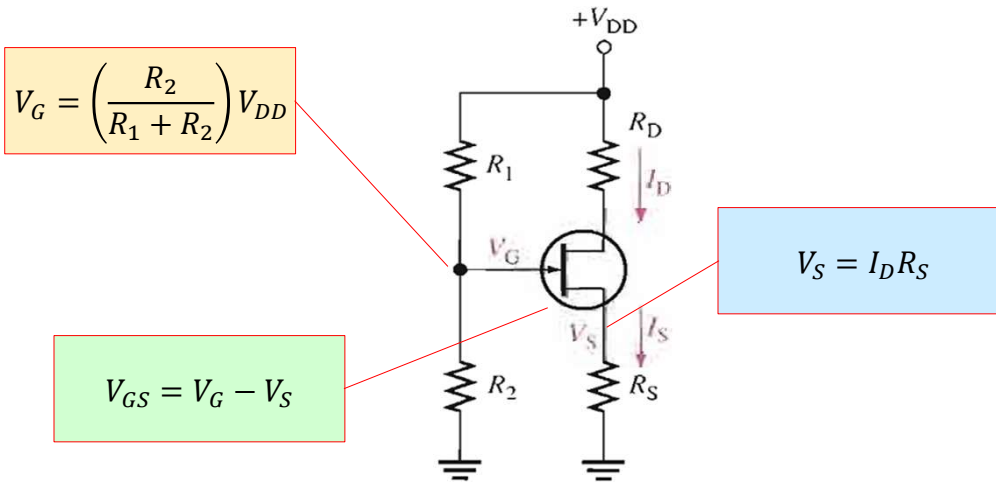

90


Potential Divider Bias Example
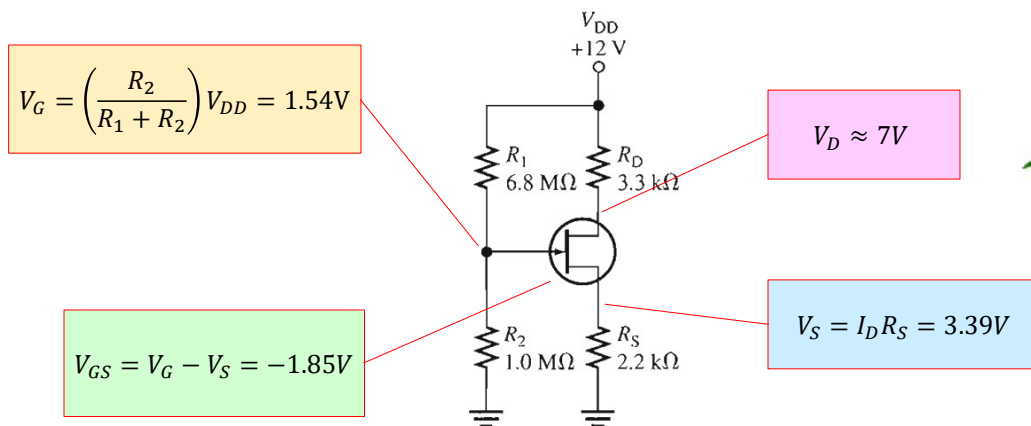
$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{12 \text{ V} - 7 \text{ V}}{3.3 \text{ k}\Omega} = \frac{5 \text{ V}}{3.3 \text{ k}\Omega} = 1.52 \text{ mA}$$




91

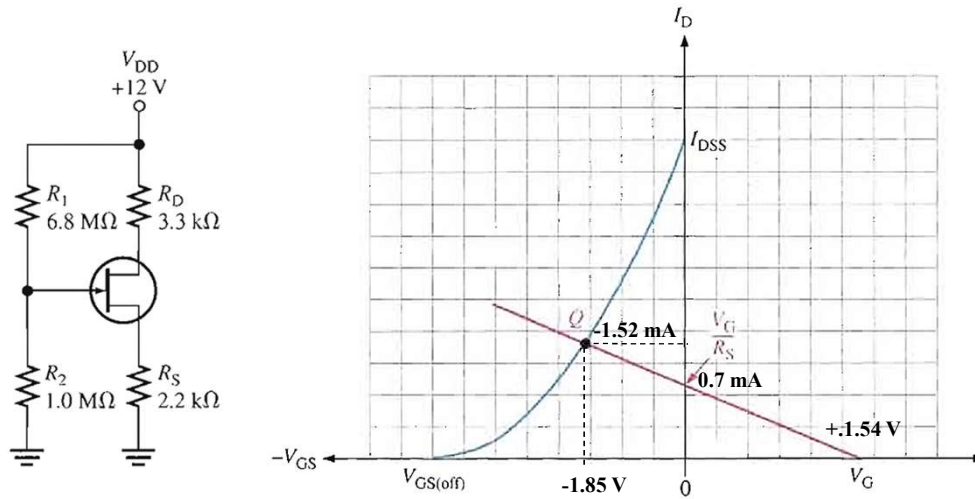
DC Load Line... on Static Mutual Characteristics




92

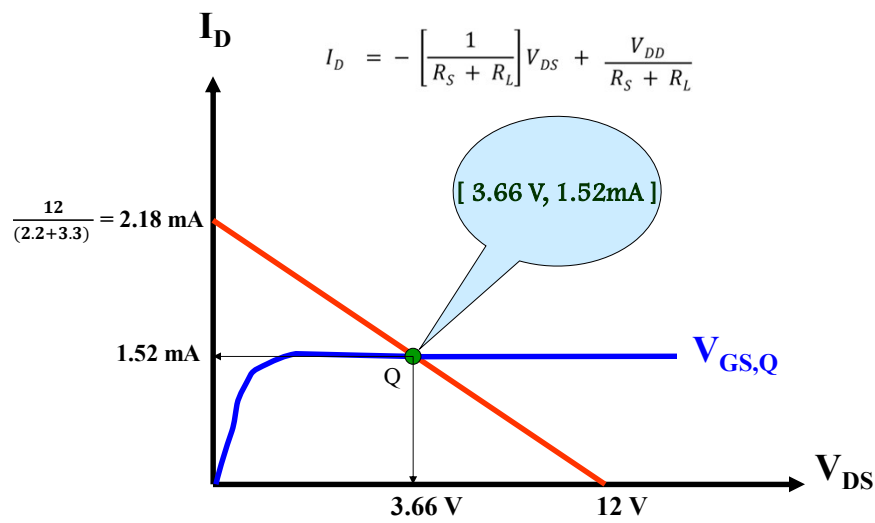DC Load Line... on Static Output Characteristics



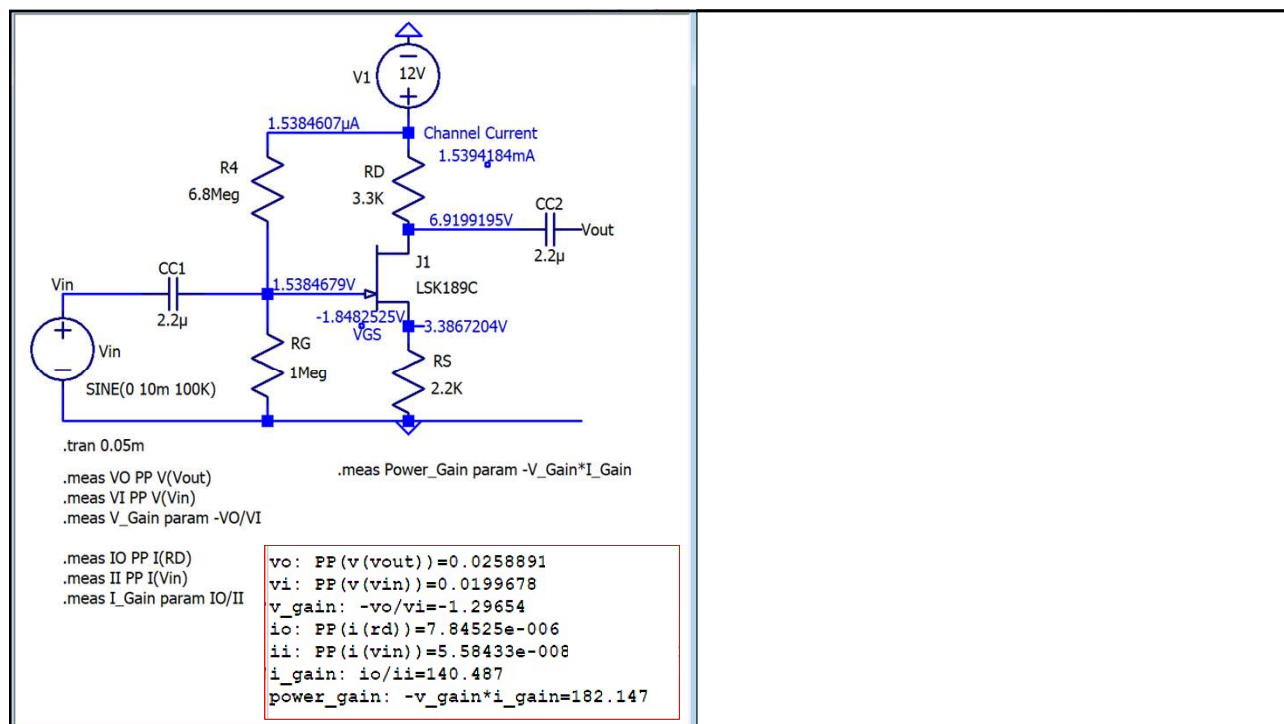


Use of Bypass Capacitors

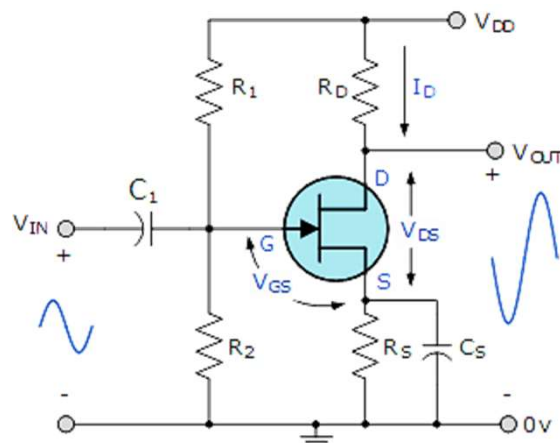

95

AC Equivalent Circuit

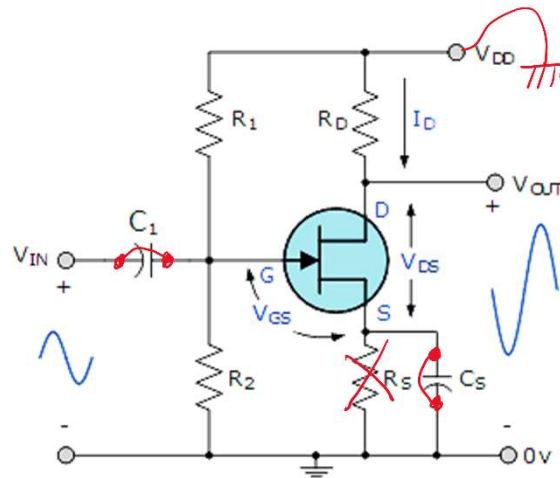


$$v_{ds} + i_d R_D = 0$$

$$i_d = \left(\frac{-1}{R_D} \right) v_{ds}$$

Gradient

96

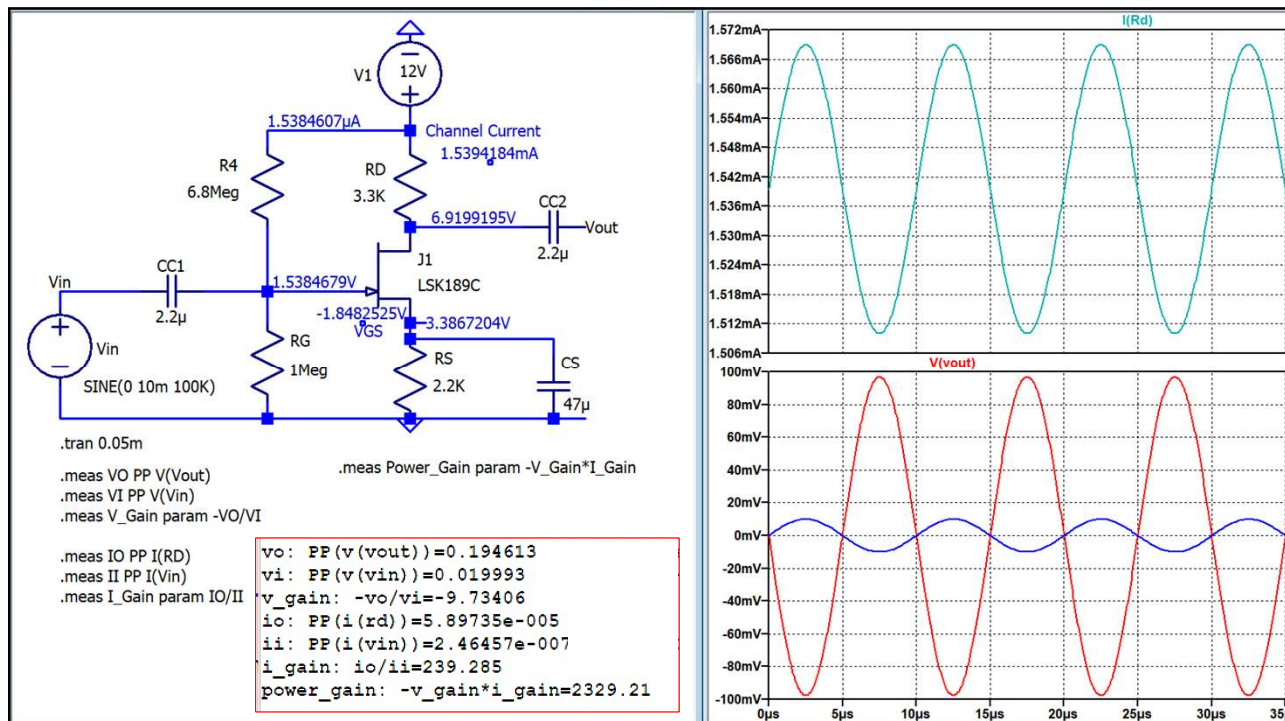

AC Load Line and Gain Calculations....

- Coupling and Bypass capacitors can be considered as S/C connections for ac signals
- Draw an ac equivalent circuit
- Using KVL for ac signals find the new gradient of the load line
- Draw ac load line with that gradient to go through the Q point.
- Then use ac load line for gain calculations


98

Moving on to MOSFET....


Watch: 1. https://youtu.be/Bine_PbyFSQ
2. <https://youtu.be/rkbjHNEKcRw>

Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET)

MOSFET

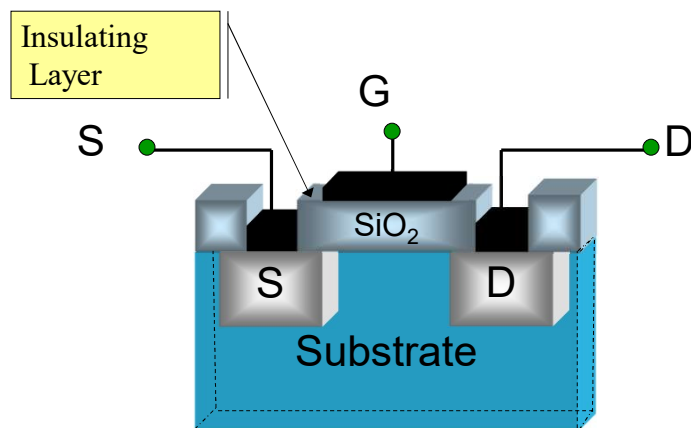


Induced N-Channel

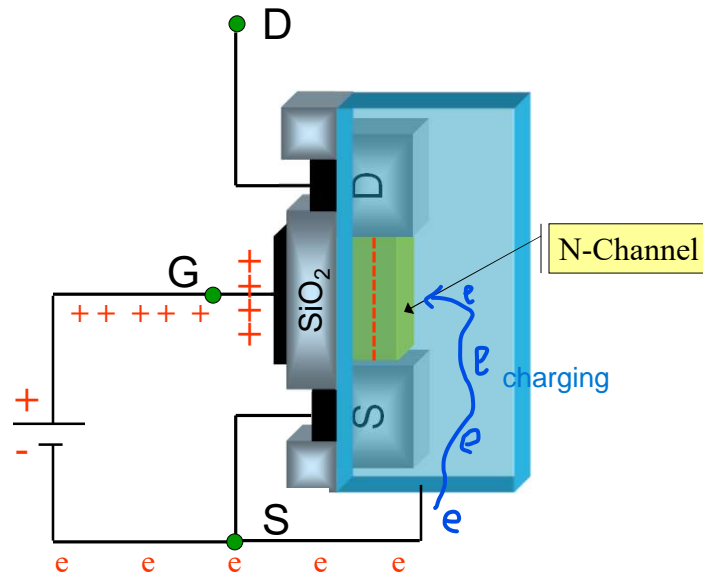


102

Idea of EMOSFET Symbol

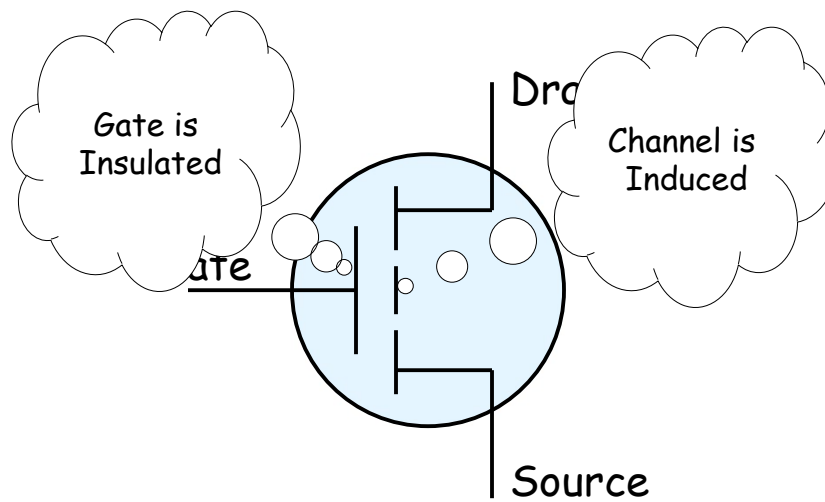


103

Normally-OFF Type N~Channel

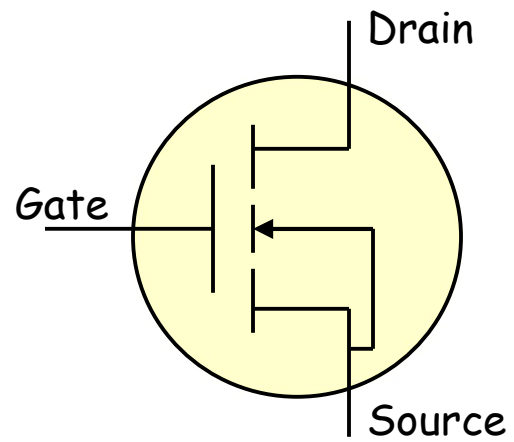

104

Normally-OFF Type P~Channel

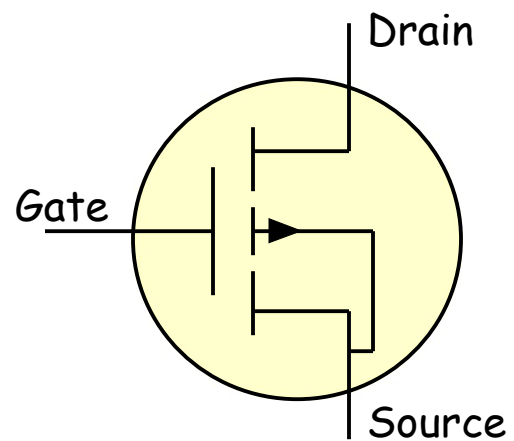

105

Handle with Care

The insulating layer is extremely thin and can be easily damaged by static charges.


The workplace must be grounded safely.

Touch some earthed point just before handling static sensitive devices


Some devices have Zener diodes built in, between gate and source, for protection.

Soldering iron tips must be earthed. You must be grounded via a wriststraps

106

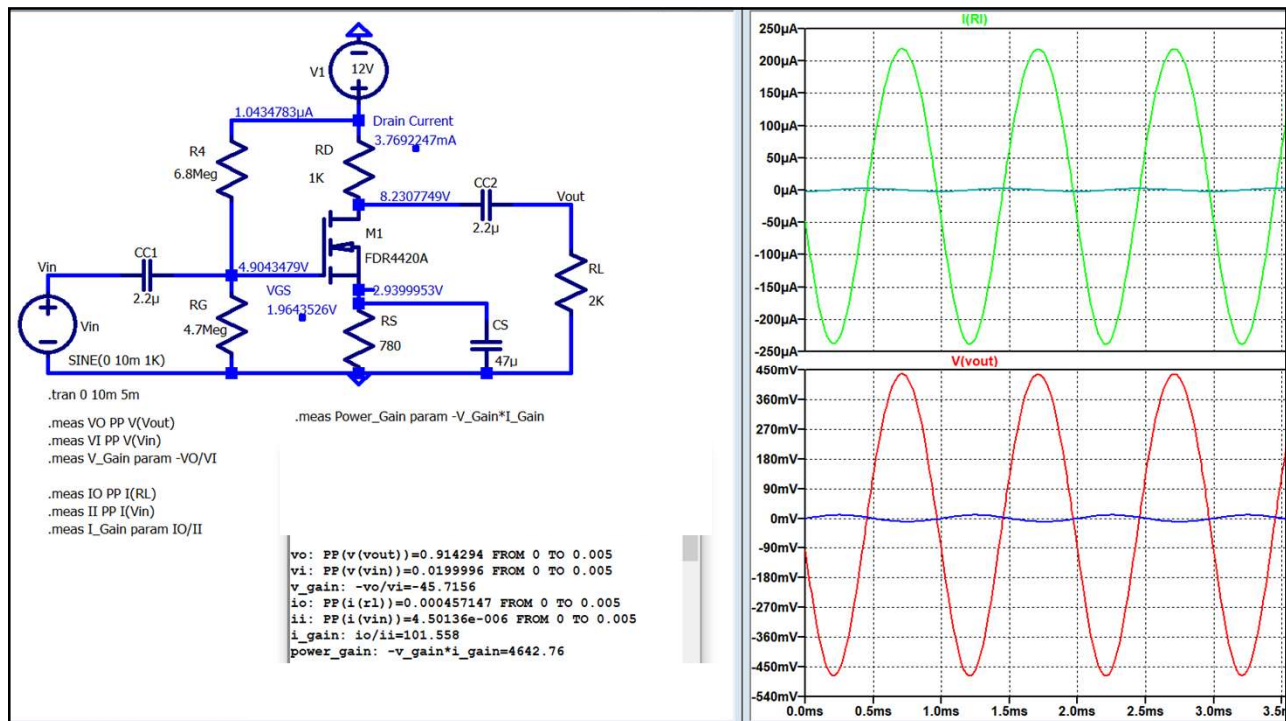


DMOSFET

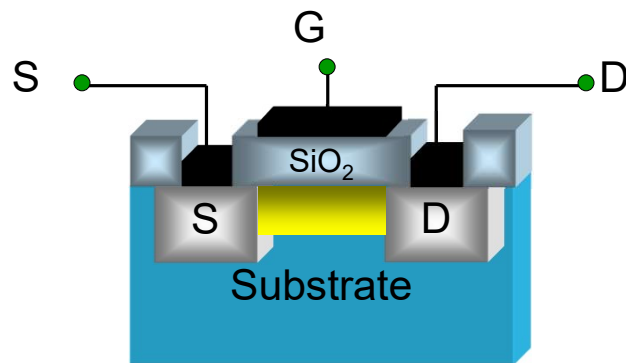


108

Idea of DMOSFET Symbol

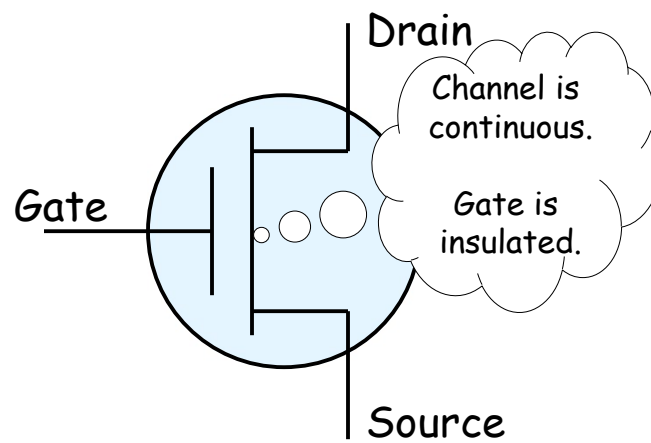


109

Normally-On Type N~Channel

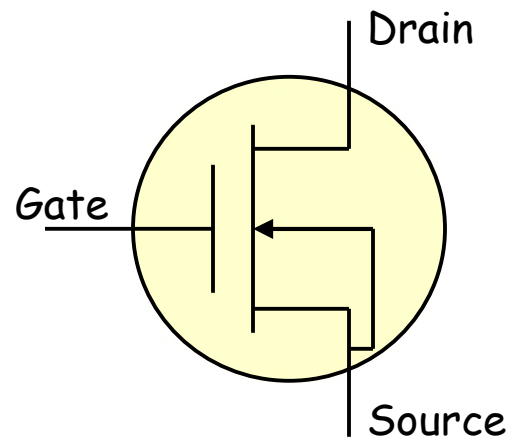


110

Normally-On Type P~Channel

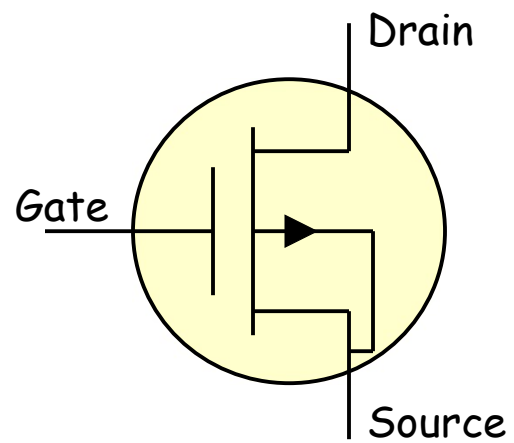


111

FET Classification

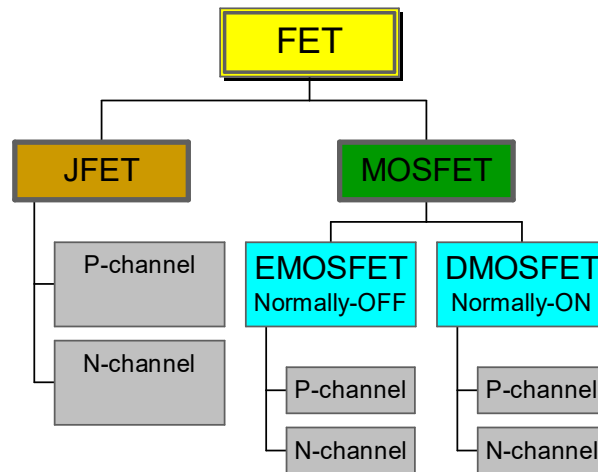


112

With Potential Divider Bias...

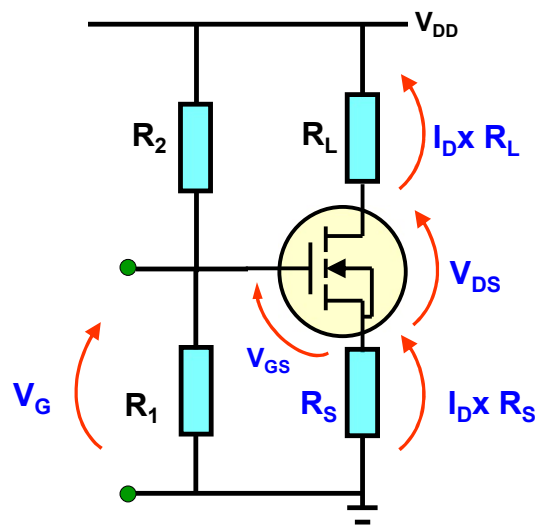

113

Dual Gate FETS

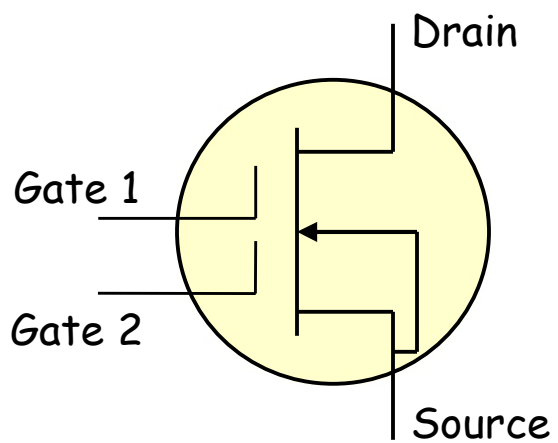


114

Some RF Applications

RF Stage of a Radio

Common Gate Amplifier


Widely used in VHF and UHF receivers

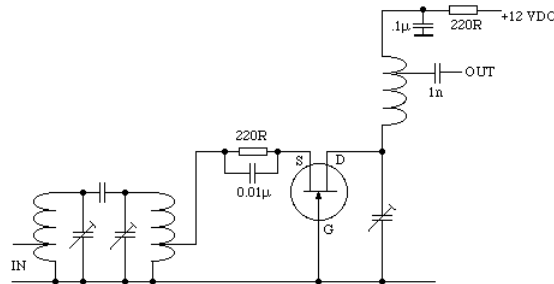

The grounded gate FET amplifier has 10 to 15dB of gain, and a low noise figure

116

FET Mixers in a Radio

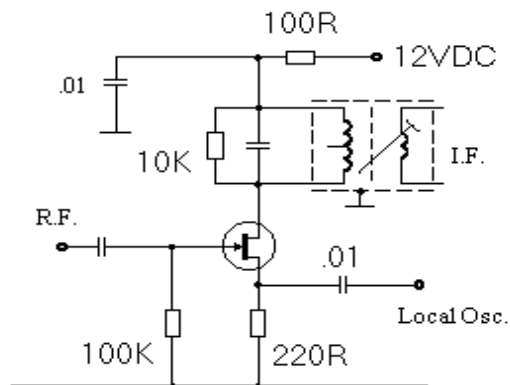

A Mixer Down-converts RF to IF

117