

EN1014 Electronic Engineering

Sequential Logic Circuits

Chamira U. S. Edussooriya

B.Sc.Eng. (Moratuwa), M.A.Sc. (UVic), Ph.D. (UVic)

Department of Electronic and Telecommunication Engineering
University of Moratuwa

Some of the tables and figures included in this presentation have been extracted from
Digital Design: With an Introduction to the Verilog HDL (M. M. Mano and M. D. Ciletti, Prentice Hall, 2012)

Introduction

- In contrast to combinational logic circuits, the outputs of a **sequential logic circuits** depend on the **past values of the inputs** in addition to the present values of the inputs.

Introduction

- In contrast to combinational logic circuits, the outputs of a **sequential logic circuits** depend on the **past values of the inputs** in addition to the present values of the inputs.
- A sequential logic circuit consists of a **combinational circuit** and **storage (memory) elements**.

 


FIGURE 5.1
Block diagram of sequential circuit

Introduction

- In contrast to combinational logic circuits, the outputs of a **sequential logic circuits** depend on the **past values of the inputs** in addition to the present values of the inputs.
- A sequential logic circuit consists of a **combinational circuit** and **storage (memory) elements**.

 


FIGURE 5.1
Block diagram of sequential circuit

- The binary information stored in the storage elements at any given time defines the **state** of the sequential logic circuit at that time.

Introduction

- In contrast to combinational logic circuits, the outputs of a **sequential logic circuits** depend on the **past values of the inputs** in addition to the present values of the inputs.
- A sequential logic circuit consists of a **combinational circuit** and **storage (memory) elements**.

 


FIGURE 5.1
Block diagram of sequential circuit

- The binary information stored in the storage elements at any given time defines the **state** of the sequential logic circuit at that time.
- Similar to the outputs of a sequential logic circuit, the **next state** of the storage elements is a function of both inputs and the present state of the storage elements.

Introduction *cont'd*

- Sequential logic circuits can be categorized in two groups, **synchronous** and **asynchronous**, based on the timing of their signals.


Introduction *cont'd*

- Sequential logic circuits can be categorized in two groups, **synchronous** and **asynchronous**, based on the timing of their signals.
- The behaviour of a synchronous sequential logic circuit can be specified from the knowledge of its signals at **discrete instants** of time.

Introduction *cont'd*

- Sequential logic circuits can be categorized in two groups, **synchronous** and **asynchronous**, based on the timing of their signals.
- The behaviour of a synchronous sequential logic circuit can be specified from the knowledge of its signals at **discrete instants** of time.
- The behaviour of an asynchronous sequential logic circuit depends on the input signals at **any instant** of time and the order in which the inputs change.

Synchronous Sequential Circuits

 

(a) Block diagram




(b) Timing diagram of clock pulses

FIGURE 5.2
Synchronous clocked sequential circuit

- In a synchronous sequential circuit, the states of the storage elements are affected at only **discrete instants** of time.

Synchronous Sequential Circuits

 

(a) Block diagram



(b) Timing diagram of clock pulses

FIGURE 5.2
Synchronous clocked sequential circuit

- In a synchronous sequential circuit, the states of the storage elements are affected at only **discrete instants** of time.
- Synchronization is achieved by a timing device called a **clock generator**, which provides a **clock signal** having the form of a periodic train of **clock pulses**.

Synchronous Sequential Circuits

 


FIGURE 5.2
Synchronous clocked sequential circuit

- In a synchronous sequential circuit, the states of the storage elements are affected at only **discrete instants** of time.
- Synchronization is achieved by a timing device called a **clock generator**, which provides a **clock signal** having the form of a periodic train of **clock pulses**.
- The clock pulses determine **when** computational activity will occur, and the inputs and the present state determine **what** changes will take place affecting the storage elements and the outputs.

Storage Elements: Latches

- The basic storage elements employed in sequential logic circuits are **latches** and **flip-flops**.

Storage Elements: Latches

- The basic storage elements employed in sequential logic circuits are **latches** and **flip-flops**.
- Latches are **level-sensitive** devices where as flip-flops are **edge-sensitive** devices.

Storage Elements: Latches

- The basic storage elements employed in sequential logic circuits are **latches** and **flip-flops**.
- Latches are **level-sensitive** devices where as flip-flops are **edge-sensitive** devices.
- Flip-flops are constructed using latches.

Storage Elements: Latches

- The basic storage elements employed in sequential logic circuits are **latches** and **flip-flops**.
- Latches are **level-sensitive** devices where as flip-flops are **edge-sensitive** devices.
- Flip-flops are constructed using latches.
- We first consider the basic **SR latch**.

Storage Elements: Latches

- The basic storage elements employed in sequential logic circuits are **latches** and **flip-flops**.
- Latches are **level-sensitive** devices where as flip-flops are **edge-sensitive** devices.
- **Flip-flops are constructed using latches.**
- We first consider the basic **SR latch**.
- An **SR latch with an enable input**.

 


FIGURE 5.5
SR latch with control input

| En | S | R | Next state of Q |
|----|---|---|-----------------------|
| 0 | X | X | No change |
| 1 | 0 | 0 | No change |
| 1 | 0 | 1 | $Q = 0$; reset state |
| 1 | 1 | 0 | $Q = 1$; set state |
| 1 | 1 | 1 | Indeterminate |


(b) Function table

Storage Elements: Latches *cont'd*

- The undesirable condition that may occur with the *SR* latch can be eliminated by adding a NOT gate.

Storage Elements: Latches *cont'd*

 - The undesirable condition that may occur with the *SR* latch can be eliminated by adding a NOT gate.
- This modified *SR* latch is called the ***D* latch**.




| <i>En</i> | <i>D</i> | Next state of <i>Q</i> |
|-----------|----------|-----------------------------|
| 0 | X | No change |
| 1 | 0 | $\bar{Q} = 0$; reset state |
| 1 | 1 | $\bar{Q} = 1$; set state |

(b) Function table

FIGURE 5.6
D latch

Storage Elements: Latches *cont'd*

 - The undesirable condition that may occur with the *SR* latch can be eliminated by adding a NOT gate.
- This modified *SR* latch is called the ***D* latch**.



| En | D | Next state of Q |
|----|---|-----------------------|
| 0 | X | No change |
| 1 | 0 | $Q = 0$; reset state |
| 1 | 1 | $Q = 1$; set state |


(b) Function table

FIGURE 5.6
***D* latch**

- The binary information present at the **data input (input *D*)** of the *D* latch is transferred to the *Q* output when the **enable** input is asserted.

Storage Elements: Latches *cont'd*

 - The undesirable condition that may occur with the *SR* latch can be eliminated by adding a NOT gate.
- This modified *SR* latch is called the ***D* latch**.



| En | D | Next state of Q |
|----|---|-----------------------|
| 0 | X | No change |
| 1 | 0 | $Q = 0$; reset state |
| 1 | 1 | $Q = 1$; set state |

(b) Function table

FIGURE 5.6
***D* latch**

- The binary information present at the **data input (input *D*)** of the ***D* latch** is transferred to the ***Q* output** when the **enable input** is asserted.
- In general, the **enable input** can be either **active-high** or **active-low**.

Storage Elements: Flip-Flops

- The state of a flip-flop is changed (or triggered) only during a **signal transition**.

Storage Elements: Flip-Flops

- The state of a flip-flop is changed (or triggered) only during a **signal transition**.
- A *D* flip-flop can be constructed by employing two latches in a special configuration, called **master-slave** configuration.

 


FIGURE 5.9
Master-slave *D* flip-flop

Storage Elements: Flip-Flops

- The state of a flip-flop is changed (or triggered) only during a **signal transition**.
- A *D* flip-flop can be constructed by employing two latches in a special configuration, called **master-slave** configuration.

 


FIGURE 5.9
Master-slave *D* flip-flop

- The value at the output of the flip-flop is the value that was stored in the master stage immediately before the negative edge occurred.

Storage Elements: Flip-Flops *cont'd*

- Another way of constructing a D flip-flop is by using three SR latches.

 


FIGURE 5.10
D-type positive-edge-triggered flip-flop

Storage Elements: Flip-Flops *cont'd*

- Another way of constructing a D flip-flop is by using three SR latches.

 


FIGURE 5.10
D-type positive-edge-triggered flip-flop

- Two SR latches respond to the D and the Clk inputs while the third SR latch provides the output of the flip-flop.

Storage Elements: Flip-Flops *cont'd*

- Another way of constructing a D flip-flop is by using three SR latches.

 


FIGURE 5.10
 D -type positive-edge-triggered flip-flop

- Two SR latches respond to the D and the Clk inputs while the third SR latch provides the output of the flip-flop.
- The value of D is transferred to Q during the **positive edge** of the clock.

Storage Elements: Flip-Flops *cont'd*

- Other types of flip-flops:
 - *JK* flip-flop

 


FIGURE 5.12
JK flip-flop

Storage Elements: Flip-Flops *cont'd*

- Other types of flip-flops:
 - JK flip-flop

 


FIGURE 5.12
 JK flip-flop

- T (toggle) flip-flop

 


FIGURE 5.13
 T flip-flop

Storage Elements: Flip-Flops *cont'd*

- **Asynchronous inputs** such as **preset** and **clear** can be used to force a flip-flop to a particular state independently of a clock.

Storage Elements: Flip-Flops *cont'd*

- **Asynchronous inputs** such as **preset** and **clear** can be used to force a flip-flop to a particular state independently of a clock.
- They are useful for bringing a flip-flop to a known starting state prior to the clock operation.

Storage Elements: Flip-Flops *cont'd*

- **Asynchronous inputs** such as **preset** and **clear** can be used to force a flip-flop to a particular state independently of a clock.
- They are useful for bringing a flip-flop to a known starting state prior to the clock operation.
- *D* flip-flop with an asynchronous reset (or clear).

