


BJT Characteristics


Number of Variables in a BJT

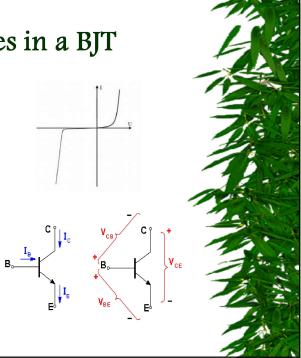- * Diode
 - One current and one voltage
- * BJT
 - Three currents and three voltages!
 - They are interdependent
 - How many characteristic graphs?



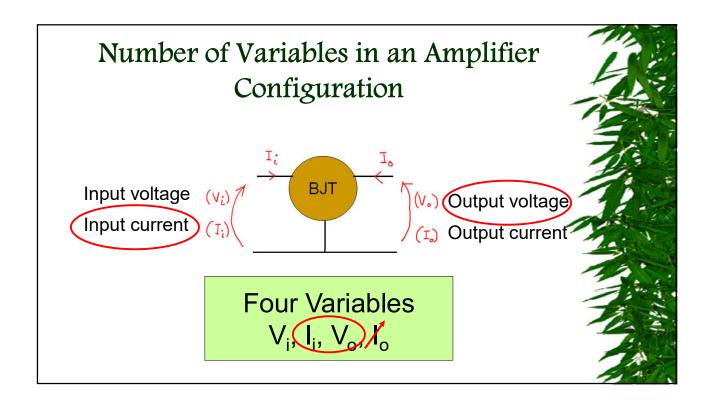

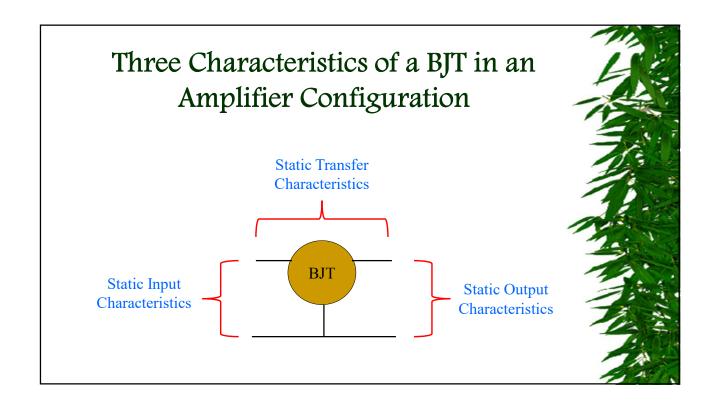

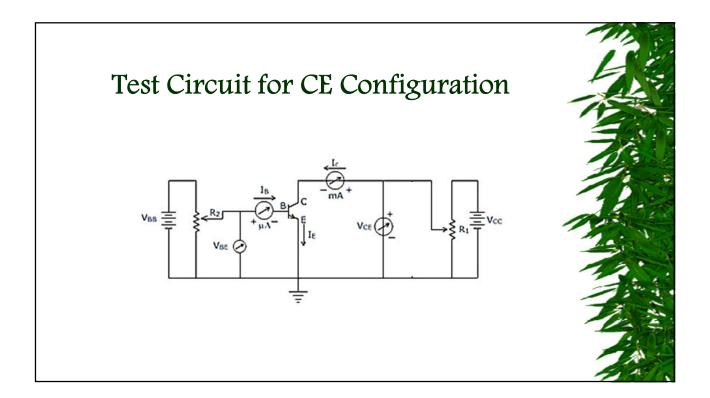

Three Characteristics of a BJT in an Amplifier Configuration


- * Static Input Characteristics
- * Static Transfer Characteristics
 - Mutual Characteristics



Static Input Characteristics

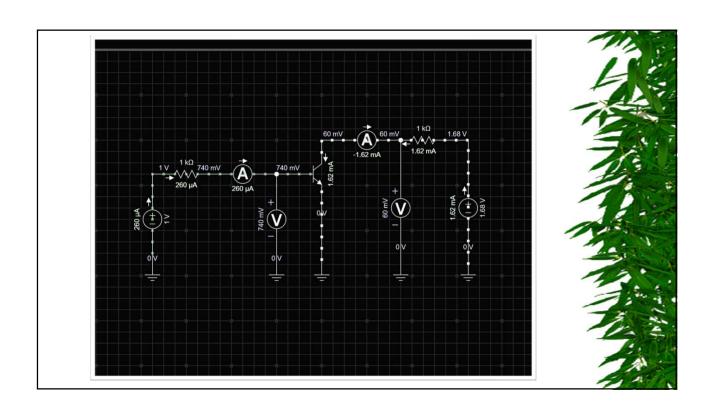
- * The plot of input current(I_i) against input voltage(V_i)
 - Keep the output voltage(V_o) constant
 - Plot one curve for each constant V_o value
 - Multiple curves in the graph





Static Input Characteristics for CE Configuration

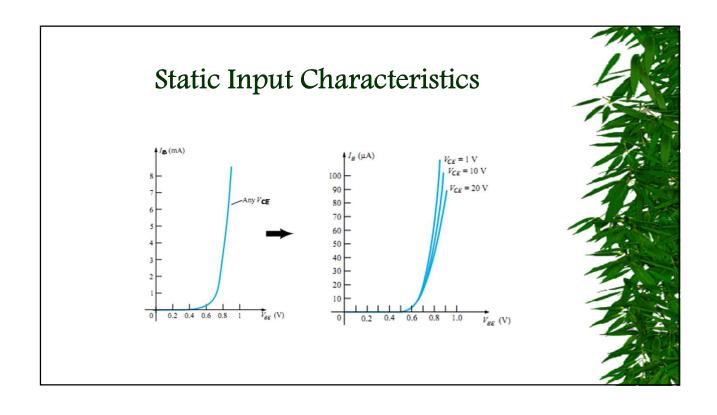- * For CE configuration it is the plot of Base current(I_B) vs Base voltage(V_{BE})
 - Collector voltage(V_{CE}) is kept constant
 - Remember the shape of diode characteristics





Static Output Characteristics


- * The plot of output current(I_o) against output voltage(V_o)
 - Keep the input current(I_i) constant
 - Multiple curves will be drawn. One each for a constant value of $(\mathbf{I_i})$

Static Output Characteristics

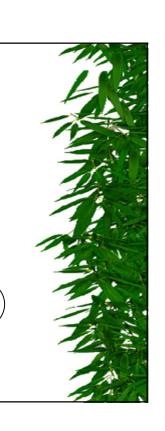- For CE configuration it is the plot of Collector current(I_C) vs Collector voltage(V_{CE})
 - Base current(I_B) is kept constant
 - One curve for each value of I_B.




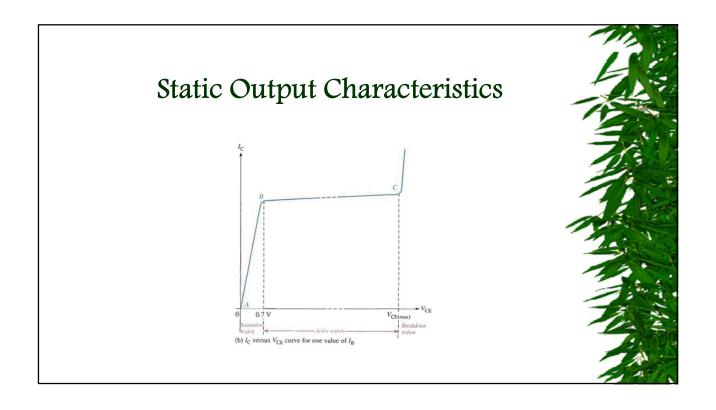


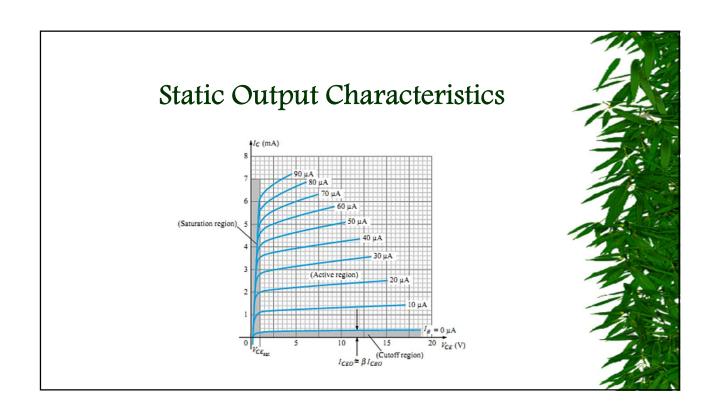



Static Transfer Characteristics

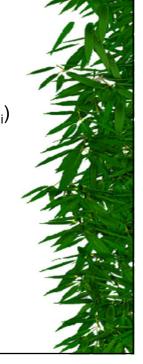
- * The plot of output current(I_o) against input current(I_i)
 - Keep the output voltage(V_o) constant
 - Multiple curves for each constant value
- For CE configuration it is the plot of Collector current(I_C) vs Base current(I_B)
 - Collector voltage(V_{CE}) is kept constant
 - Linear behaviour




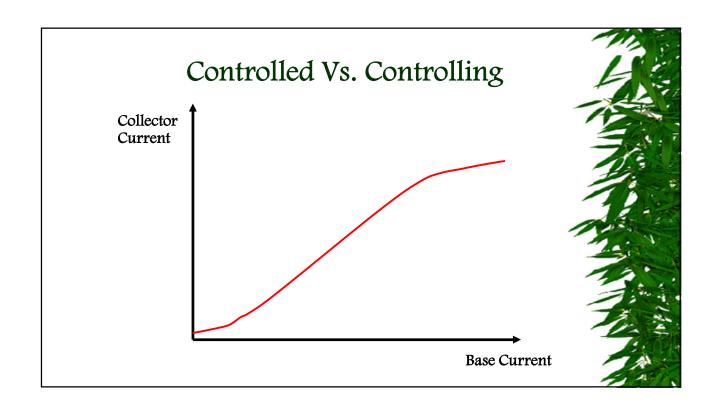


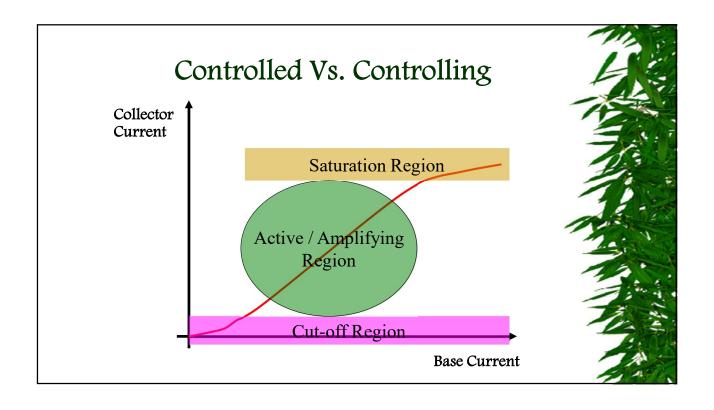

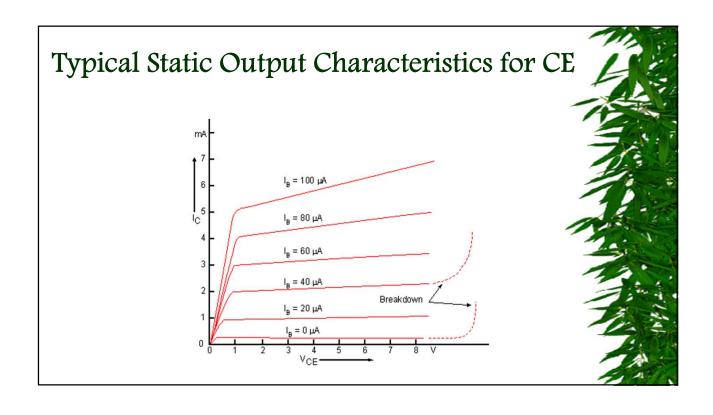


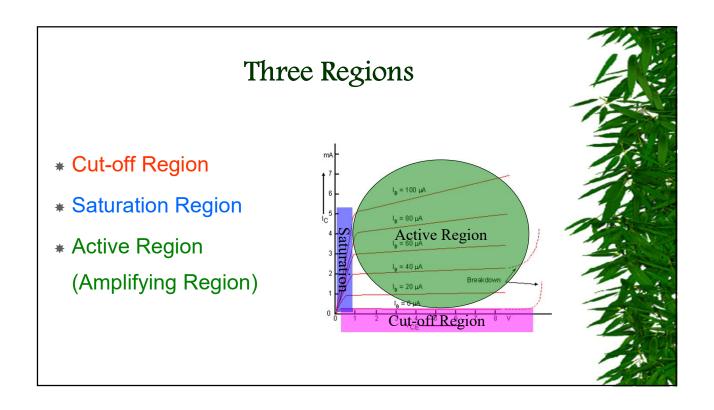


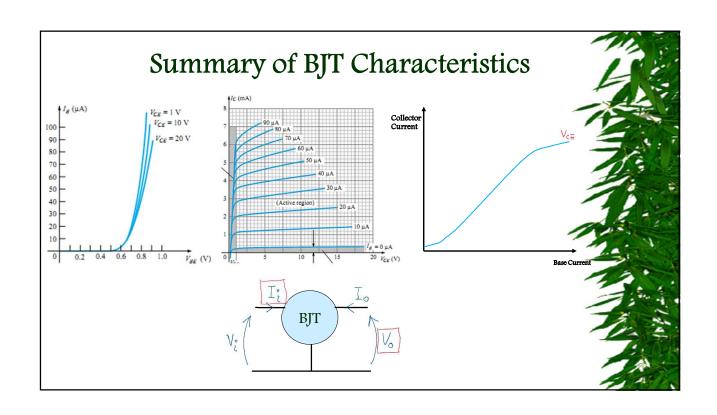

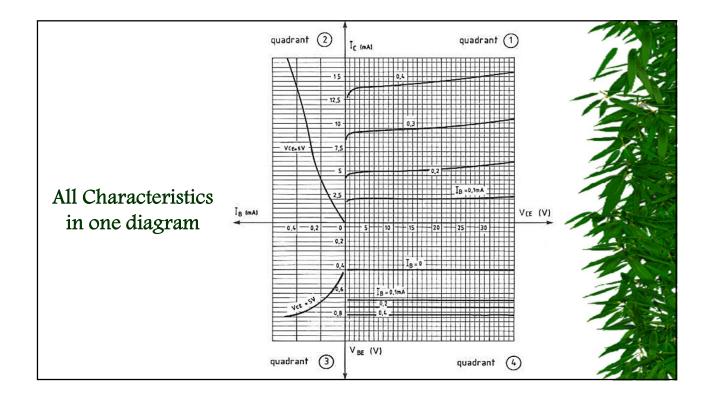


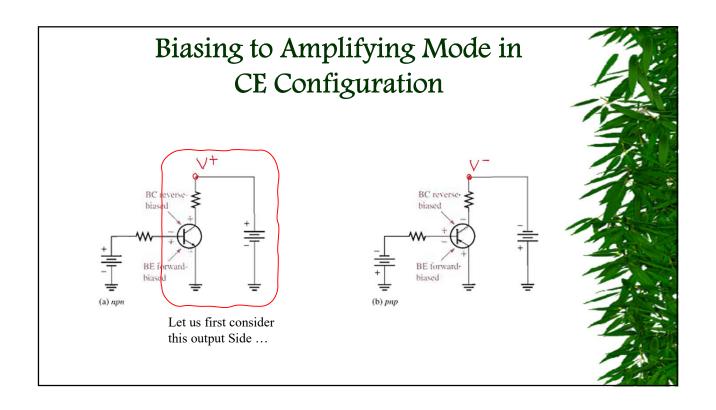BJT in
Common Emitter Amplifier
Configuration



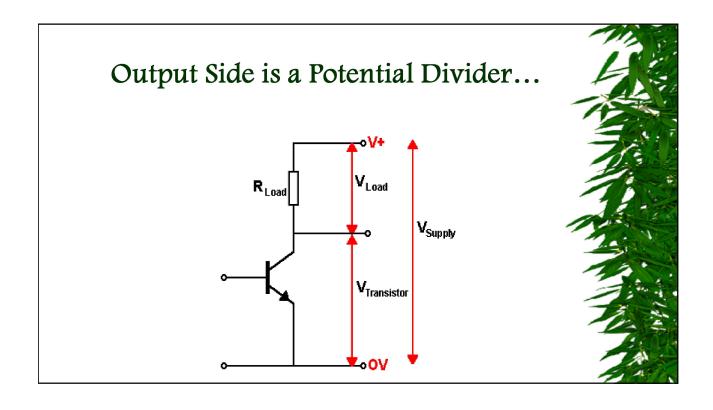

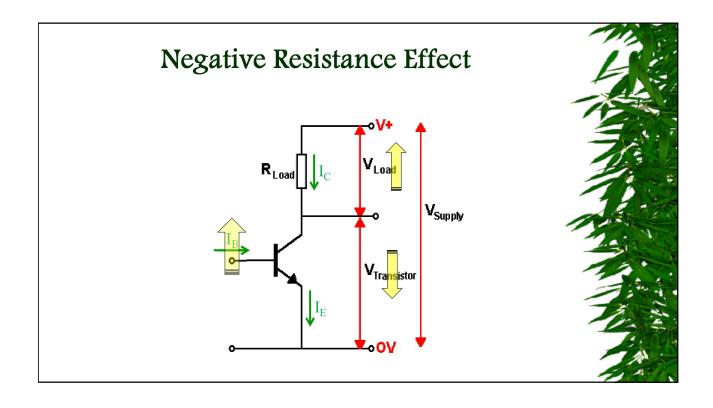Kirchoff's Voltage Law
$$V_{Load} + V_{Transistor} = V_{Suppy}$$





Activity

When collector current is increased voltage across
rises and voltage across
decreases. When the input voltage increases,
collector current, and the voltage
across the load
voltage is the C-E voltage across the transistor. It
, as a result of the increase in load voltage.


Answer

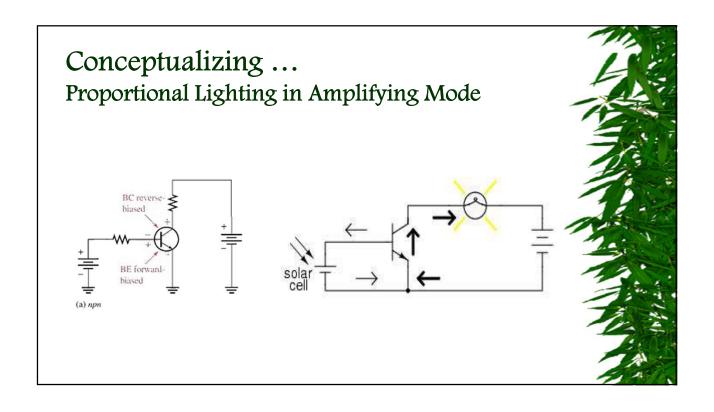When collector current is increased voltage across the LOAD rises and voltage across TRANSISTOR decreases. When the input voltage increases, collector current RISES, and the voltage across the load RISES AS A RESULT. The output voltage is the C-E voltage across the transistor. It DROPS, as a result of the increase in load voltage.



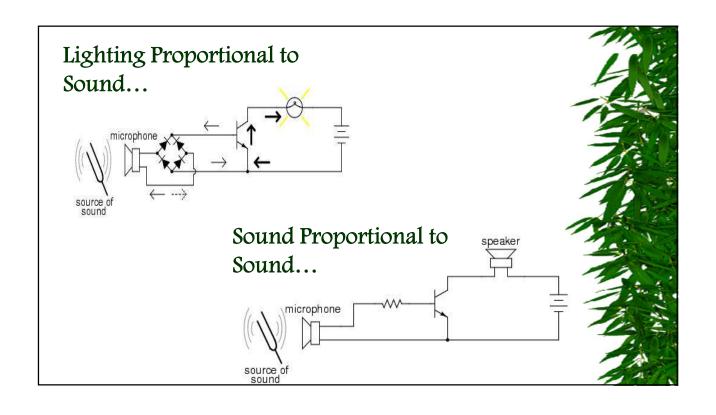



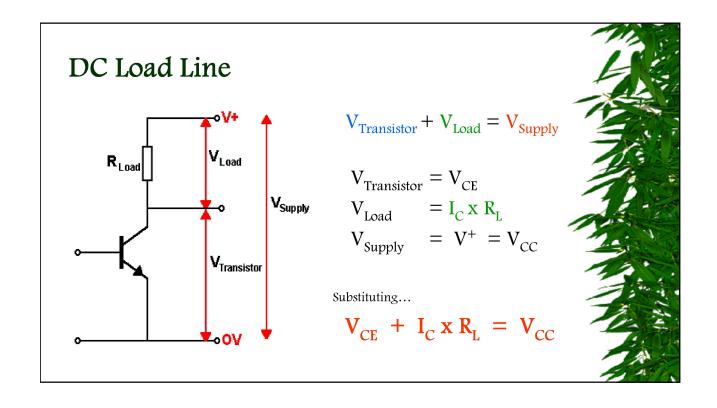

DC Load Line


$$V_{CE} + IC . RL = VCC$$


$$I_C . RL = -(V_{CE}) + V_{CC}$$


$$I_C = -\left(\frac{V_{CE}}{R_L}\right) + \left(\frac{V_{CC}}{R_L}\right)$$

$$I_C = -\left(\frac{1}{R_L}\right) V_{CE} + \left(\frac{V_{CC}}{R_L}\right)$$

$$Y = m . X + C$$

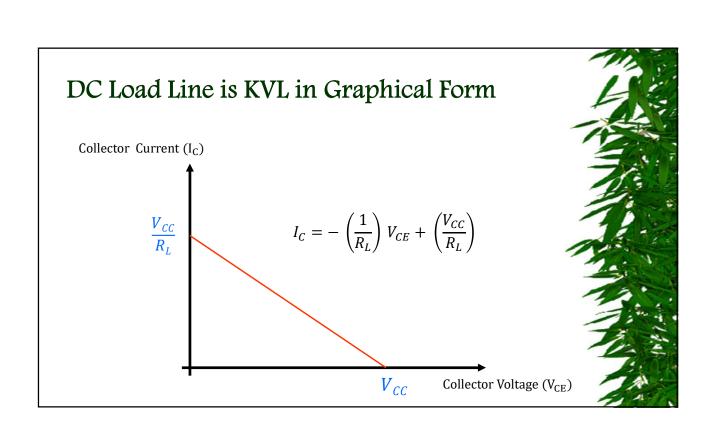

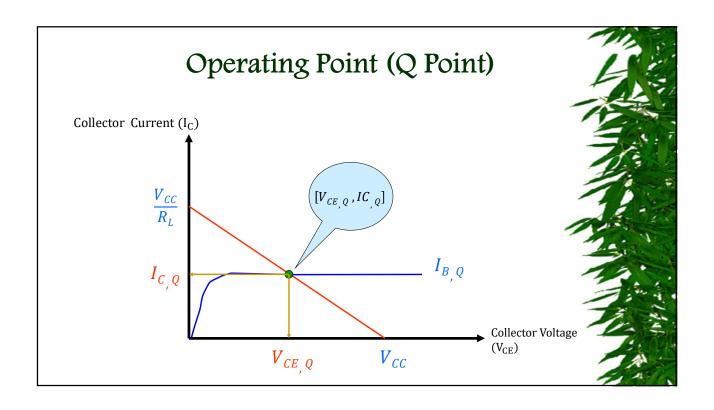


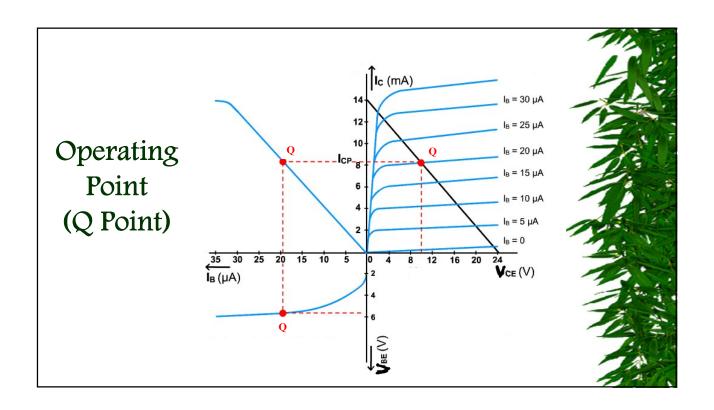


BJT Biasing Techniques

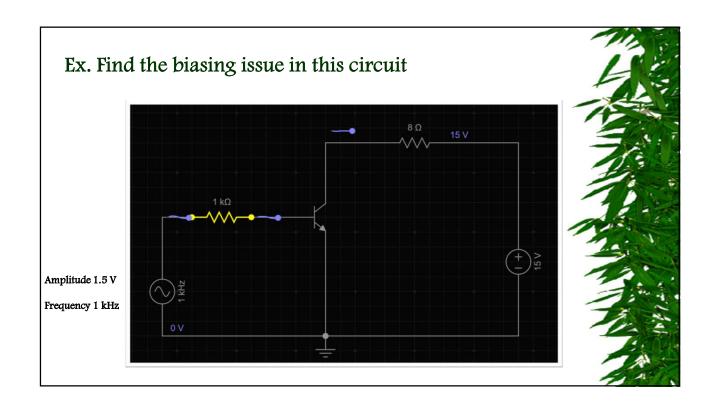- 1. Base Bias
- 2. Fixed Bias
- 3. Collector Feedback bias
- 4. Potential Divider Bias





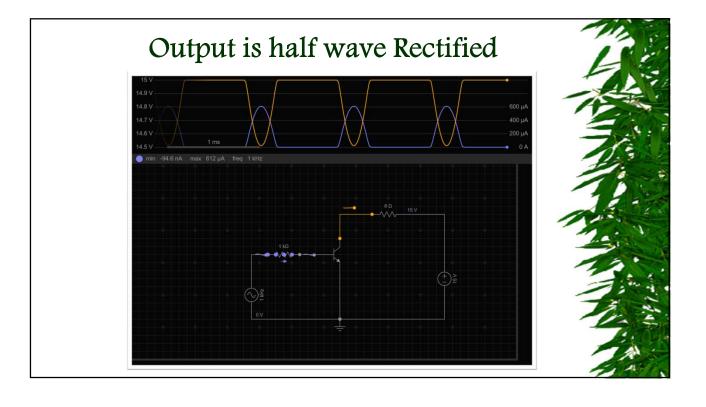

DC Bias of BJT Junctions

- Transistor must be in its active mode throughout the entire cycle of the input AC signal.
 - This is called 'Class A' operation.
- · Solution:
 - Superimpose the small input AC signal on a DC voltage.



