

Tutorial 1, Question 1.

Calculate the following;
1) Output Voltage
2) Current drawn from the input
3) Current delivered to a 100Ω load
4) Overall power gain

$$A_v = -\left(\frac{R_f}{R}\right)$$
$$A_v = -\left(\frac{40}{10}\right) = -4$$
$$V_o = A_v V_i$$
$$V_o = -4(0.5) = -2\text{ V}$$
$$I_i = \frac{0.5}{10} \text{ mA} = 50\text{ }\mu\text{A}$$
$$I_o = \frac{-2}{100} \text{ A} = -20\text{ mA}$$
$$P_o = |V_o I_o| = 2\text{ V} \times 20\text{ mA} = 40\text{ mW}$$
$$P_i = |V_i I_i| = 0.5\text{ V} \times 50\text{ }\mu\text{A} = 25\text{ }\mu\text{W}$$
$$G = \frac{P_o}{P_i} = \frac{40,000}{25} = 1600$$

20

Tutorial 1, Question 2.

Calculate the following;
1) Output Voltage
2) Current drawn from the input
3) Current delivered to a 100Ω load
4) Output power
5) Input power
6) Power Gain

$$A_v = -\left(\frac{R_f}{R}\right)$$
$$A_v = -\left(\frac{40}{10}\right) = -4$$
$$V_o = A_v V_i$$
$$V_o = -0.8 \sin \omega t \text{ V}$$
$$I_o = \frac{-0.8 \sin \omega t}{100} \text{ A} = -8 \sin \omega t \text{ mA}$$
$$P_o = \frac{1}{2} |V_{o,pk} I_{o,pk}| = \frac{1}{2} 0.8\text{ V} \times 8\text{ mA} = 3.2\text{ mW}$$
$$P_i = \frac{1}{2} |V_{i,pk} I_{i,pk}| = \frac{1}{2} 0.2\text{ V} \times 20\text{ }\mu\text{A} = 2\text{ }\mu\text{W}$$
$$G = \frac{P_o}{P_i} = \frac{3200}{2} = 1600$$

21

Tutorial 1, Question 3.

Calculate the following;
1) Voltage at the output
2) Current drawn from the input
3) Current delivered from this amplifier to a 100Ω load
4) AC power and DC Power delivered to the load
5) Overall power gain

$$A_v = -\left(\frac{40}{10}\right) = -4$$
$$V_o = A_v V_i$$
$$V_o = -4(0.5 + 0.2 \sin \omega t)$$
$$V_o = -(2 + 0.8 \sin \omega t) \text{ V}$$
$$I_i = (50 + 20 \sin \omega t) \text{ mA}$$
$$I_o = -(20 + 8 \sin \omega t) \text{ mA}$$

22

Tutorial 1, Question 4.

Calculate the following;
1) Output Voltage
2) Current drawn from the input
3) Current delivered from this amplifier to a 100Ω load
4) AC power and DC Power delivered to the load
5) Overall power gain

$$A_v = -\left(\frac{R_f}{R}\right)$$
$$A_v = -\left(\frac{100}{5}\right)$$
$$A_v = -20$$
$$V_o = A_v V_i$$
$$V_o = -20(20 + 5 \sin \omega t)$$
$$V_o = -(400 + 100 \sin \omega t) \text{ mV}$$

23

4) Non-Inverting Amplifier

Calculate the following;
1) Output Voltage
2) Current drawn from the input
3) Current delivered from this amplifier to a 100Ω load
4) AC power and DC Power delivered to the load
5) Overall power gain

24


Non-Inverting Amplifier

Calculate the following;
1) Output Voltage
2) Current drawn from the input
3) Current delivered from this amplifier to a 100Ω load
4) AC power and DC Power delivered to the load
5) Overall power gain

$$V_o = A_{vcl} \cdot (V_i - V_f)$$
$$V_o = A_{vcl} \cdot (V_i - V_f)$$
$$\frac{V_o}{A_{vcl}} = (V_i - V_f)$$
$$(V_i - V_f) = 0$$
$$V_i = V_f$$
$$V_i = \left(\frac{R_1}{R_1 + R_2}\right) \cdot V_o$$
$$A_v = \frac{V_o}{V_i} = \left(\frac{R_1 + R_2}{R_1}\right)$$
$$A_v = \left(1 + \frac{R_2}{R_1}\right)$$

25

Non-Inverting Amplifier

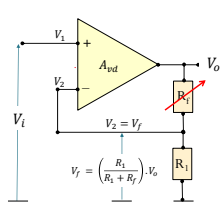


$$A_v = \left(1 + \frac{R_f}{R_1}\right)$$

- Opamp provides the virtual short circuit and current drive
- Vol. gain totally depend on the two resistors.
- Amplify ac and dc components of input signal by same gain.
- No phase change
- Voltage gain always > 1

26

Tutorial 1, Question 5.

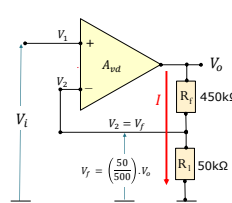


$$A_v = \left(1 + \frac{R_f}{R_1}\right)$$
$$A_v = \left(1 + \frac{450}{50}\right)$$
$$A_v = 10$$
$$V_o = A_v V_i$$
$$V_o = 10(100 + 20 \sin \omega t) \text{ mV}$$
$$V_o = (1000 + 200 \sin \omega t) \text{ mV}$$
$$V_o = 1 + 0.2 \sin \omega t \text{ V}$$

$$V_i = (100 + 20 \sin \omega t) \text{ mV}$$
$$I = \left(\frac{V_o}{500}\right) = 2 + 0.4 \sin \omega t \text{ } \mu\text{A}$$

27


5) Scaling Adder

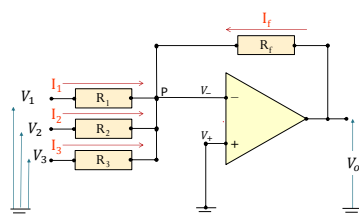

$$V_- = V_+ = 0$$
$$V_P = 0$$

28


Scaling Adder

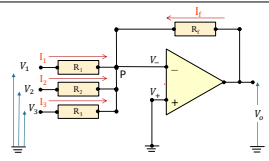

$$I_1 + I_2 + I_3 + I_f = 0$$
$$\left(\frac{V_1 - V_P}{R_1}\right) + \left(\frac{V_2 - V_P}{R_2}\right) + \left(\frac{V_3 - V_P}{R_3}\right) + \left(\frac{V_O - V_P}{R_f}\right) = 0$$
$$\left(\frac{V_1 - 0}{R_1}\right) + \left(\frac{V_2 - 0}{R_2}\right) + \left(\frac{V_3 - 0}{R_3}\right) + \left(\frac{V_O - 0}{R_f}\right) = 0$$
$$\left(\frac{V_1}{R_1}\right) + \left(\frac{V_2}{R_2}\right) + \left(\frac{V_3}{R_3}\right) + \left(\frac{V_O}{R_f}\right) = 0$$
$$V_O = -R_f \left[\left(\frac{V_1}{R_1}\right) + \left(\frac{V_2}{R_2}\right) + \left(\frac{V_3}{R_3}\right) \right]$$

29

Scaling Adder

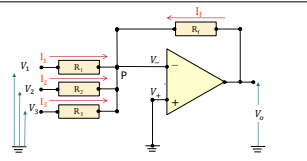

$$V_o = -R_f \left[\left(\frac{V_1}{R_1}\right) + \left(\frac{V_2}{R_2}\right) + \left(\frac{V_3}{R_3}\right) \right]$$
$$V_o = \left[\left(\frac{R_f}{R_1}\right) V_1 + \left(\frac{R_f}{R_2}\right) V_2 + \left(\frac{R_f}{R_3}\right) V_3 \right]$$
$$V_o = K_1 V_1 + K_2 V_2 + K_3 V_3$$

K_1, K_2, K_3 are scaling factors applied to respective inputs

If $R_1 = R_2 = R_3 = R$; $V_o = \frac{R_f}{R} (V_1 + V_2 + V_3)$

30