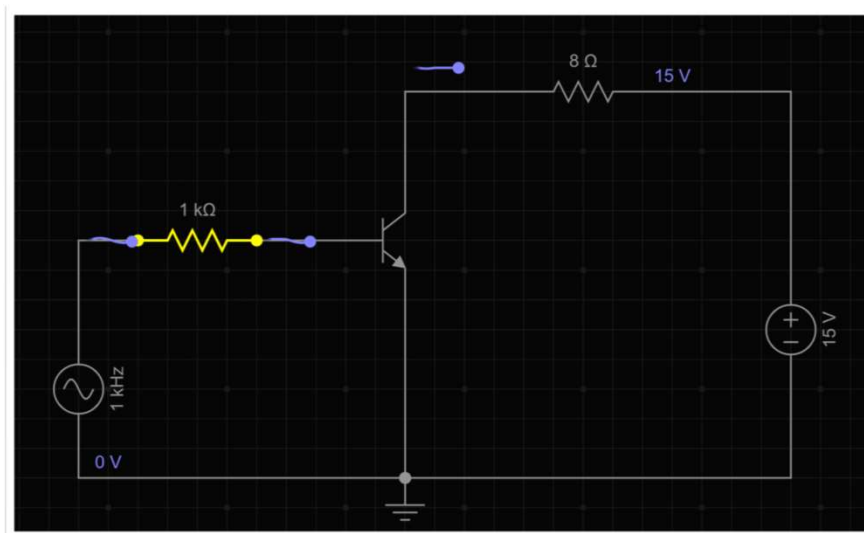


## BJT Biasing Techniques


1. Base Bias
2. Fixed Bias
3. Collector Feedback bias
4. Potential Divider Bias

Ex. Find the biasing issue in this circuit

Amplitude 1.5 V  
Frequency 1 kHz



## Output is half wave Rectified


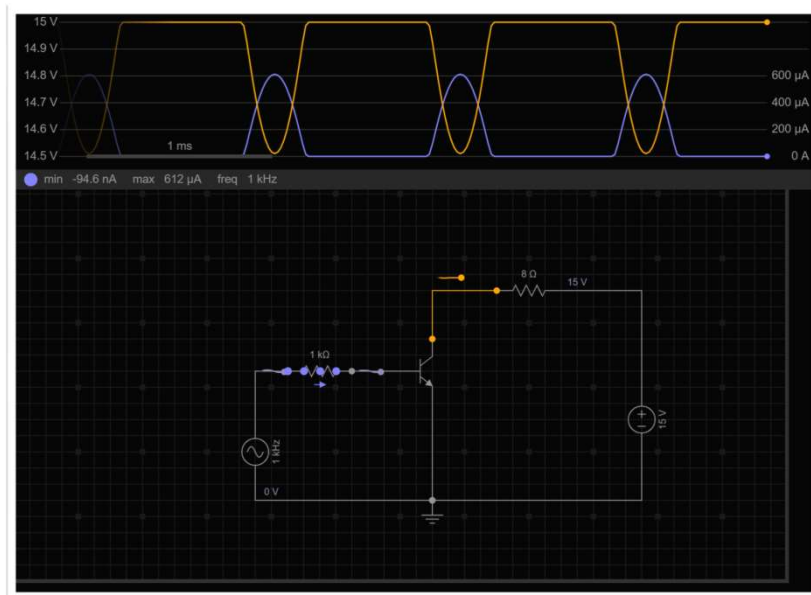


## DC Bias of BJT Junctions


- Transistor must be in its active mode throughout the entire cycle of the input AC signal.
  - This is called 'Class A' operation.
- Solution :
  - Superimpose the small input AC signal on a DC voltage.
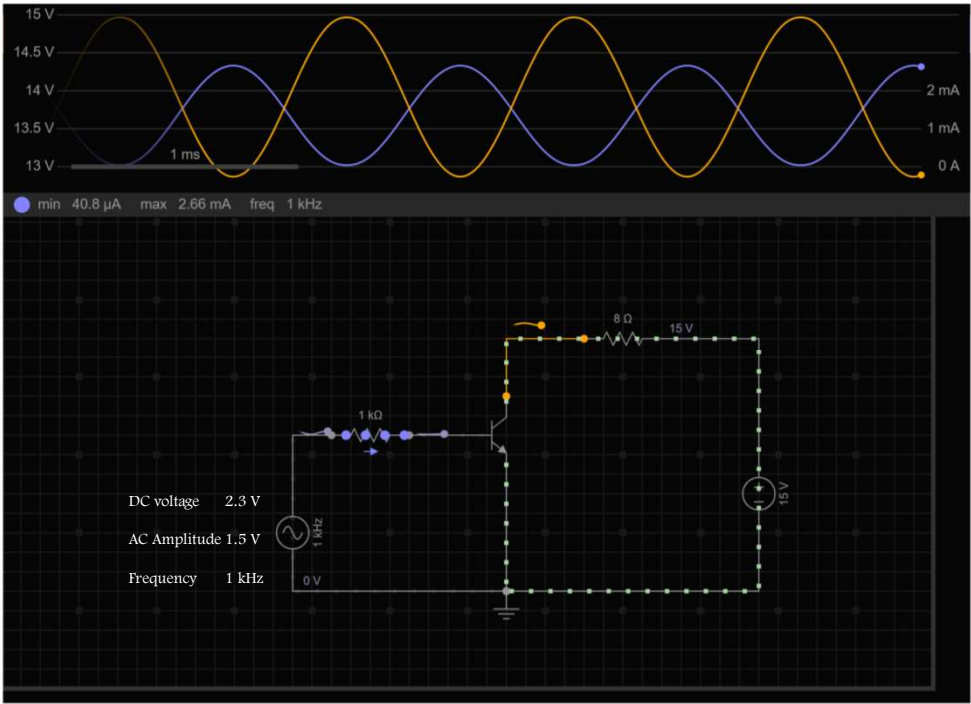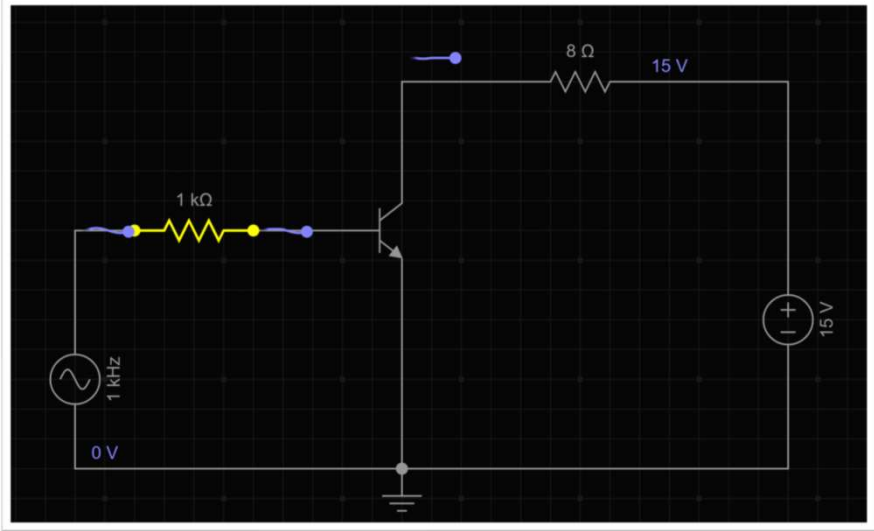
# The Base Bias

DC bias 2.3 V  
Amplitude 1.5  
Frequency 1 kHz




## DC Analysis


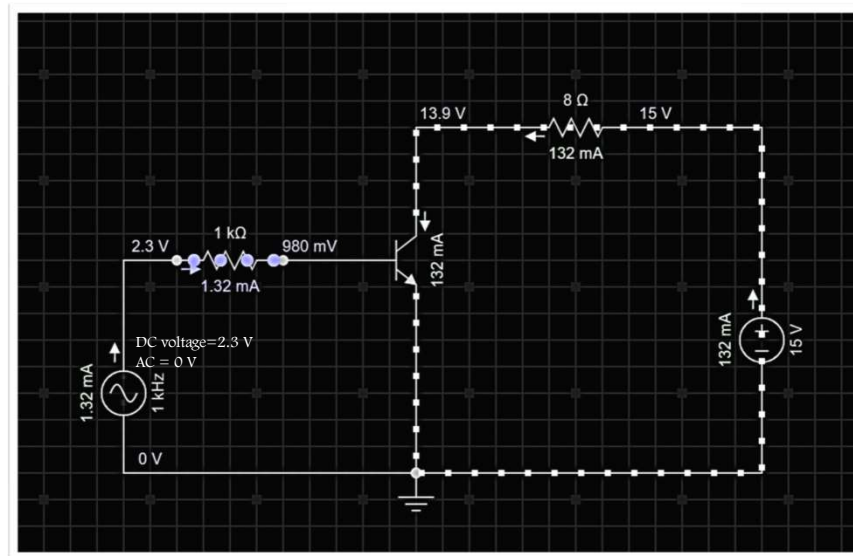

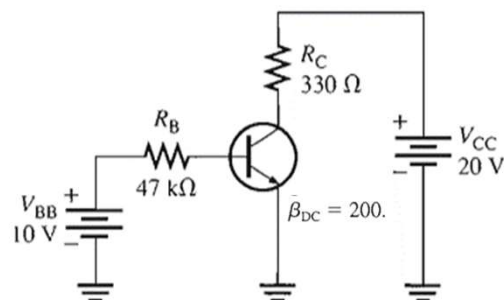
## Tutorial Question

Analyze this circuit. Find  $I_B$ ,  $I_C$  and  $V_{CE}$  and plot the DC load line






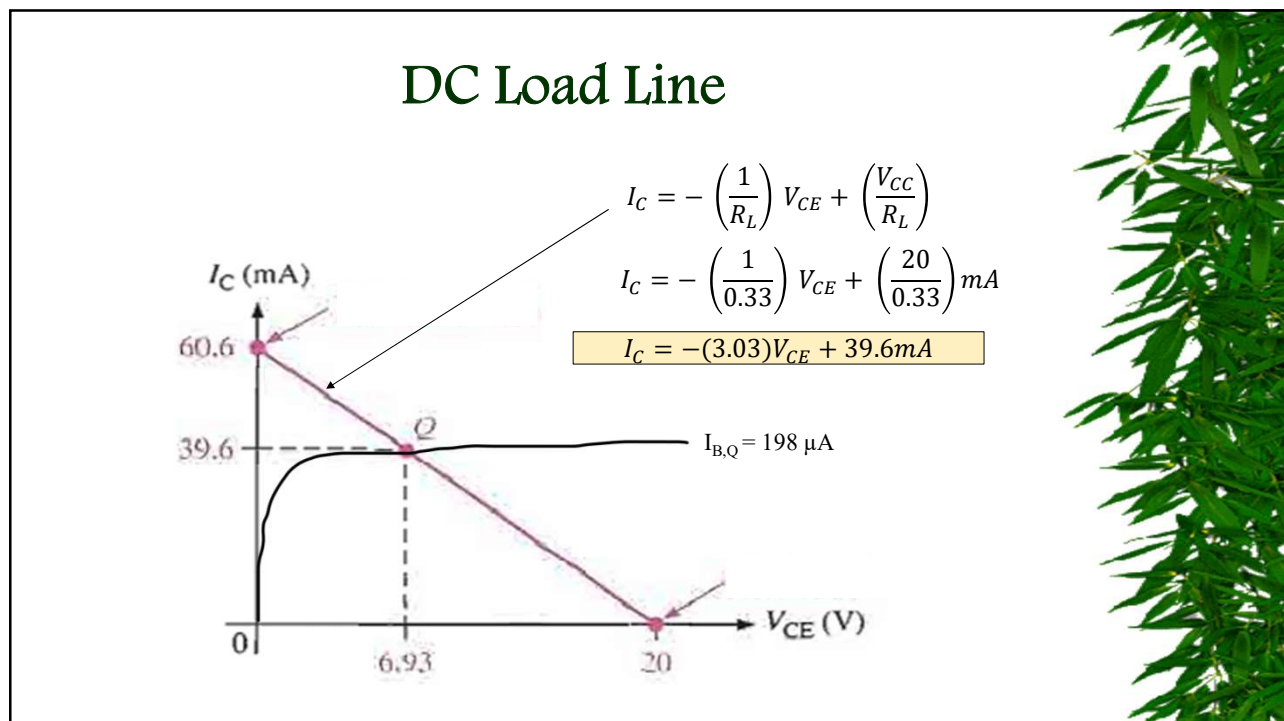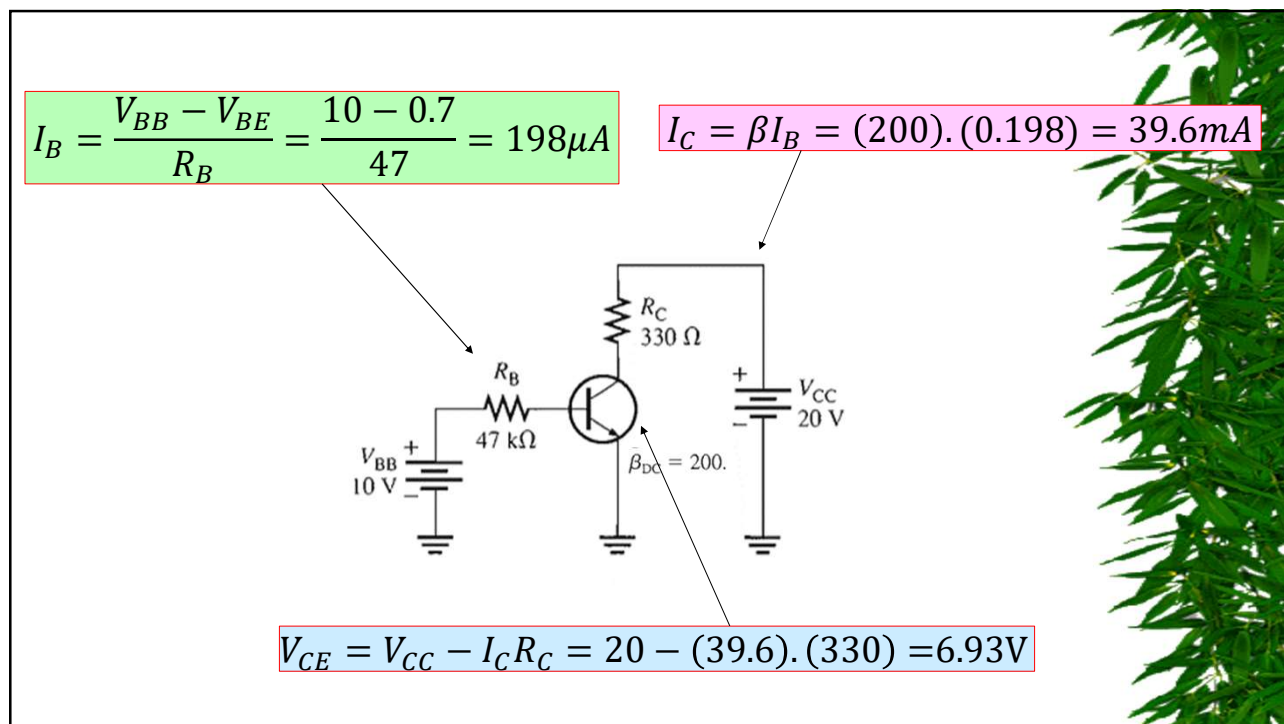

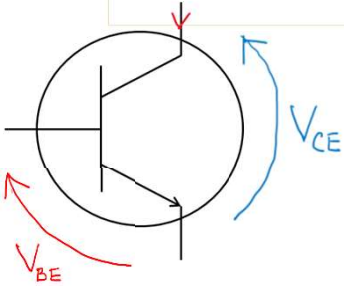
# Simplified Math Model of a BJT

$$i_C = I_S e^{V_{BE}/V_T} \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$
$$i_B = \frac{I_S}{\beta_F} e^{V_{BE}/V_T}$$




$I_S$  = Saturation current  
 $V_T$  = Thermal equivalent voltage  
 $\beta_F$  = Forward current gain in CE config.  
 $V_{AF}$  = Forward early voltage

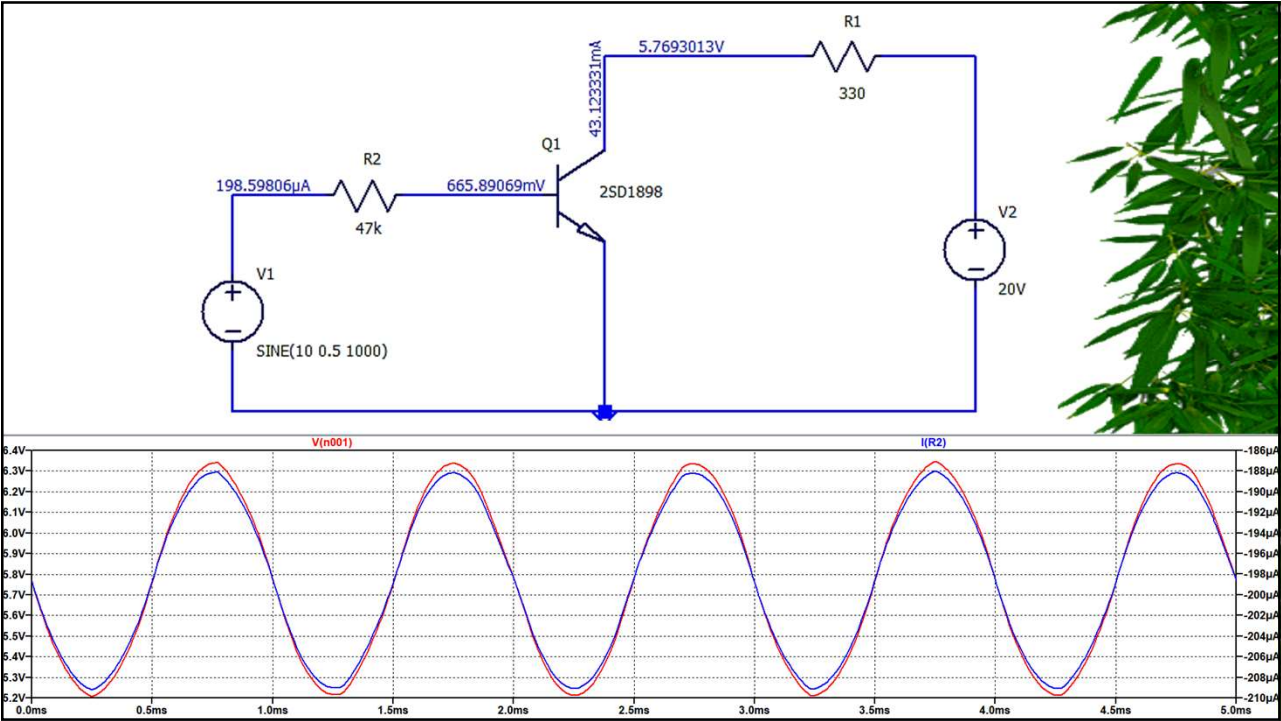Early voltage parameter that describes the variation in the effective width of the base region due to changes in  $V_{CB}$ . This effect (known as the Early effect) leads to a slight increase in the collector current with an increase in the collector-emitter voltage



## The Fixed Bias

### Fixed Bias Circuit

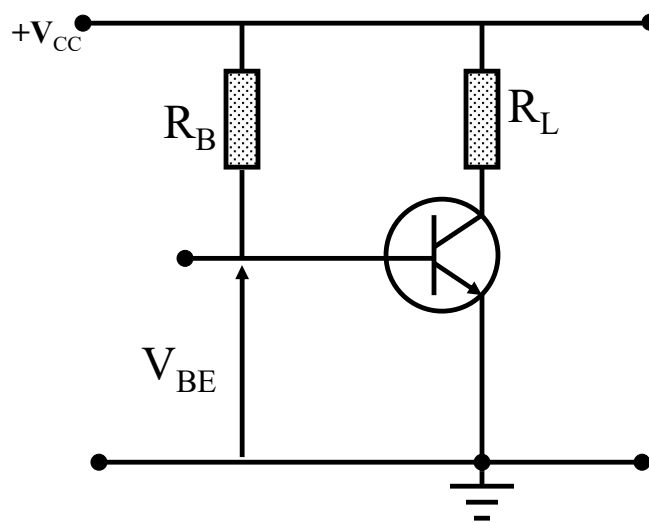

## Apply KVL

$$V_{BE} + I_B \cdot R_B = V_{CC}$$

### For analyzing

$$V_{BE} + I_B \cdot R_B = V_{CC}$$

$$I_B \cdot R_B = V_{CC} - V_{BE} \quad \begin{array}{l} 0.7 \text{ V} \\ \text{Typical} \end{array}$$

$$I_{B,Q} = (V_{CC} - V_{BE,Q}) / R_B$$

### For designing

$$V_{BE} + I_B \cdot R_B = V_{CC}$$

$$I_B \cdot R_B = V_{CC} - V_{BE} \quad \begin{array}{l} 0.7 \text{ V} \\ \text{Typical} \end{array}$$


$$R_B = (V_{CC} - V_{BE,Q}) / I_{B,Q}$$

## Plotting DC Load Line

Selecting Static Output  
Characteristics



## DC Load Line

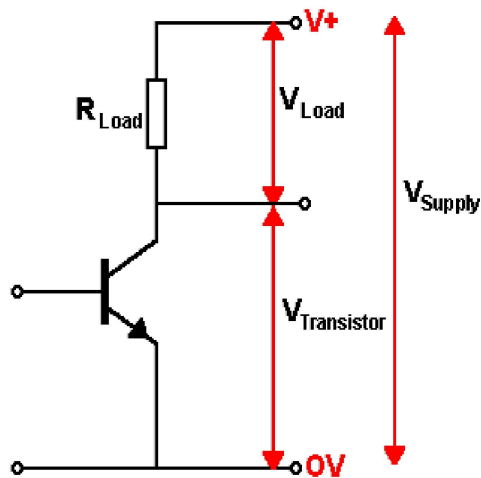

$$V_{Load} = I_C \times R_L$$

$$V_{Transistor} = V_{CE}$$

$$V_{Supply} = V^+ = V_{CC}$$

Using Kirchoff's Voltage Law ...

$$V_{CE} + I_C \times R_L = V_{CC}$$

## DC Load Line

$$V_{CE} + I_C \times R_L = V_{CC}$$


$$I_C \times R_L = -(V_{CE}) + V_{CC}$$

$$I_C = -\left(\frac{V_{CE}}{R_L}\right) + \left(\frac{V_{CC}}{R_L}\right)$$



$$I_C = -\left(\frac{1}{R_L}\right) V_{CE} + \left(\frac{V_{CC}}{R_L}\right)$$

$$Y = m \cdot X + C$$
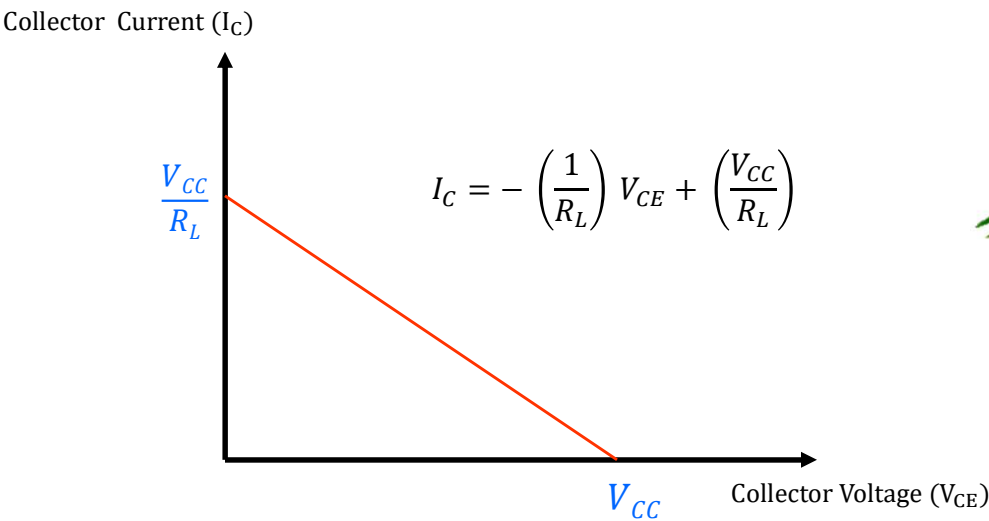
### DC Load Line is KVL in Graphical Form




### Operating Point (Q Point)

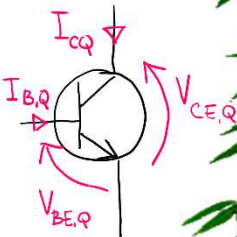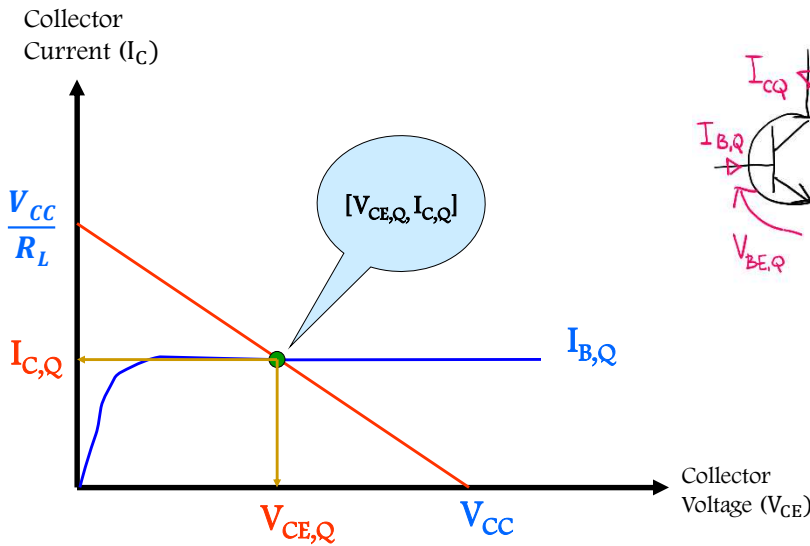

## Feeding the Input


- Input signal is a small a.c. signal (called drive signal)
  - Eg. Audio from a microphone
- Input signal should be arranged to ride on the d.c. bias. This is called superimposing ac on dc.
  - A coupling capacitor can be used for this purpose.
  - It will superimpose small ac signal on the dc base bias.

## Use of input coupling capacitor

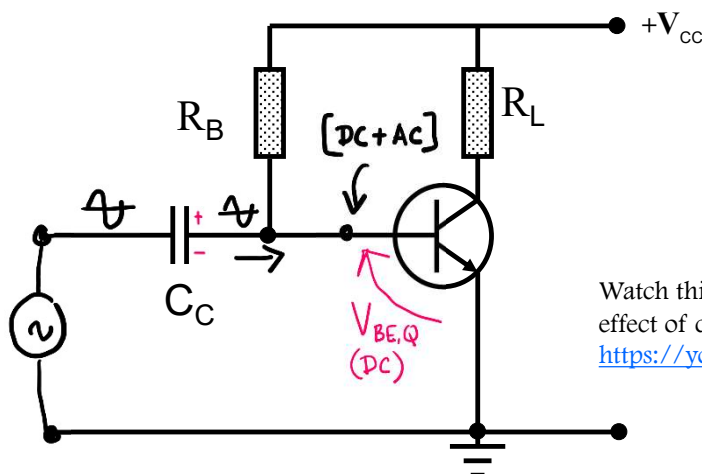


Watch this Video to understand the effect of coupling capacitor.  
<https://youtu.be/eF8e-FmtDh4>



# Use of an output coupling capacitor

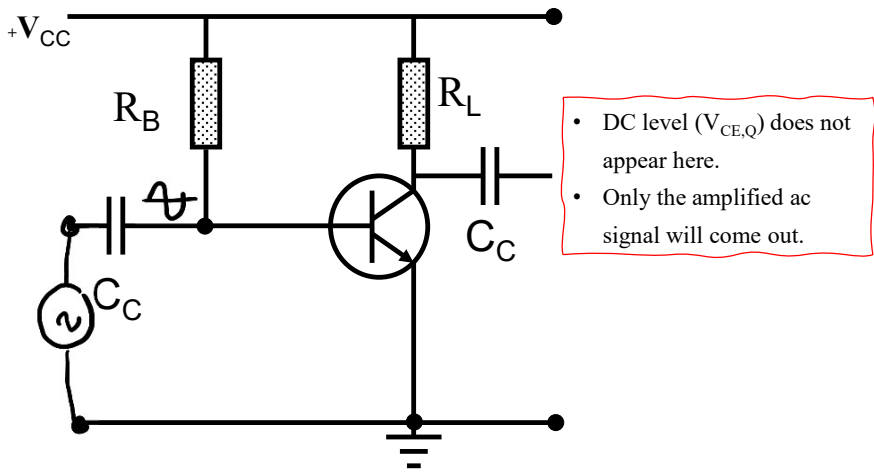

# An Example of a CE Amplifier

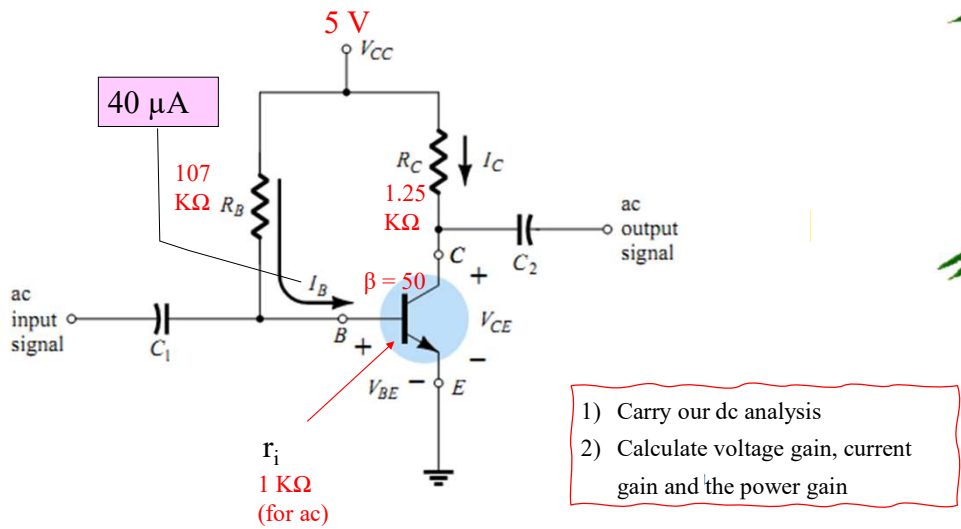

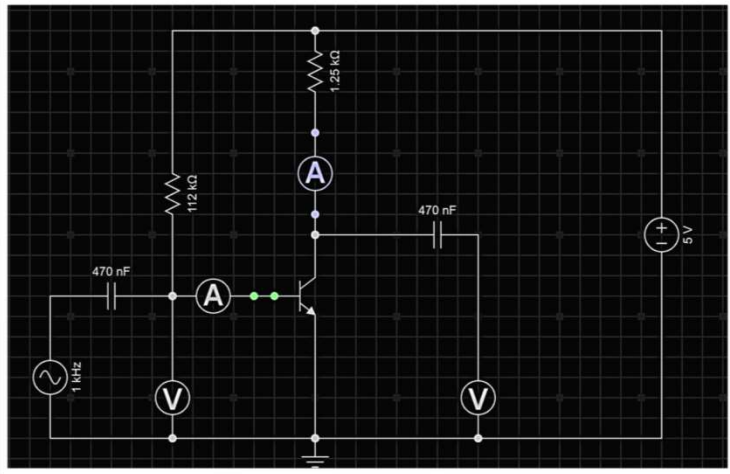
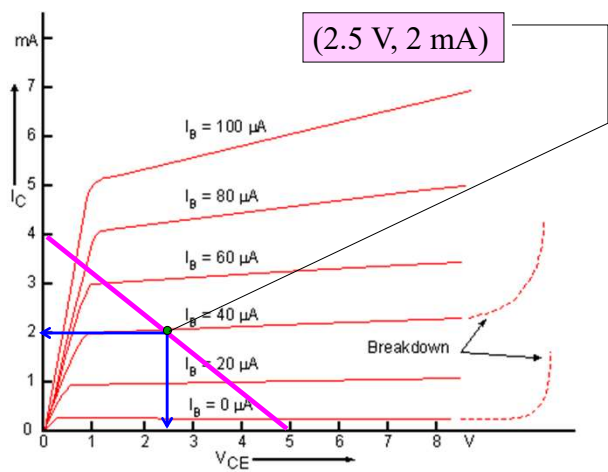
# Load Line on Static Output Characteristics





DC voltage	0 V	Saturation current	1 fA
Amplitude	16.8 mV	Forward beta	50
Frequency	1 kHz	Collector resistance	1 Ω
		Base resistance	1 Ω
		Emitter resistance	1 Ω



The graph shows the collector current  $I_C$  (mA) on the y-axis versus the collector-emitter voltage  $V_{CE}$  (V) on the x-axis. The y-axis ranges from 0 to 7 mA, and the x-axis ranges from 0 to 8 V. Several red curves represent different base currents  $I_B$ :  $I_B = 0 \mu A$ ,  $I_B = 20 \mu A$ ,  $I_B = 40 \mu A$ ,  $I_B = 60 \mu A$ ,  $I_B = 80 \mu A$ , and  $I_B = 100 \mu A$ . A blue load line is drawn from  $V_{CE} = 5$  V to  $I_C = 4$  mA. The operating point (Q-point) is marked at  $V_{CE} = 3$  V and  $I_C = 2$  mA. A green signal waveform is shown, and a red dashed line indicates the breakdown region.

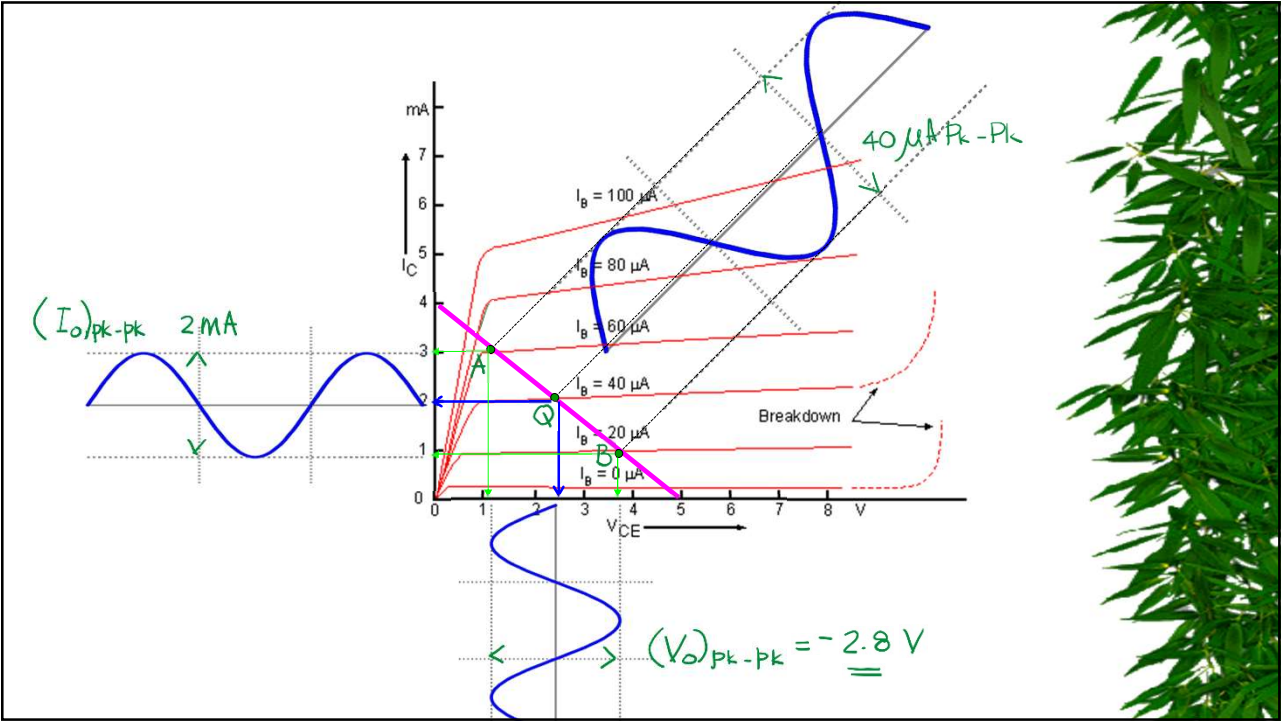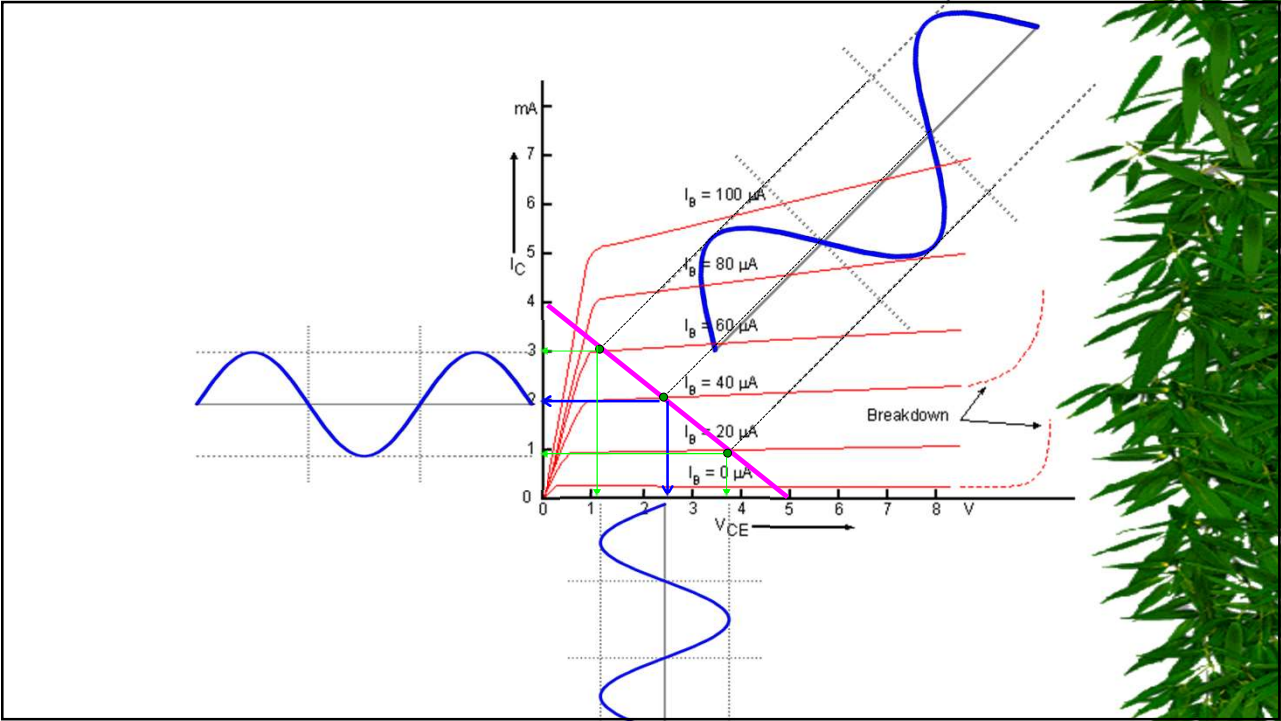

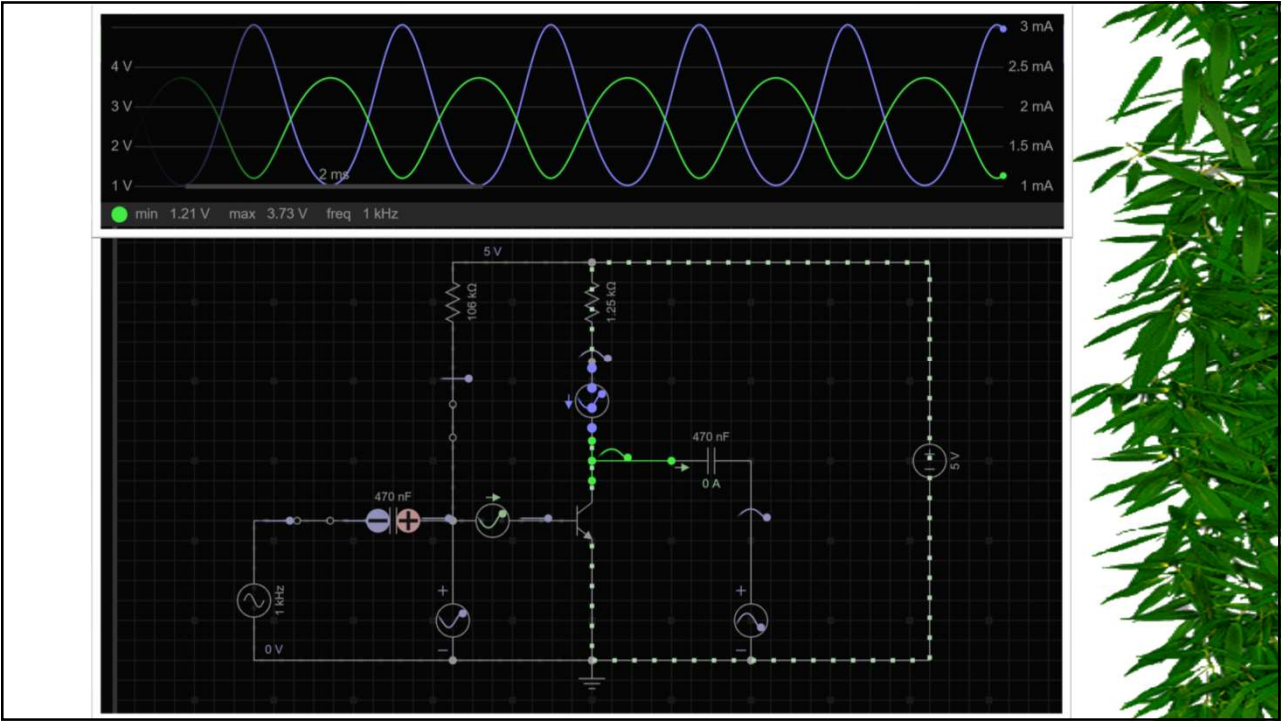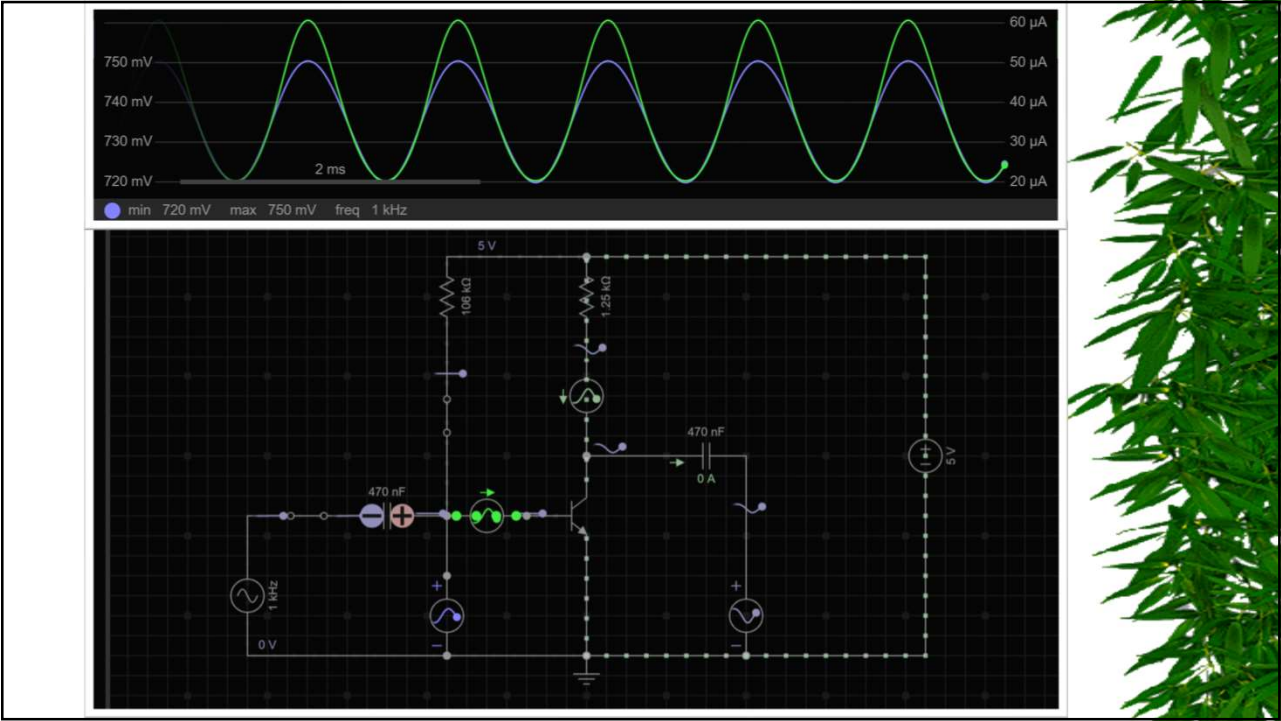

## Gain Calculations of an Amplifier

- Gain is a ratio between an output parameter and the corresponding input parameter
- Gain is specified in three ways
  - Power Gain (G)
  - Voltage Gain ( $A_v$ )
  - Current Gain ( $A_i$ )

## Current Gain of an Amplifier

- Ratio between the peak-peak output current variation and the peak-peak input current variation

$$A_i = \frac{I_{o,(pk-pk)}}{I_{i,(pk-pk)}}$$

Ex. Find the current gain of the circuit





$$A_i = \frac{I_{o,(pk-pk)}}{I_{i,(pk-pk)}}$$

## Voltage Gain of an Amplifier

- Ratio between the peak-peak output voltage variation and the peak-peak input voltage variation

$$A_v = \frac{V_{o,(pk-pk)}}{V_{i,(pk-pk)}}$$

Ex. Find the voltage gain of the circuit.  
Assume input resistance as 1 K $\Omega$





$$A_v = \frac{V_{o,(pk-pk)}}{V_{i,(pk-pk)}}$$

## Power Gain of an Amplifier

- Ratio between the output signal power and the input signal power

$$G = \frac{P_o}{P_i}$$


## Power Gain of an Amplifier

Power = voltage x current


$$G = \frac{V_o \cdot I_o}{V_i \cdot I_i} = \left( \frac{V_o}{V_i} \right) \cdot \left( \frac{I_o}{I_i} \right) = |A_v| \cdot |A_i|$$

$$G = |A_v| \cdot |A_i|$$

Ex. Find the power gain of the circuit


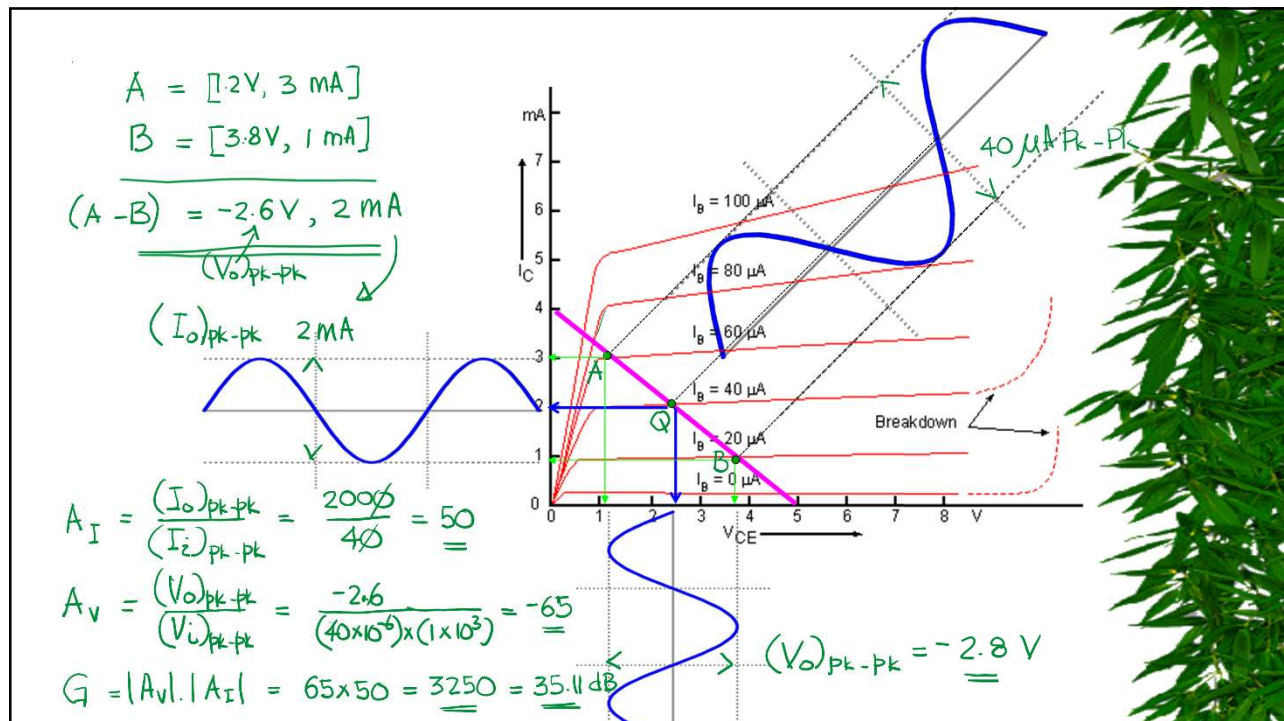


## Input voltage vs. Output voltage

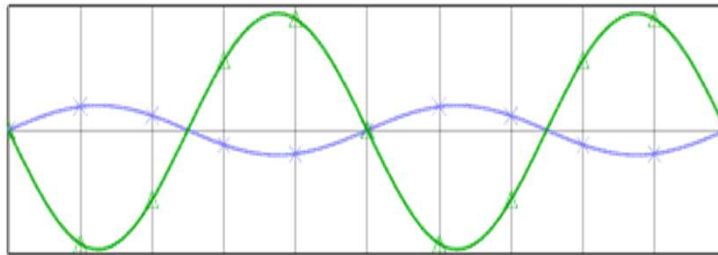

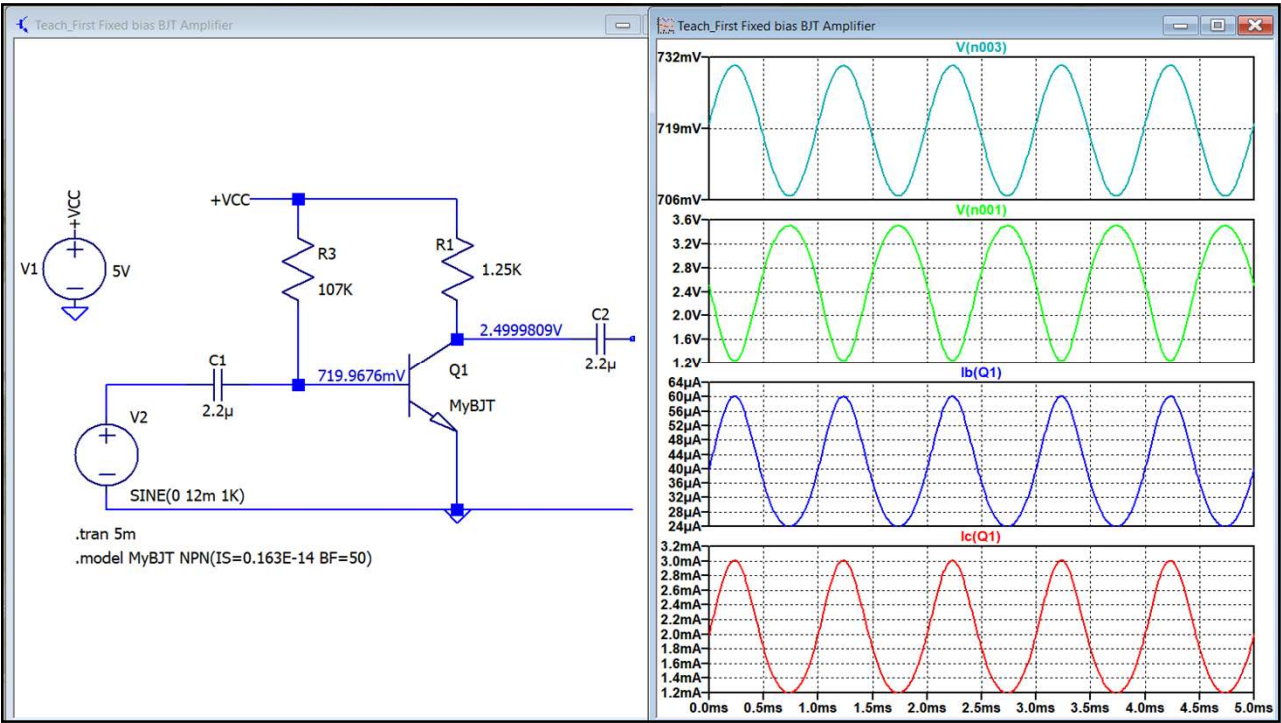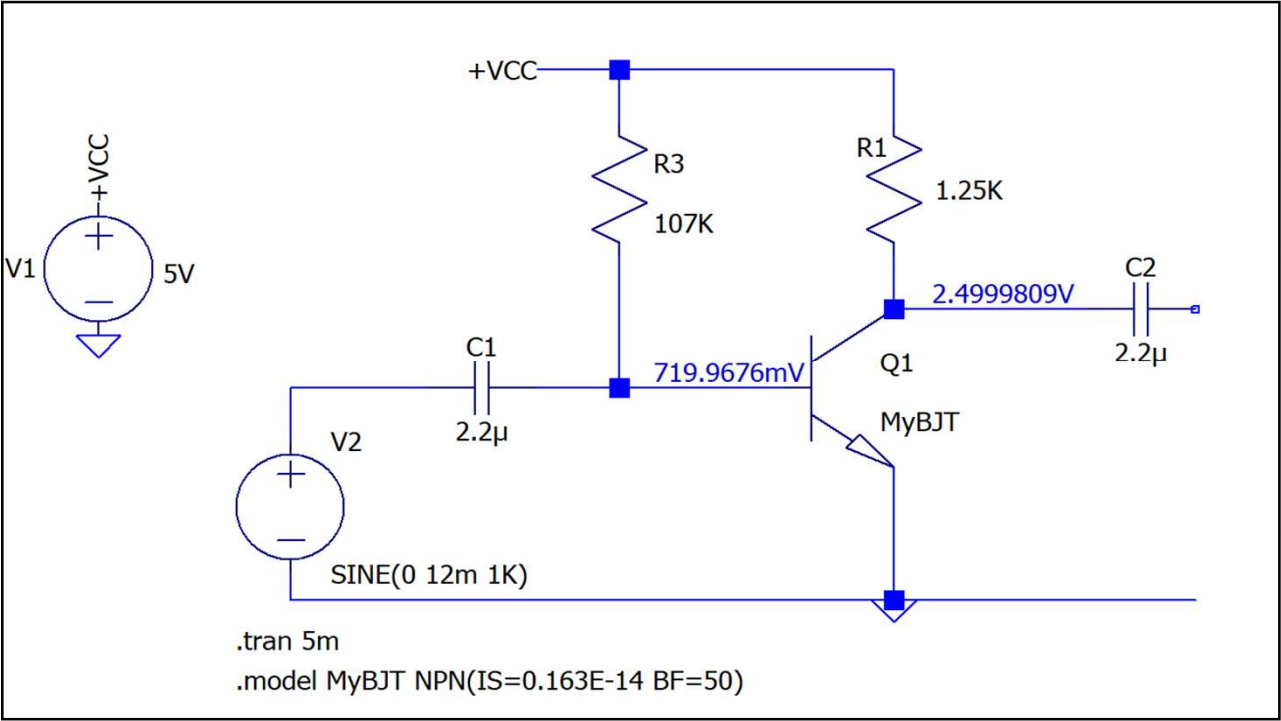
## Phase Inversion


- Output voltage measured between emitter and collector on a common-emitter amplifier, is 180 degrees out of phase with the input voltage waveform.
- Common-emitter amplifier is called an *inverting* amplifier circuit.





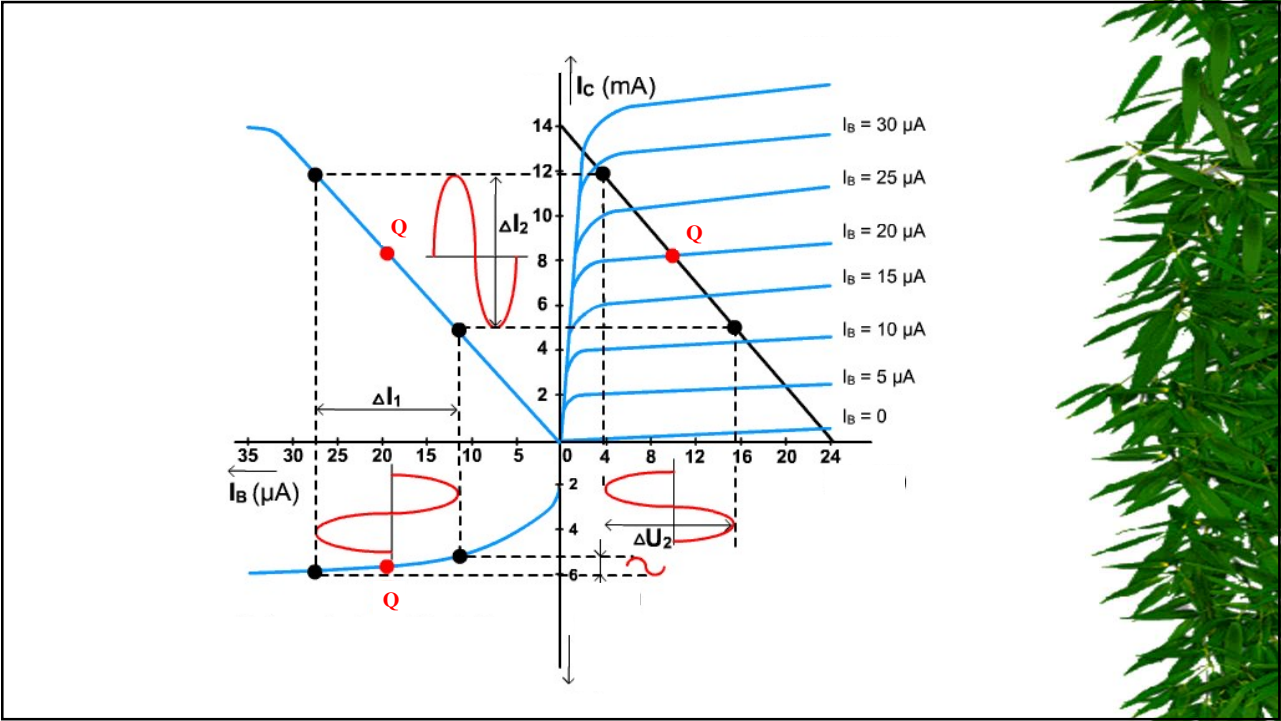

## Power Efficiency of an Amplifier

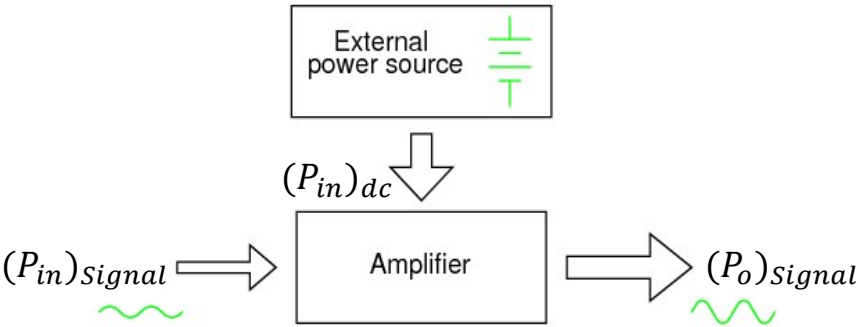

Power Efficiency = Proportion of the input DC power converted to useful output signal power




## Power Efficiency of an Amplifier

Efficiency = Proportion of the input DC power converted to useful output signal power

$$\eta = \frac{(P_o)_{\text{signal}}}{(P_{in})_{dc}} = \frac{(V_o \cdot I_o)_{\text{signal}}}{(V_{dc} \cdot I_{dc})_{\text{bias}}}$$


$$\eta = \frac{\left(\frac{V_{o(pk-p)}}{2 \cdot \sqrt{2}}\right) \cdot \left(\frac{I_{o(pk-p)}}{2 \cdot \sqrt{2}}\right)}{V_{dc} \cdot I_{dc}}$$

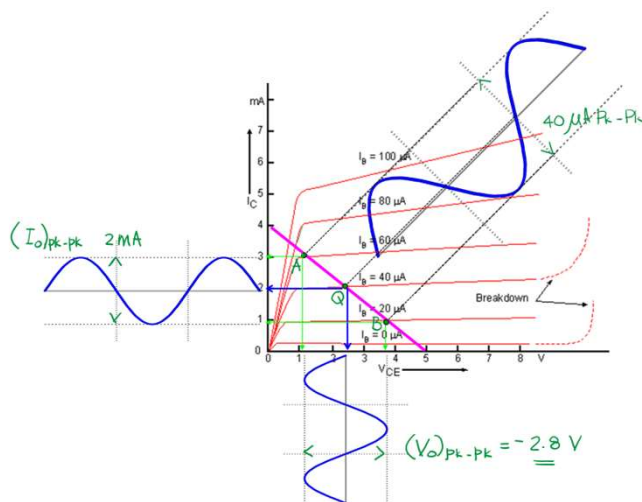Ex. Find the power efficiency of the example amplifier




$$\begin{aligned} \eta &= \frac{\left(\frac{V_{o(pk-p)}}{2 \cdot \sqrt{2}}\right) \cdot \left(\frac{I_{o(pk-p)}}{2 \cdot \sqrt{2}}\right)}{V_{dc} \cdot I_{dc}} \\ &= \frac{\left(\frac{2.8}{2 \cdot \sqrt{2}}\right) \cdot \left(\frac{2}{2 \cdot \sqrt{2}}\right)}{5 \times 2.04} \\ &= \frac{\left(\frac{2.8}{2 \cdot \sqrt{2}}\right) \cdot \left(\frac{2}{2 \cdot \sqrt{2}}\right)}{5 \times 2.04} \\ &= 0.0686 ! \end{aligned}$$


Theoretical Max. Efficiency of Class A

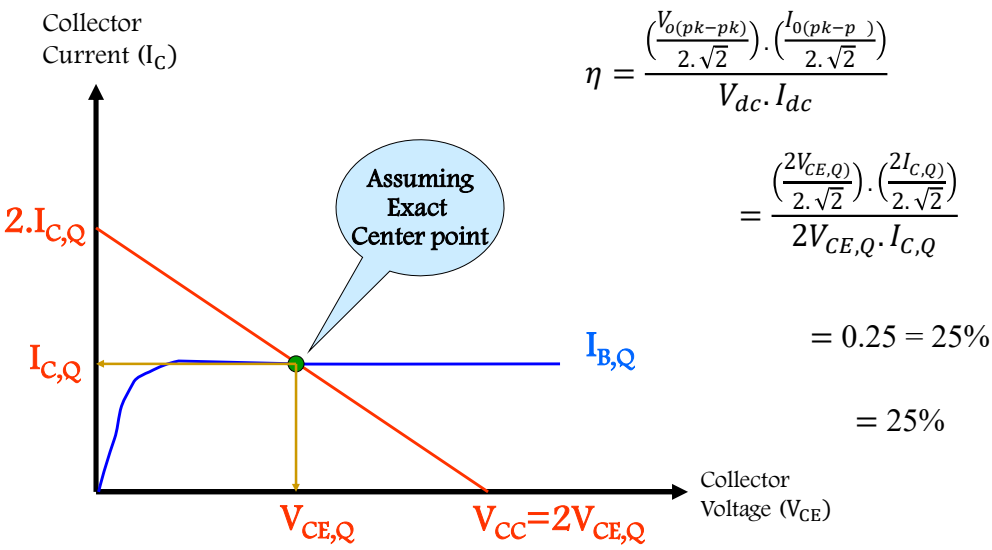

Power Dissipation in the BJT

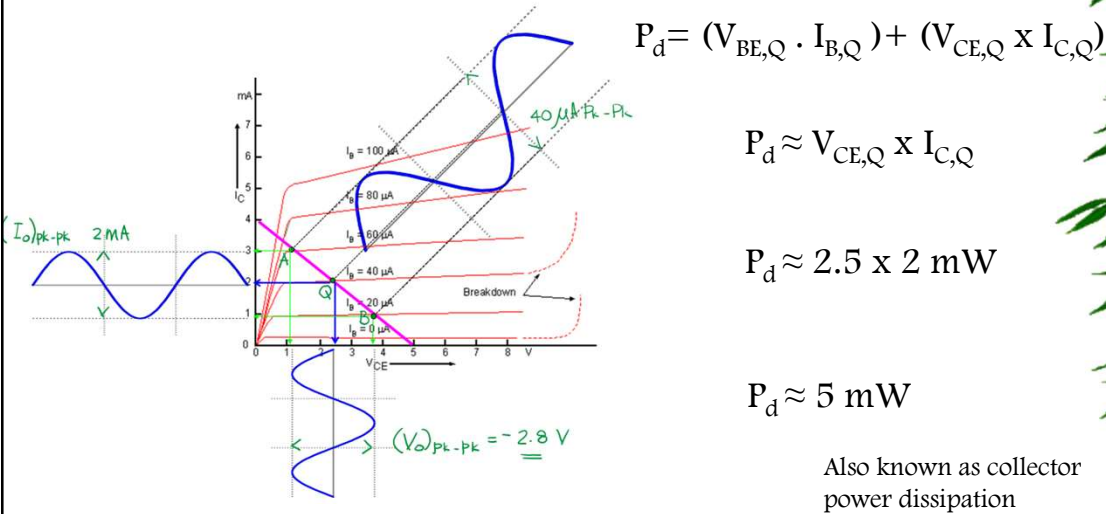


Ex. Calculate  $A_v$   $A_i$  and  $G$

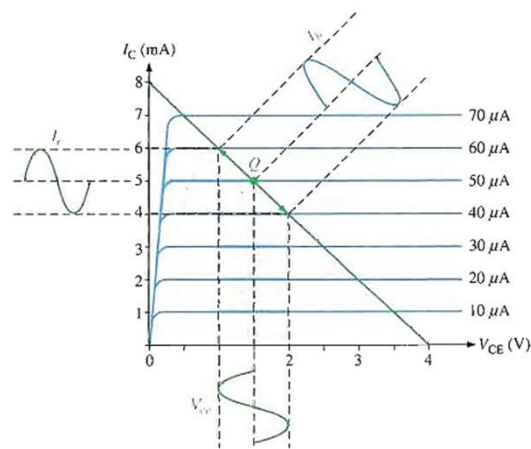


Assume  $R_i = 1\text{ K}\Omega$  for BE junction


Incorrect Q Point

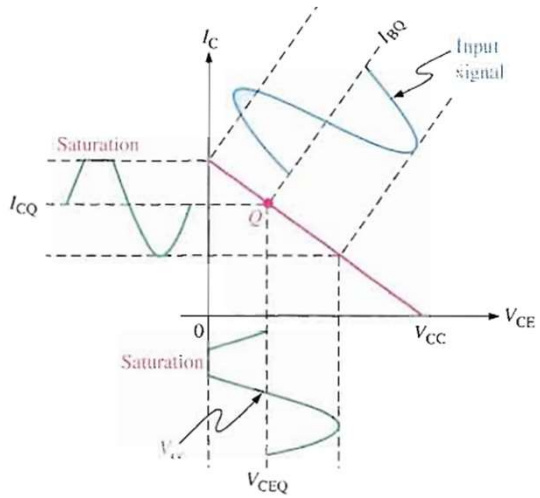

# Incorrect Q Point


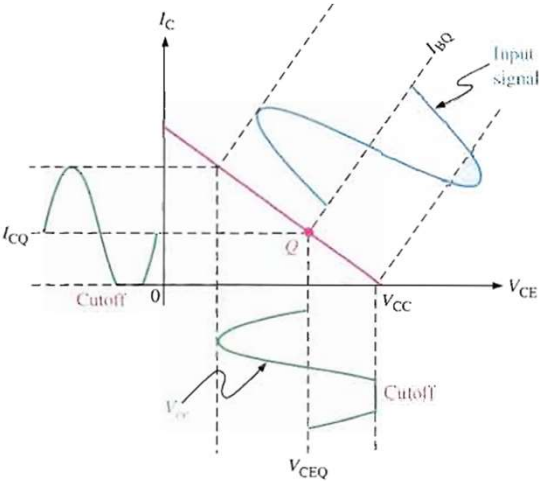


# Q Point

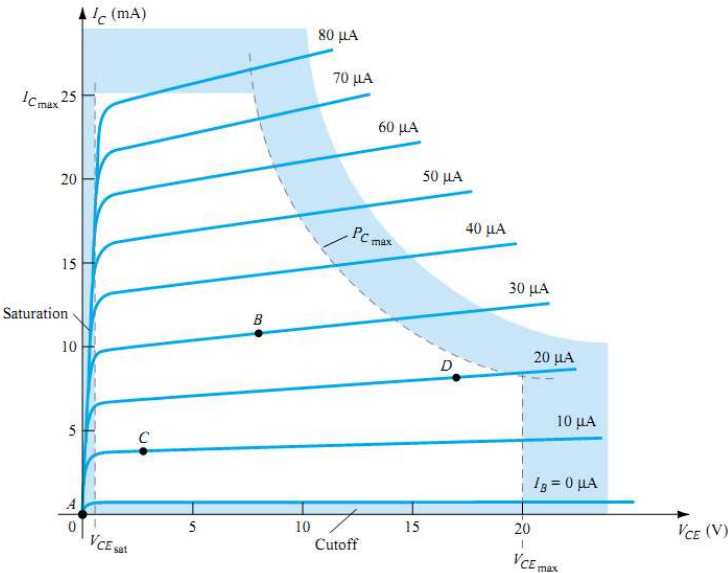




Too much drive...

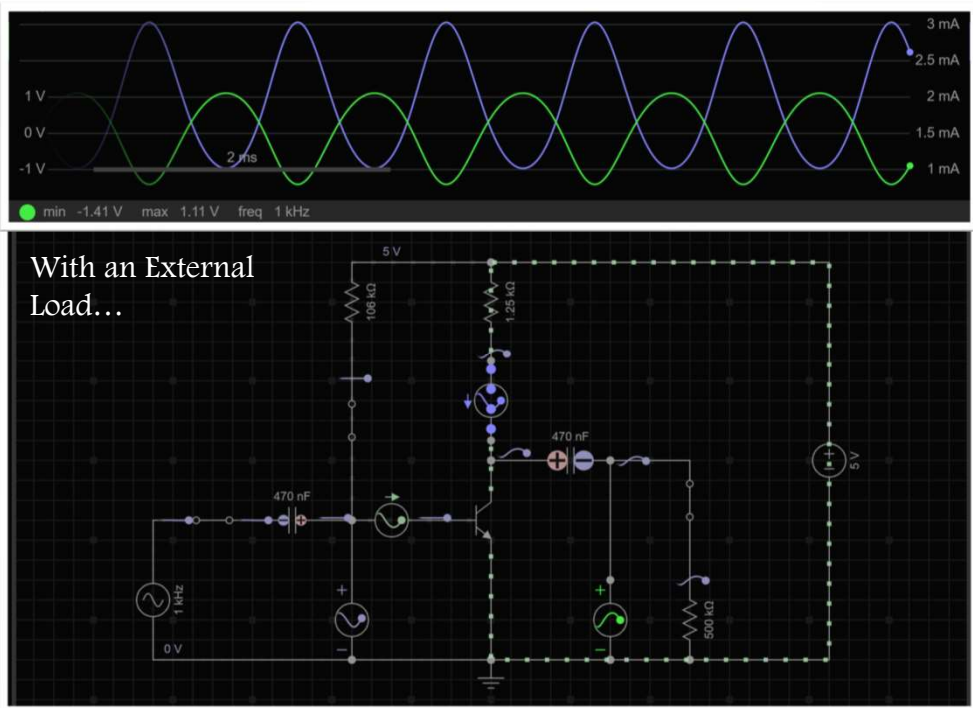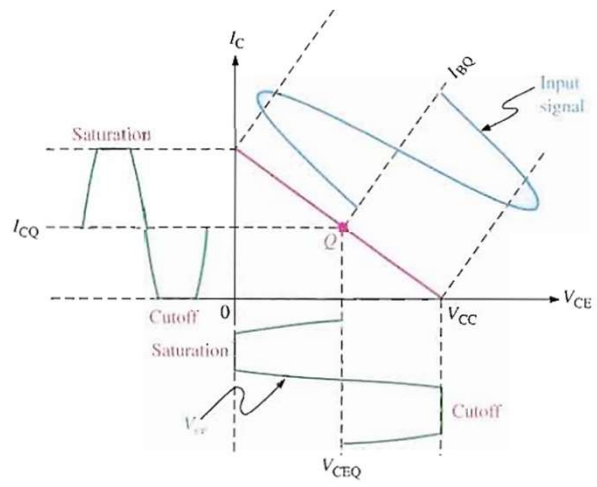



## AC load line and Gain Calculations

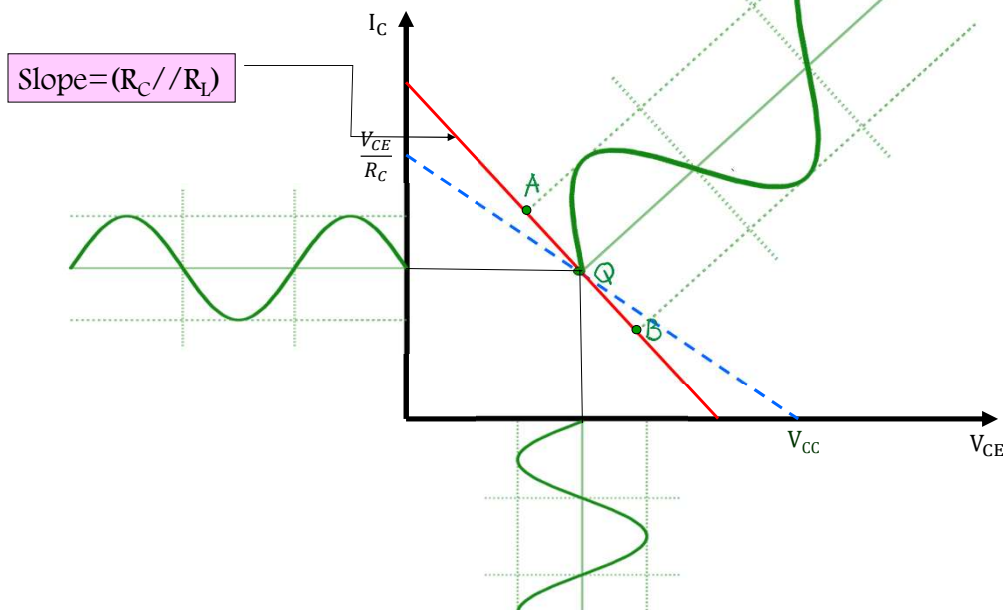

## Thermal Runaway

- \* Power is dissipated in the collector and hence it is made physically larger than the emitter and base region.
- \* As the power is dissipated the base-collector junction temperature increase.
- \* The reverse leakage current  $I_{CBO}$  increases due to the flow of thermally generated minority carriers

$$I_C = \alpha I_E + I_{CBO}$$

## Thermal Runaway

- \* Process is cumulative leading eventually to the destruction of the transistor.
- \* Thermal runaway can be prevented by using a heat sink.
- \* Emitter degenerative feedback can also be used.

