



## UNIVERSITY OF MORATUWA

Faculty of Engineering

Department of Electronic and Telecommunication Engineering

B.Sc.Engineering

Semester 2 (2018 Batch) Examination

### EN1013 ELECTRONICS I

Time allowed: *Two (2)* hours

February 2020

---

#### INSTRUCTIONS TO CANDIDATES:

- This paper contains 4 questions on 7 pages.
- Answer **all** questions.
- This paper contains **two** sections. Use a **separate** answer book for each section.
- All questions carry **equal** marks.
- This examination accounts for **70%** of the module assessment. The total maximum mark attainable is **100**. The marks assigned for each question & sections thereof are indicated in square brackets.
- The symbols used in this paper have their usual meanings.
- This is a closed book examination.
- Electronic/communication devices are not permitted. Only equipment allowed is a calculator approved and labeled by the Faculty of Engineering.
- Derivations are not required if they are not explicitly requested in the question.
- Assume reasonable values for any data not given in or with the examination paper. Clearly state such assumptions.
- If you have any doubt as to the interpretation of the wording of a question, make your own decision, and clearly state it.

#### ADDITIONAL MATERIAL:

- No additional material is provided.

This page is intentionally left blank.

## SECTION A

Question 1.

- (a) Draw the energy band diagram of a  $pn$  junction at equilibrium state. [3 marks]
- (b) Explain why the majority carriers will not continue to cross the  $pn$  junction until the energy levels of the two sides equalize. [3 marks]
- (c) Define the dynamic resistance of a diode. [2 marks]
- (d) Prove that the dynamic resistance of a forward-biased diode is inversely proportional to the forward DC current flowing through it. [3 marks]
- (e) A diode conducts a forward current of 10 mA when a 5 V battery is connected through a 1 k $\Omega$  resistor to forward bias it. In this instance, the forward voltage measured across the diode is 0.72 V.
  - i. Calculate the values of  $DC$  resistance and *dynamic* resistance of the diode. [2 marks]
  - ii. Derive the equation of the DC load line. Sketch it and mark the operating point. [3 marks]
  - iii. If an additional AC source of  $2\sin(\omega t)$  V is connected in series with the battery in the above circuit, find the new voltage across the diode. [5 marks]
- (f) Compare and contrast between the bipolar junction transistor (BJT) and the field effect transistor (FET). Give your answer in tabulated format. [4 marks]

**Question 2.**

A simple fixed-biased small signal amplifier made of the following electronic components produce an output signal of 4 V (peak to peak) across the collector load resistance when the input signal source provides a base current variation of 20  $\mu\text{A}$  (peak to peak).

A 12V DC supply

An input signal source

A 2.2  $\mu\text{F}$  coupling capacitor

BC547 BJT having a DC current gain ( $\beta_{DC}$ ) of 325 and  $R_i$  of 1  $\text{k}\Omega$

A Collector load having 820  $\Omega$  resistance

A variable resistor with variation ranging from 200  $\text{k}\Omega$  to 2  $\text{M}\Omega$

- (a) Sketch the circuit diagram of the amplifier. Properly label all circuit components, voltages and currents. [3 marks]
- (b) Find the required bias resistance to set the DC base bias current to 22.6 mA. [2 marks]
- (c) Find the quiescent collector current and voltage. [2 marks]
- (d) Derive the equation of the DC load line. [2 marks]
- (e) Sketch the DC load line. Mark the quiescent point on it and comment on its location on the DC load line. [2 marks]
- (f) Using the equation of the DC load line, find the peak to peak variation of the collector current. [2 marks]
- (g) Find the AC signal power delivered to the load. [2 marks]
- (h) Find the DC power dissipation in the load. [2 marks]
- (i) Mark all relevant points on the DC load line and graphically illustrate the operation of the circuit using appropriate waveforms on the graph. Clearly label the axes and the waveforms. [2 marks]
- (j) Find the voltage gain, current gain and the power gain of the circuit. [3 marks]
- (k) In what scenario you should not use the DC load line for gain calculations of an amplifier. Briefly explain the method used for gain calculations in such cases. [3 marks]

## SECTION B

Question 3.

- (a) Consider the following 5-variable Boolean function;

$$f(a, b, c, d, e) = \prod(2, 5, 7, 10, 13, 15, 16, 24, 31) \cdot D(0, 1, 18, 23, 26, 30),$$

where  $D(\cdot)$  denotes don't care maxterms.

- i. Draw the corresponding 4-variable Karnaugh maps for the two cases:  $a = 0$  and  $a = 1$ . [4 marks]
  - ii. Hence, express the Boolean function  $f$  in the *product-of-sums* form with a minimal number of literals. [9 marks]
- (b) A two-bit magnitude comparator compares the magnitude of two 2-bit binary numbers  $A$  and  $B$ . The 2-bit magnitude comparator has four inputs  $A_1, A_0, B_1$  and  $B_0$ , and three outputs  $X, Y$  and  $Z$ . Here,  $A_1, A_0, B_1$  and  $B_0$  are the bits of  $A$  and  $B$ , that is,  $A = A_1A_0$  and  $B = B_1B_0$ . Furthermore, the outputs  $X, Y$  and  $Z$  indicate  $A > B, A = B$  and  $A < B$ , respectively.
- i. Express the truth table corresponding to the 2-bit magnitude comparator. [3 marks]
  - ii. Derive the simplified Boolean expressions, in the *sum-of-products* form with a minimal number of literals, for the outputs  $X, Y$  and  $Z$ . [6 marks]
  - iii. Draw the realization of the digital circuit of  $X$  using only 2-input and 3-input NAND gates. [3 marks]

**Question 4.**

- (a) Consider the design of a full adder of which the inputs are  $X$ ,  $Y$  and  $C_{i-1}$  and the outputs are  $S$  and  $C_i$ . Here,  $X$  and  $Y$  denote the two bits to be added, and  $C_{i-1}$  denotes the carry from the previous full adder. Further,  $S$  and  $C_i$  denote the sum and carry of the full adder, respectively.
- Express the truth table corresponding to the full adder. [2 marks]
  - Draw the realization of the full adder using two 2-to-4-line decoders with *active-high* enable inputs, and NOT and OR gates. Clearly indicate all the inputs and outputs of the 2-to-4-line decoders. [5 marks]
- (b) The parameters of a 2-input transistor-transistor logic (TTL) NAND gate is presented in Table Q4. Calculate the following specifications of the 2-input TTL NAND gate using the values given in Table Q4.
- Fan-out [2 marks]
  - Propagation delay [2 marks]
  - Power dissipation [2 marks]
  - Noise margin [2 marks]

Table Q4

Parameter	Description	Value
$V_{CC}$	Supply voltage	5 V
$I_{CCH}$	High-level supply current	2 mA
$I_{CCL}$	Low-level supply current	4 mA
$V_{OH}$	High-level output voltage (min)	2.8 V
$V_{OL}$	Low-level output voltage (max)	0.5 V
$V_{IH}$	High-level input voltage (min)	2 V
$V_{IL}$	Low-level input voltage (max)	0.8 V
$I_{OH}$	High-level output current (max)	1 mA
$I_{OL}$	Low-level output current (max)	20 mA
$I_{IH}$	High-level input current (max)	0.05 mA
$I_{IL}$	Low-level input current (max)	2 mA
$t_{PLH}$	Low-to-high delay	12 ns
$t_{PHL}$	High-to-low delay	8 ns

- (c) A 2-input NAND gate of the diode-transistor logic (DTL) family is shown in Figure Q4. The transistor  $Q1$  and all the diodes are made of Si, and  $h_{FE}$  ( $\beta_{DC}$ ) of the transistor  $Q1$  is 20. Consider the case where the output  $Y$  of this logic gate is connected to  $N$  similar logic gates, and the transistor  $Q1$  is *saturated*. Further, assume that  $I_B$  of the transistor  $Q1$  is 0.45 mA.

 


Figure Q4

- Calculate the total collector current  $I_C$  of the transistor  $Q1$  as a function of  $N$ . [6 marks]
- Find the highest value of  $N$  that will keep the transistor  $Q1$  in saturation. [4 marks]

- End of Question Paper -