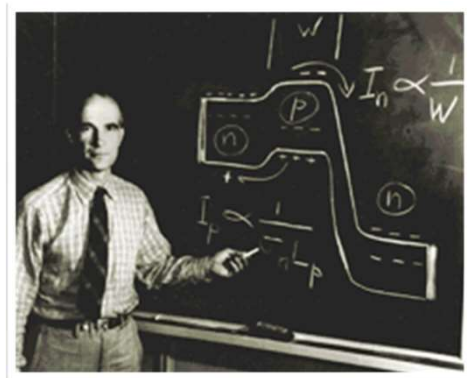


Bipolar Junction Transistor Amplifier

Kithsiri Samarasinghe

Senior Lecturer
Dept. of Electronic & Telecommunication Engineering

The Great Invention in 1948




William Shockley explaining their invention

Team : William Shockley, John Bardeen, Walter Brattain


Bell Laboratories, USA

The First-ever Transistor

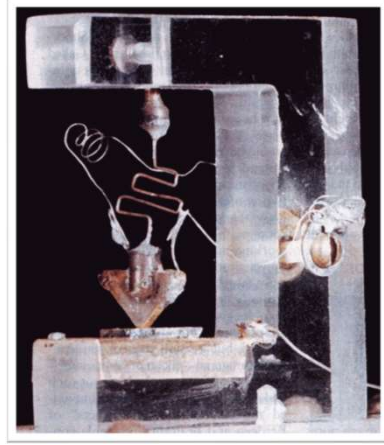


World's First Transistor developed by Shokley, Bardeen and Brattain

Early Developments

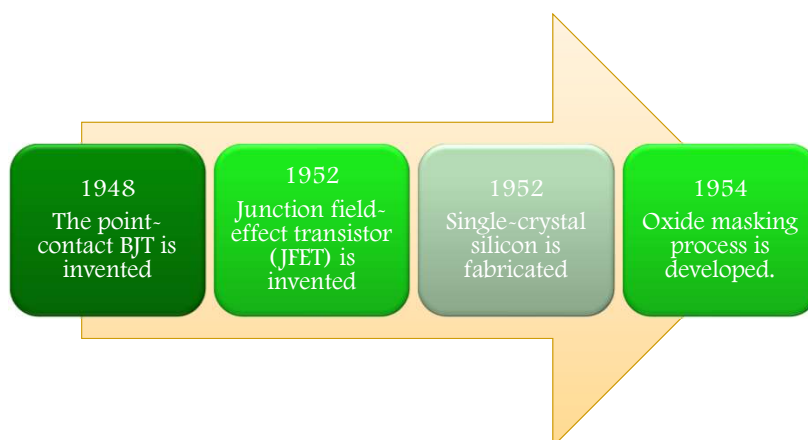


Packages for BJT

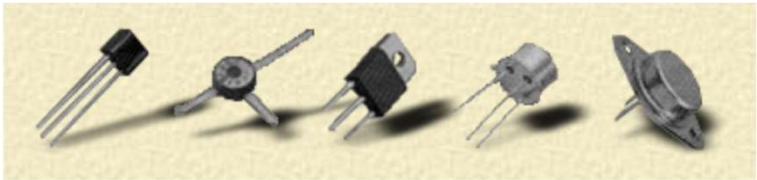

- TO 18 , TO 39, TO 92, TO 99
- TO 5, TO247
- TO 3


Packaging BJTs for practical use

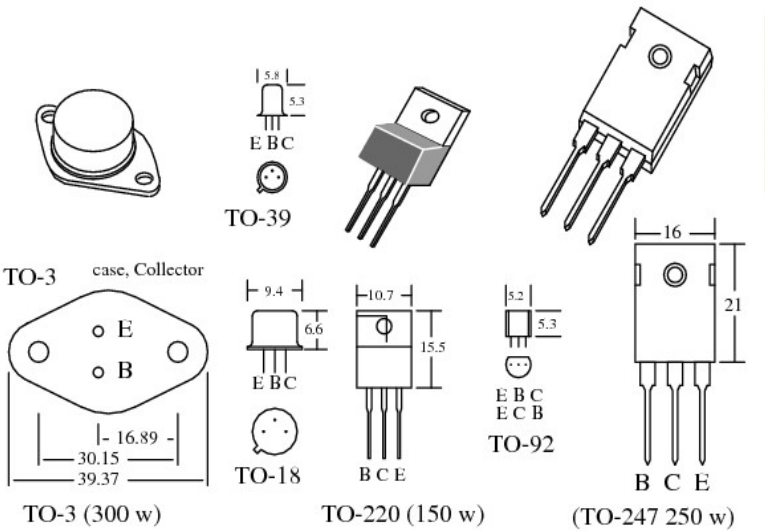

Miniaturizing trend



A Paradigm Shift

TO-92

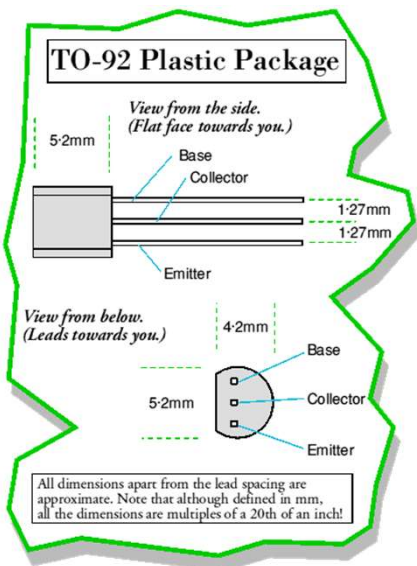

Three Terminals of a BJT

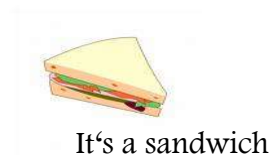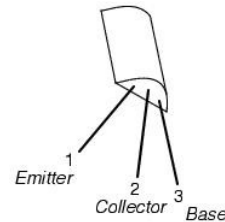- **E** ~ Emitter
- **B** ~ Base
- **C** ~ Collector






Internal Structure



Three Layers of
Extrinsic
Semiconductors

Middle Layer is
the BASE


Base is thin

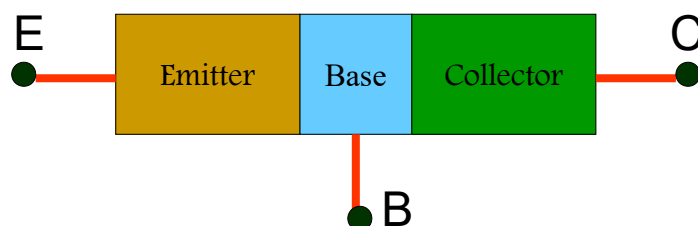

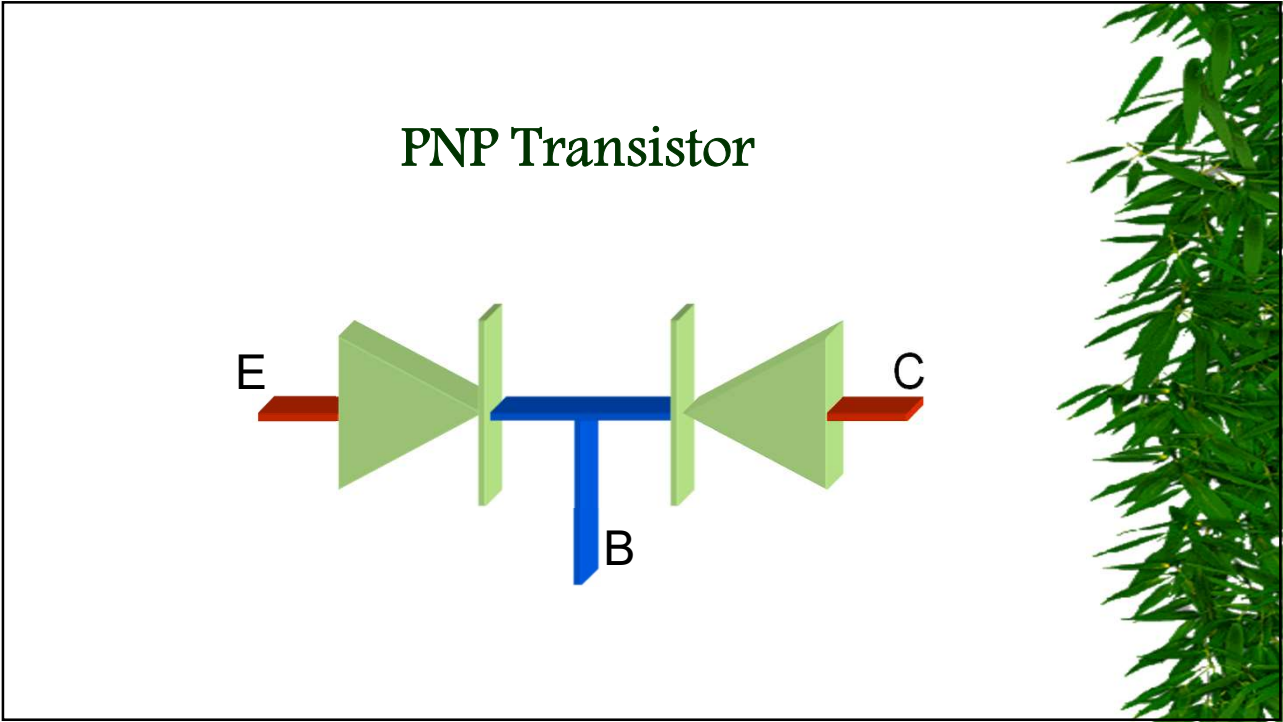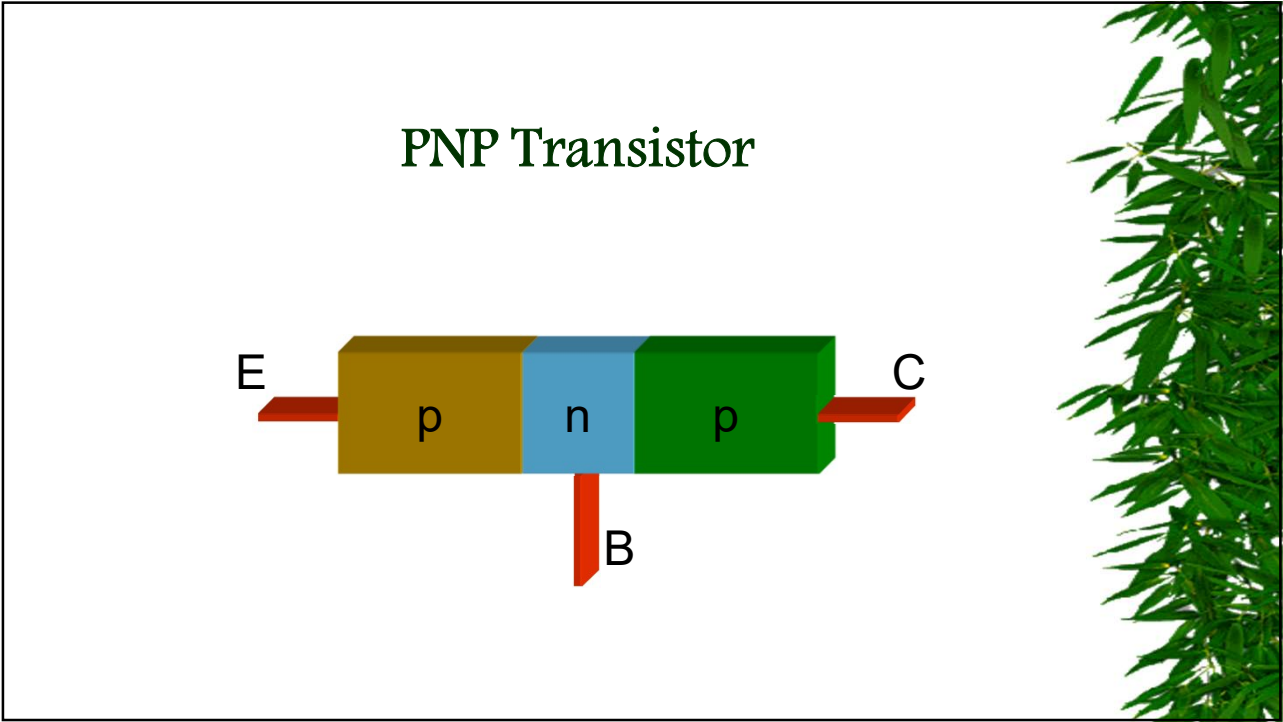


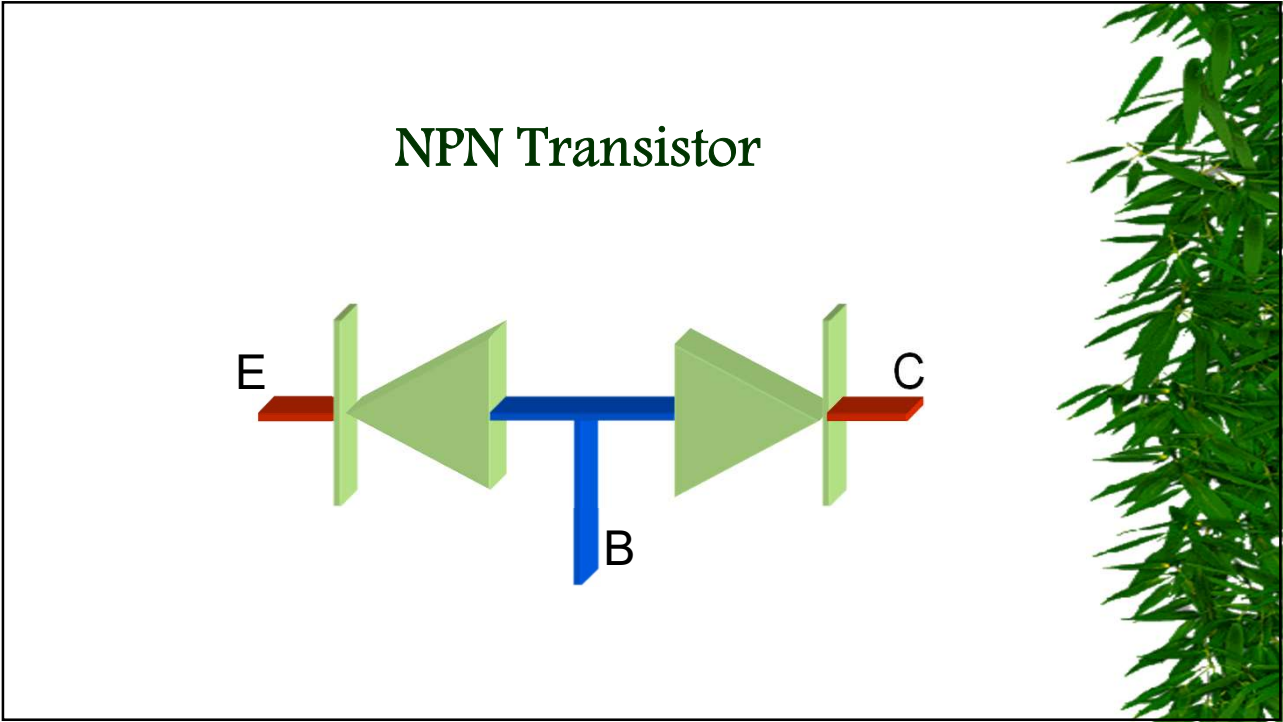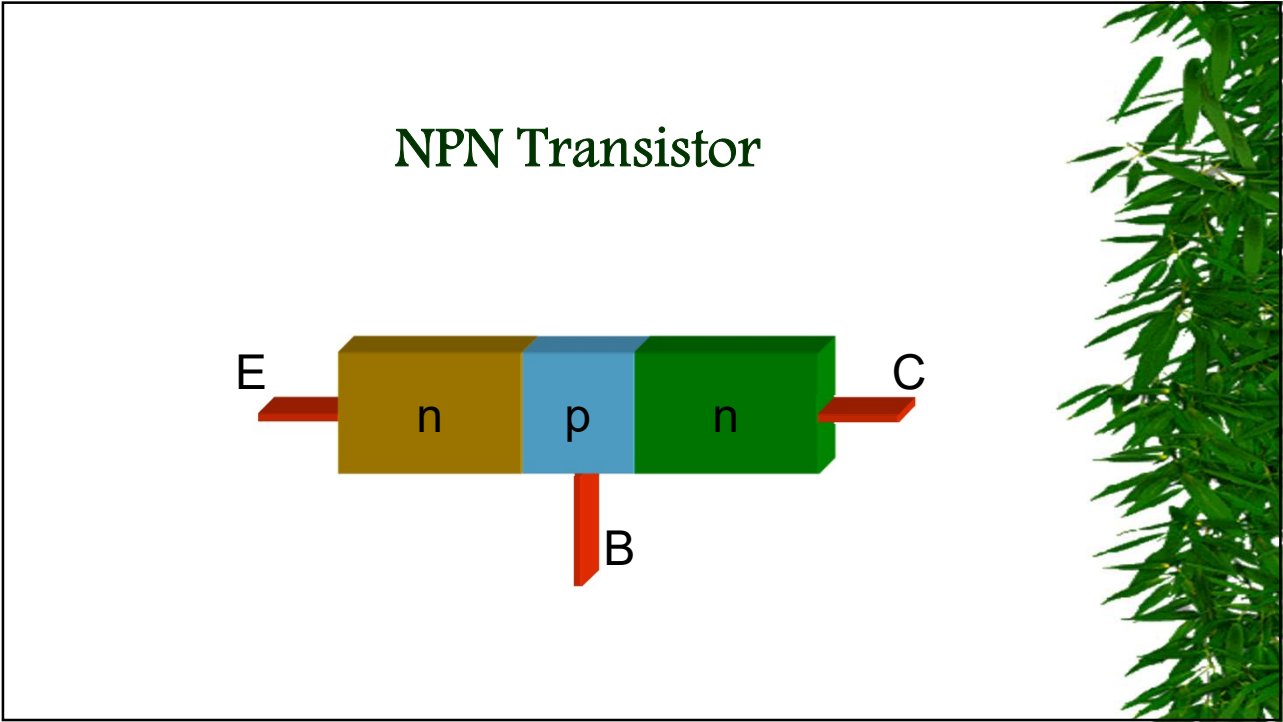

Summary

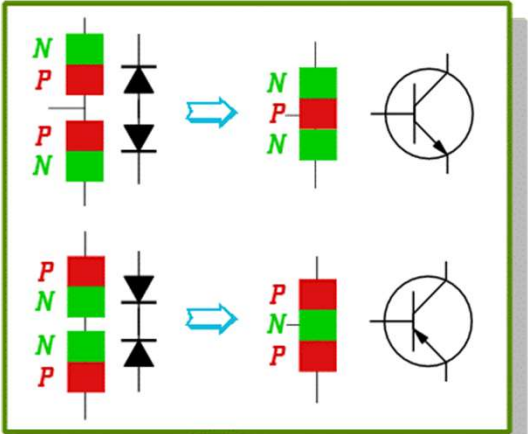

DC Bias & Operating Modes

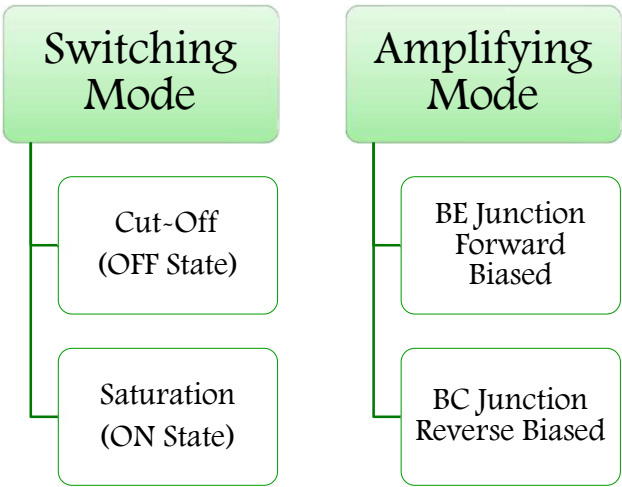

Summary of Modes

Mode & State		BIAS	
		BE	BC
Switching	Cut-Off	Rev	Rev
	Saturation	Fwd	Fwd
Amplifying	Active	Fwd	Rev

Analog & Digital


Analog Electronics

we study how transistors
are used as amplifiers


Digital Electronics

we study how they are used
as switching devices


BJT as an Amplifier

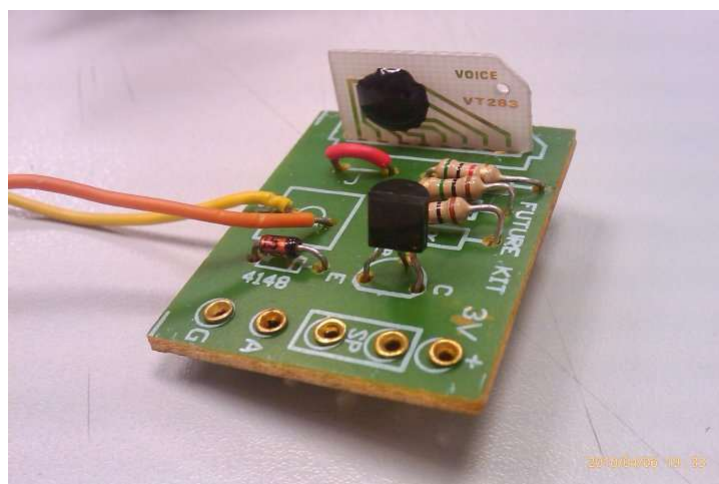


Amplification

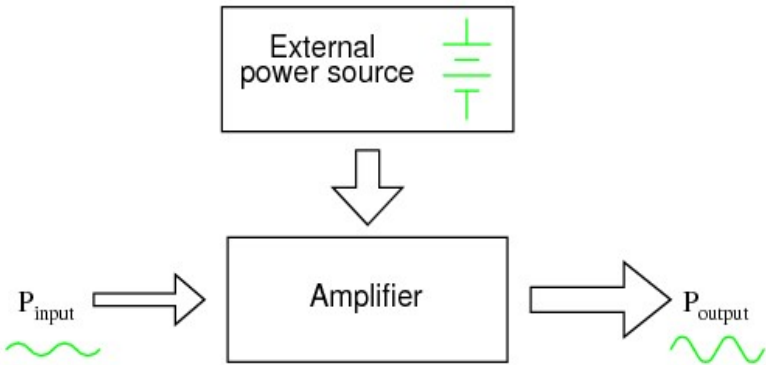


Amplification


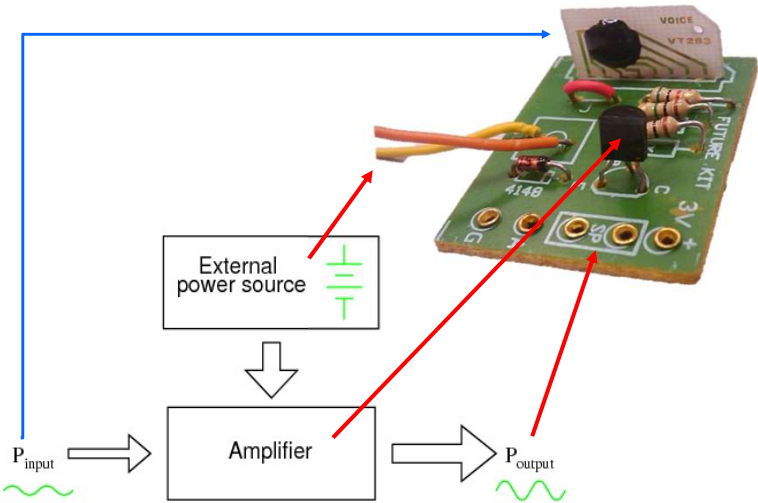


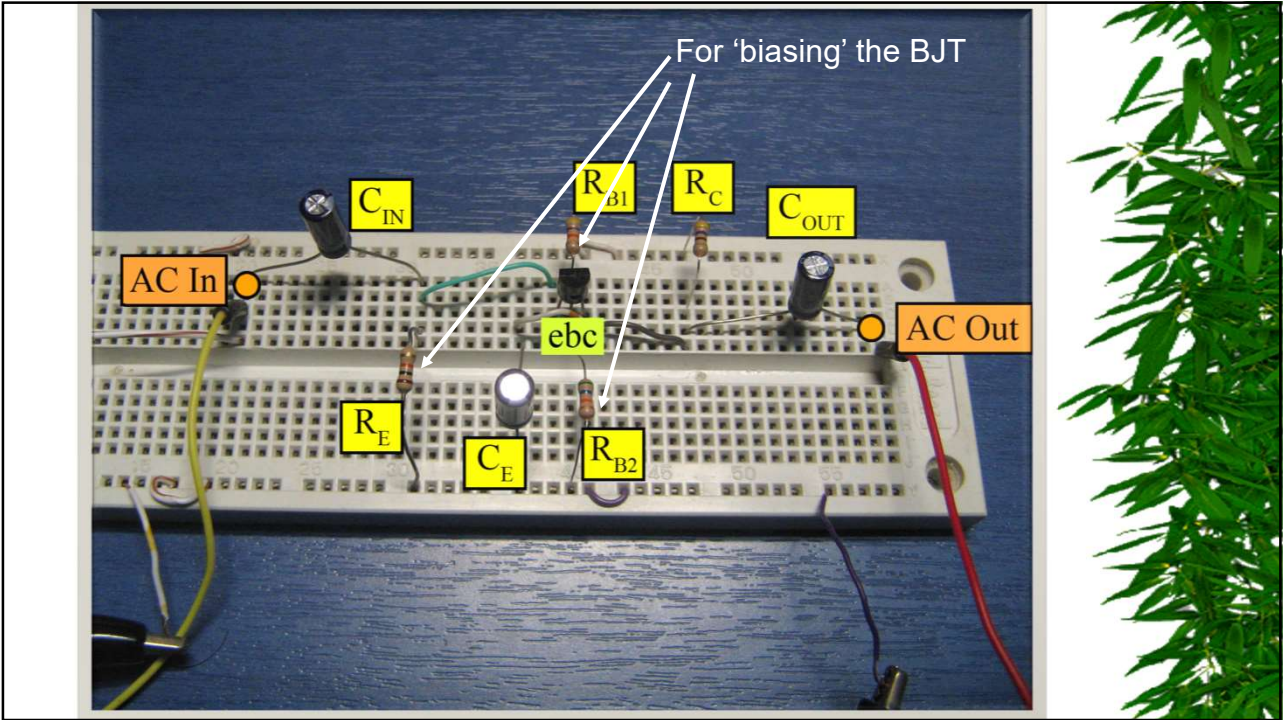

Biasing an NPN BJT for Amplifying Mode

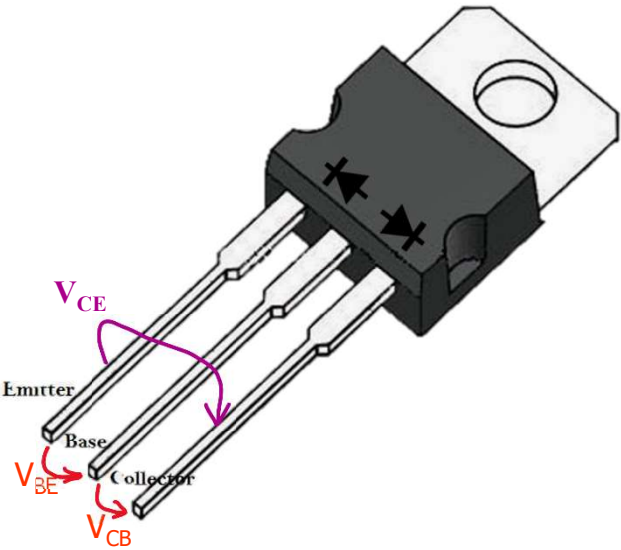


Biasing an NPN BJT for Amplifying Mode

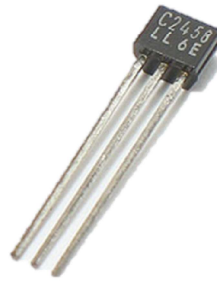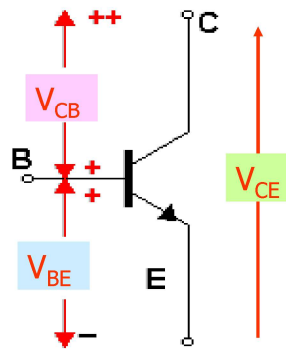

NPN BJT Biasing

- The Base must be more positive than the Emitter
- The Collector must be even more positive than the Base

Biassing the PNP BJT

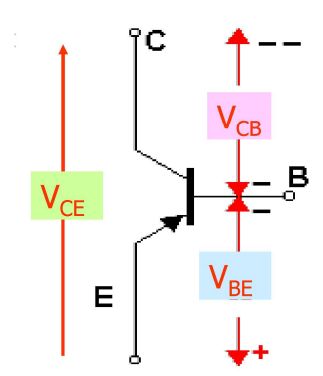

Activity

If a PNP transistor is selected, The base terminal must be more than the emitter terminal in order to forward bias the B-E junction.


The collector terminal must be even..... than the base terminal in order to reverse bias the B-C junction.

Solution

If a PNP transistor is selected, The base terminal must be more NEGATIVE than the emitter terminal in order to forward bias the B-E junction.

The collector terminal must be even MORE NEGATIVE than the base terminal in order to reverse bias the B-C junction.

External Voltages and Currents

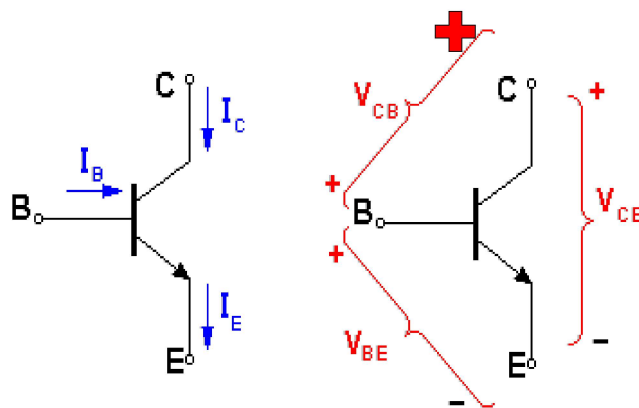


Kirchoff's Current Law


$$\mathbf{I}_E = \mathbf{I}_B + \mathbf{I}_C$$

Internal Operation of BJT


Junctions Biased by External DC sources

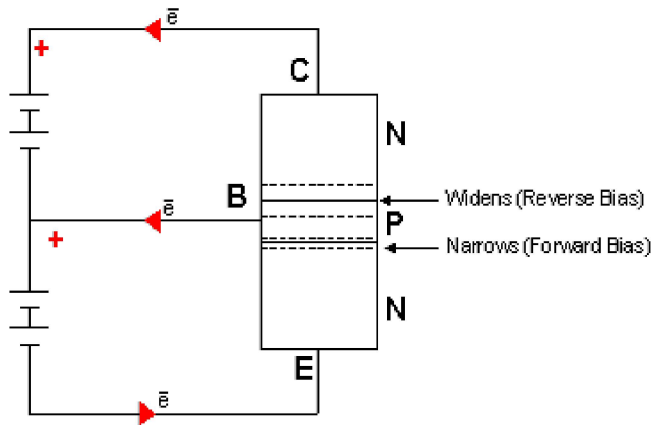


Junctions Biased by External DC sources

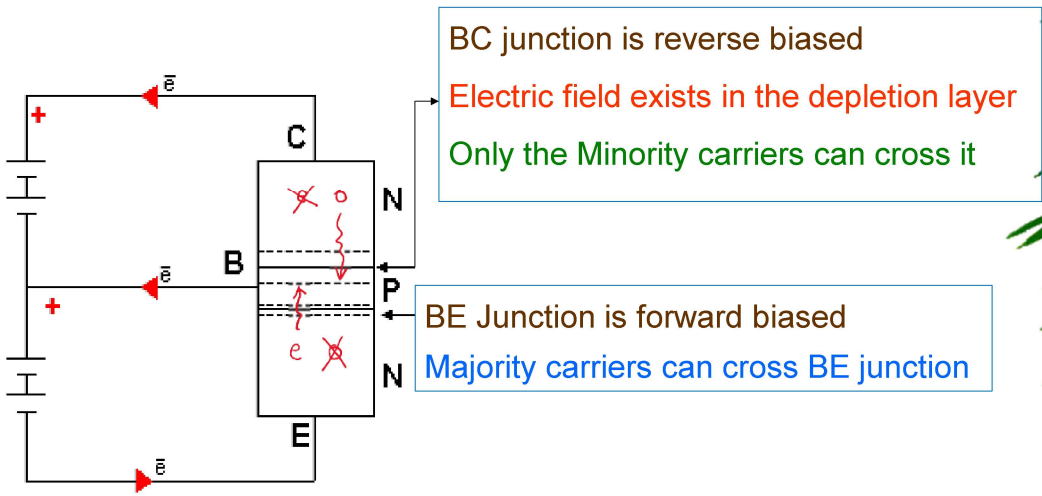

Behaviour of Current Carriers

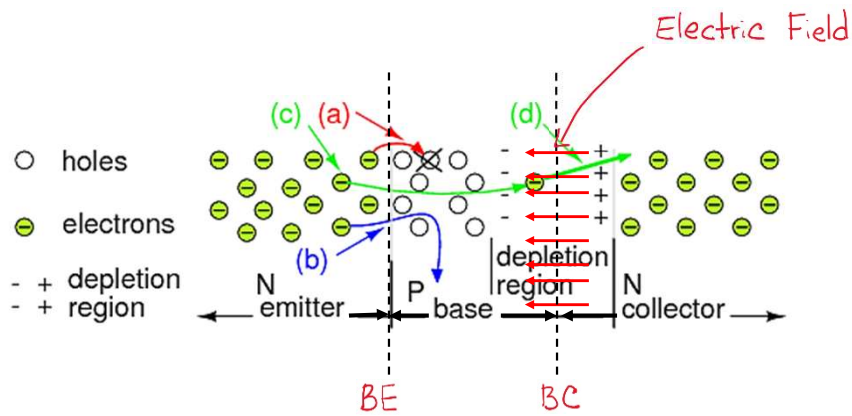

Transistor Action

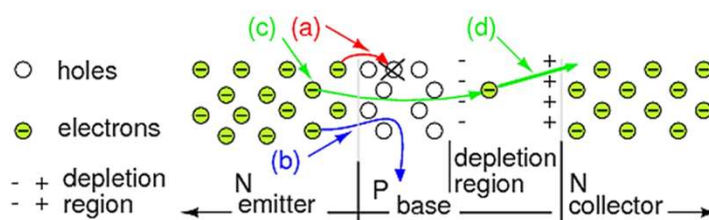


Majority carriers from emitter gets injected to the base at high velocity

But the Base is thin


Therefore most of them get caught in the electric field of BC junction

They are swept to the Collector


Rearranging the Bias Supplies

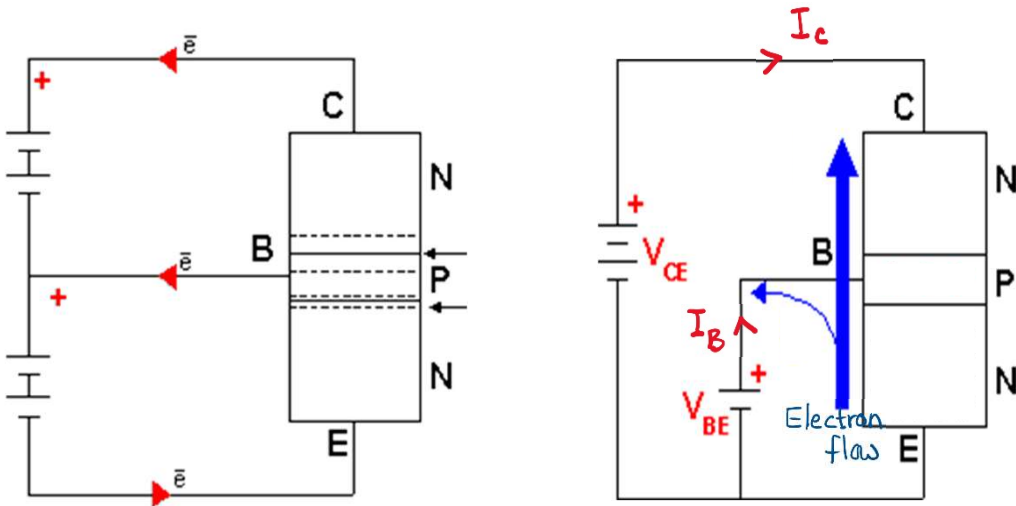


Replacing BJT with its Symbol...

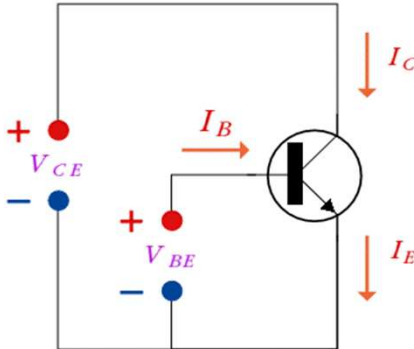

Separating Input and Output Terminals...

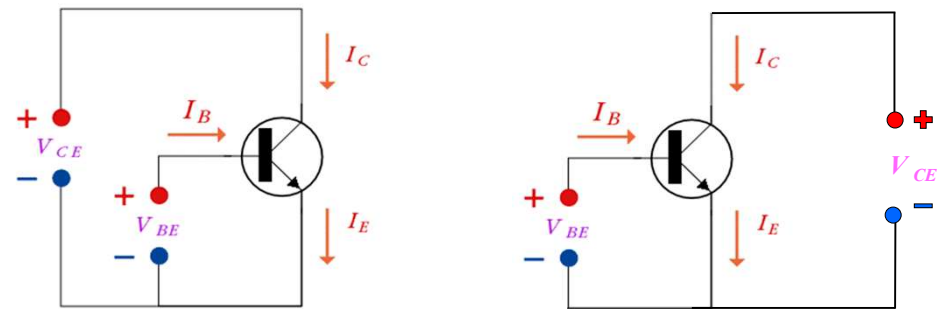

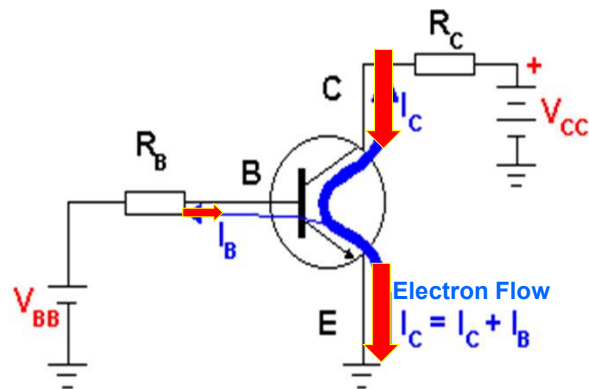Limiting Currents with External Resistors



BJT Current Relationships

Static Current Gain Concept

- * Ratio between static output current and static input current.
- * Also given as h_{FE}

$$\beta = h_{FE} = \frac{I_C}{I_B}$$

$$\alpha = h_{FB} = \frac{I_C}{I_E}$$

$$I_E = I_C + I_B$$

$$\frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$


Current Relations

$$I_C = \beta I_B$$

$$I_E = I_B + I_C$$


$$I_E = I_B + \beta I_B$$

$$I_E = (1 + \beta) I_B$$

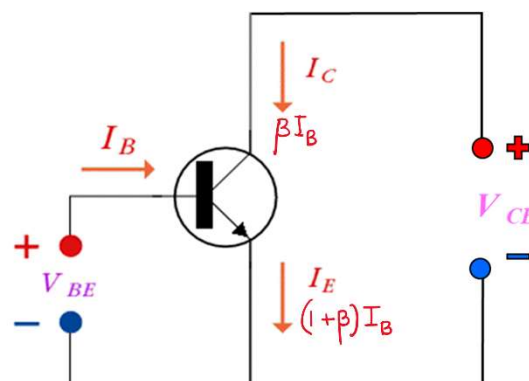

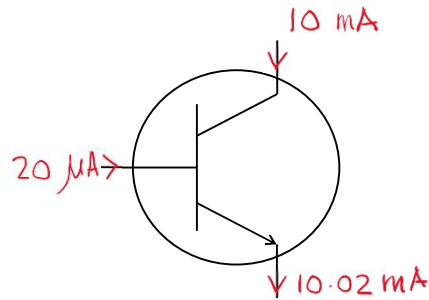Example

- * BC 109C BJT
- * $\beta = 500$ (Typ.)
- * Find currents in the three terminals when the Base current is $20\ \mu\text{A}$?



Generating a Higher Force...



Current Control Concept

- * Using a small current to **control** a larger current
- * Collector current is determined by the base current.
- * BJT is a current-controlled device.
- * Controlling + Controlled = Emitter current
- * Current means; electron and hole movement

BJT Amplifier Configurations

An Amplifier

- * An amplifier should have an input port and an output port (Four wires).




Two Ports from Three Terminals ?



- * BJT is a three terminal device !
- * Solution : Take one of it's terminals as a common terminal for both ports.

Three Amplifier Configurations

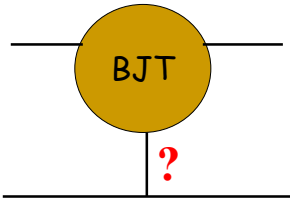


Common Base
Configuration
(CB)

Common
Emitter
Configuration
(CE)

Common
Collector
Configuration
(CC)

Three Amplifier Configurations

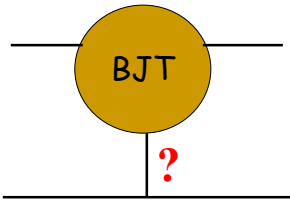


Common Base
Configuration
(CB)

Common
Emitter
Configuration
(CE)

Common
Collector
Configuration
(CC)

Three Amplifier Configurations

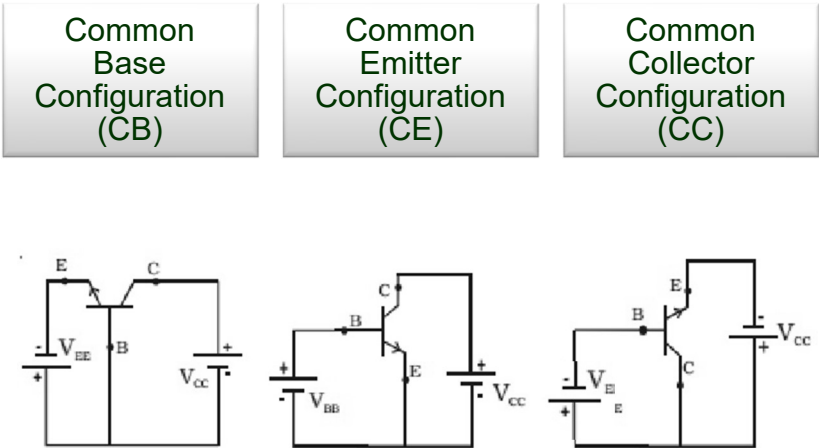

Configuration	CE	CC	CB
Voltage Gain	High	<1	High
Current Gain	High	High	<1
Power Gain	High	Moderate	Moderate
Phase Inversion	Yes	No	No
Input Impedance	Moderate (~1K)	High (~300K)	Low (~50 Ohm)
Output Impedance	Moderate (~50K)	Low (~300 Ohm)	High (~1M)